

### Tute-1

1. For silicon at  $T=300\text{K}$ , Intrinsic carrier concentration ( $n_i$ ) =  $1.45 \times 10^{10} \text{ cm}^{-3}$ . This silicon is doped at room temperature (300K) with Arsenic atoms (pentavalent), and the donor concentration is ( $N_D$ ) =  $6 \times 10^{16} \text{ cm}^{-3}$ .


Find the equilibrium concentration of electrons, holes and shift of the chemical potential (Fermi level) with respect to intrinsic chemical potential.

2. For the circuit shown, assume  $\beta = h_{FE} = 100$

a) Find if the silicon transistor is in cutoff, saturation or in the active region.

b) Find  $V_o$

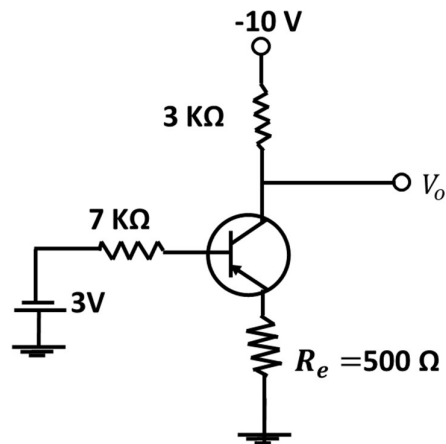
c) Find the minimum value for the emitter resistance  $R_e$  for which the transistor operates in the active region.




3. A transistor circuit is given below (silicon transistor). The transistor has a minimum value of  $\beta=30$

i) Find  $V_o$  for  $V_i = 12\text{V}$

ii) Find  $V_o$  for  $V_i = 1\text{V}$

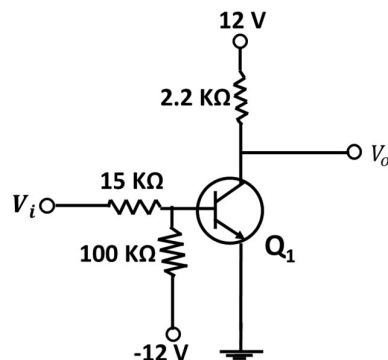


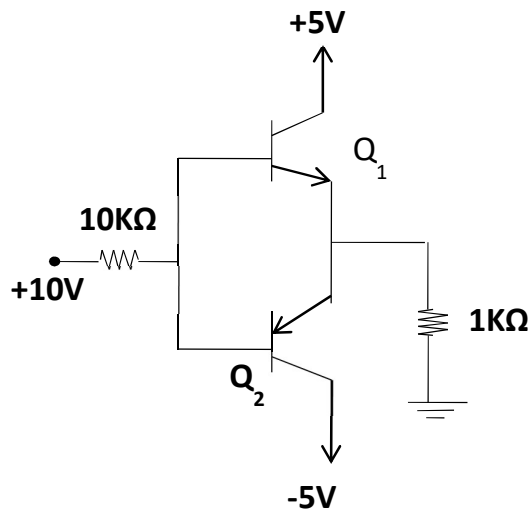Q4. Assume  $\beta_{\min}=30$ . Find  $V_B$ ,  $V_E$ ,  $I_{C1}$ ,  $I_{C2}$  for the following circuit.



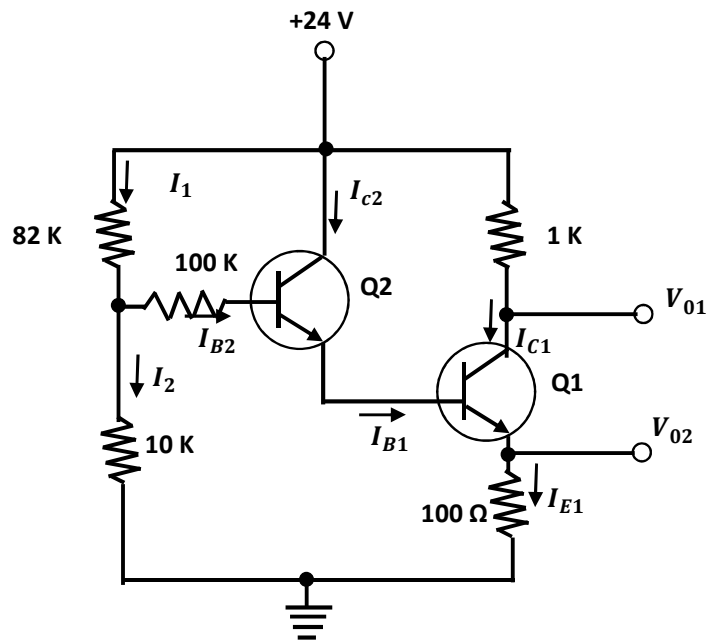Q5. For the circuit shown, transistors Q1 and Q2 operate in the active region with  $V_{BE1} = V_{BE2} = 0.7\text{ V}$ ,  $\beta_1 = 100$ , and  $\beta_2 = 50$ . The reverse saturation current may be neglected.

- Find the currents  $I_{B2}$ ,  $I_1$ ,  $I_2$ ,  $I_{C2}$ ,  $I_{B1}$ ,  $I_{C1}$ , and  $I_{E1}$
- Find the voltage  $V_{O1}$  and  $V_{O2}$



Q6. In the circuit given below, find the minimum value of  $R$ , for which one out of the two transistors remains in active region. Both the transistors are similar and made of silicon with  $\beta = 100$ , Neglect reverse saturation current

