

PH
~~EE~~-211 Electronics lab.
Experiment ~~6~~ - Integration & Differentiator Circuit
Using OP-AMP.

Name - Rohit . R

Roll No - 220121072

48
50

Experiment No - ~~6~~

Experiment Name - Integration & Differentiator Circuits
Using Operational Amplifiers.

Date - 28/06/23

Integrator and Differentiator circuits using op.amp.

A: To study the integrator and differentiator circuits using operational amplifier (IC 741).

Formula Used..

(a) Integrator Circuit

$$A = \frac{V_o}{V_i} = -\frac{R_f}{R} \left[\frac{1}{j2\pi \nu R_f C_f + 1} \right]$$

$$|A| = \frac{R_f / R}{\sqrt{1 + \omega^2 R_f^2 C_f^2}}$$

where

A = voltage gain

V_o = o/p voltage

V_i = i/p voltage

ω = Angular frequency.

R_f = feedback resistance

R = input resistance in series with V_i

ν = frequency of V_i

C_f = feedback capacitance

(b) Differentiator circuit

$$A = \frac{V_o}{V_i} = -\frac{R_f (j\omega C)}{1 + j\omega CR}$$

$$|A| = \frac{R_f \omega C}{\sqrt{1 + \omega^2 C^2 R^2}}$$

where

A = voltage gain

V_o = o/p voltage

V_i = i/p voltage

ω = angular frequency


R_f = feedback resistance

R = resistance in series with V_i


C = Capacitor

Circuit Diagram:

1) Integrator Circuit

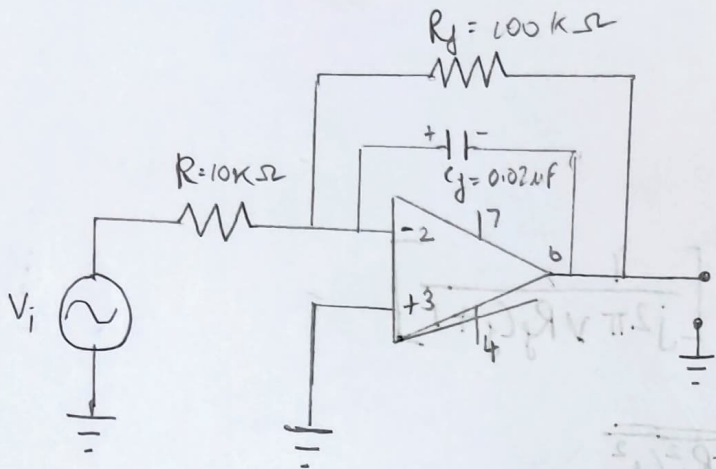


2) Differentiation Circuit

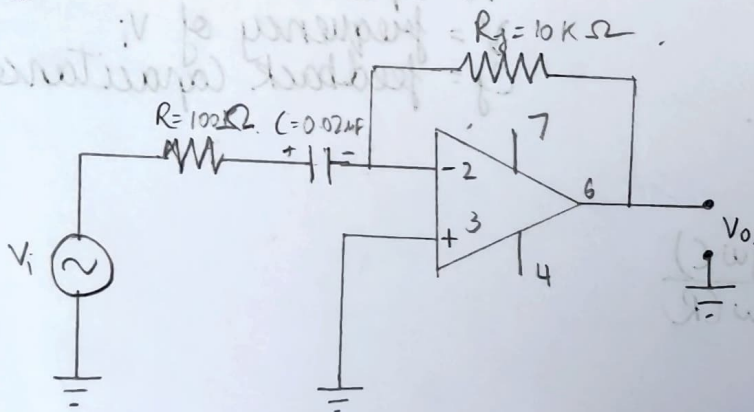


Expected Waveforms


(a) Integrator Circuit

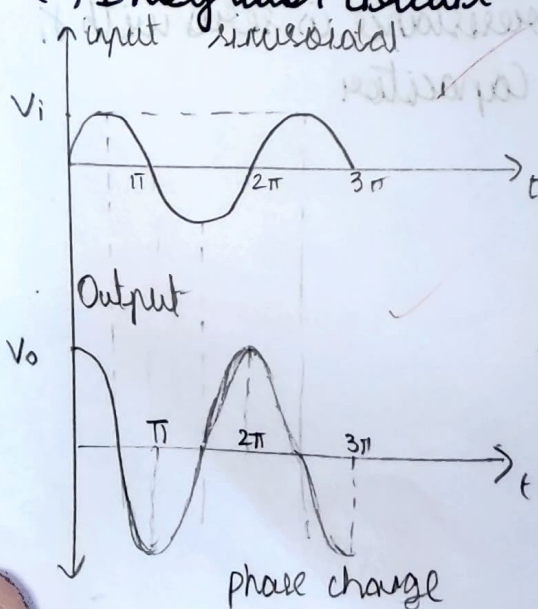

Square

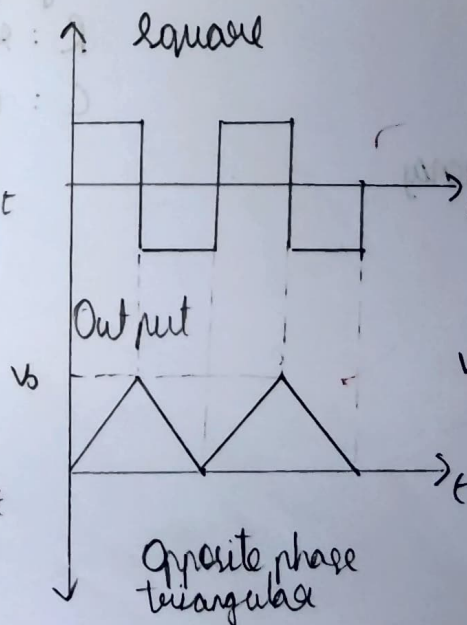

Triangular

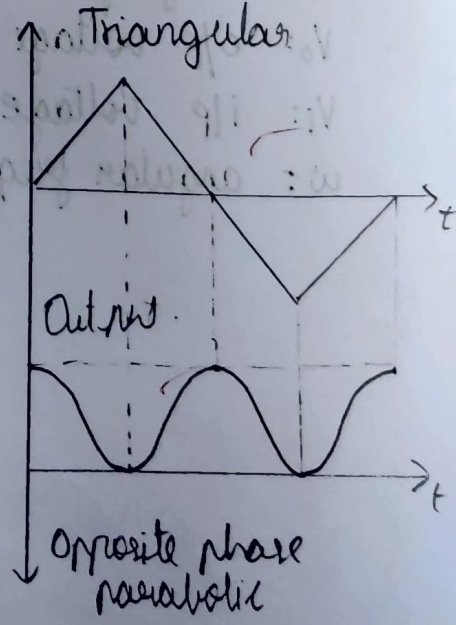

Differentiator Circuits


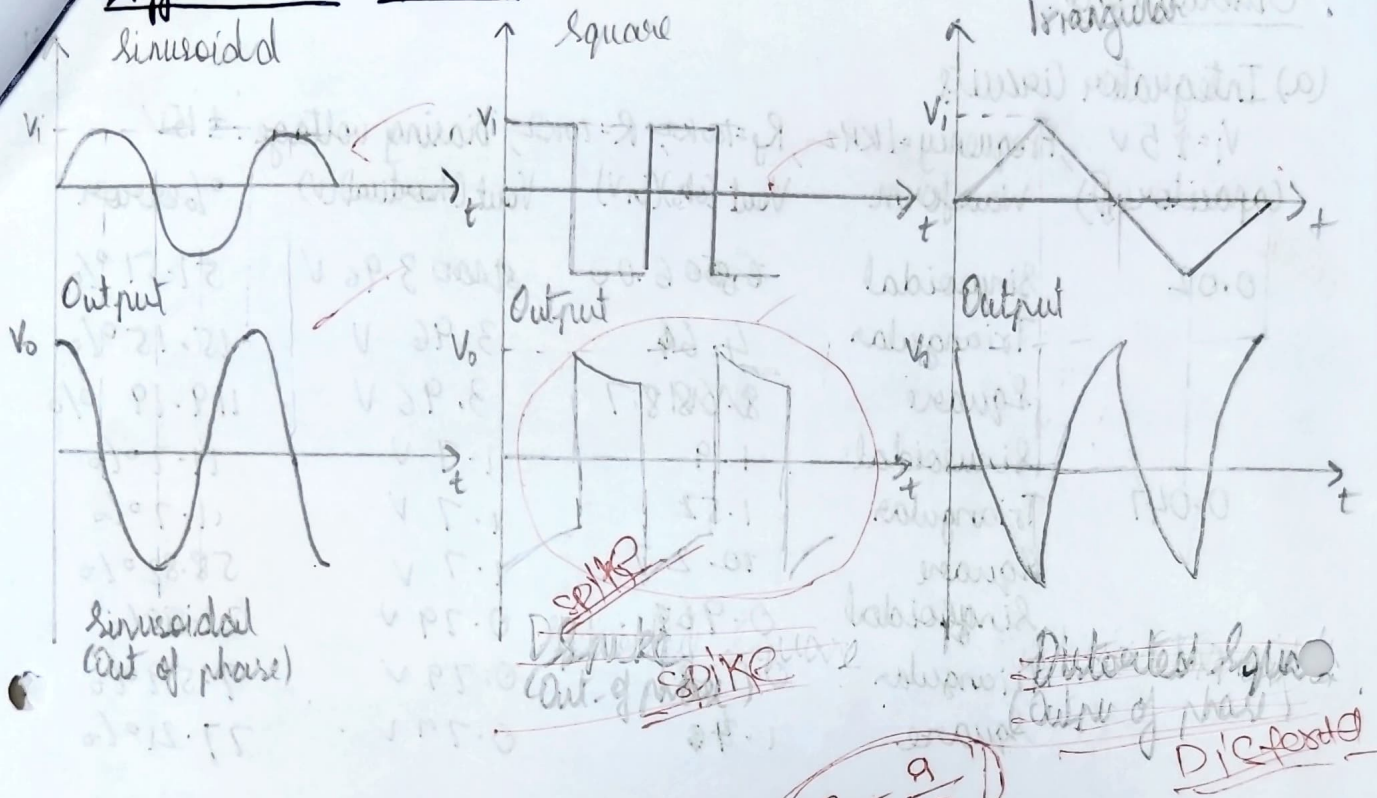


Diagram of IC 741

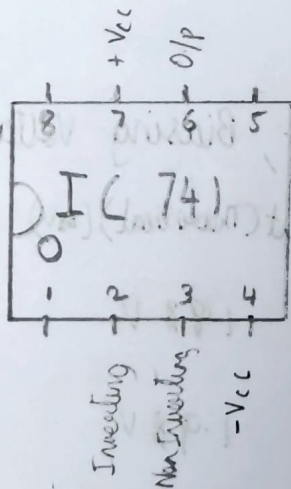

$$P_p = \frac{9}{10}$$

Observations:

(a) Integrator Circuits

$V_i = \pm 5V$, Frequency = 1 KHz, $R_f = 100k\Omega$, $R = 10k\Omega$, biasing voltage = $\pm 15V$

Capacitor (μF)	Waveform	V_{out} (obs) (in V)	V_{out} (Theoretical) (V)	% error
0.02	Sinusoidal	6.00 6.00	3.96 V	51.51%
	Triangular	4.64	3.96 V	15.15%
	Square	8.68 8.7	3.96 V	119.19%
0.047	Sinusoidal	1.9	1.7 V	11.7%
	Triangular	1.52	1.7 V	11.7%
	Square	2.7	1.7 V	58.82%
0.1	Sinusoidal	0.96	0.79 V	21.51%
	Triangular	0.73	0.79 V	7.59%
	Square	1.4	0.79 V	77.21%

(b) Differentiator Circuits

$V_i = \pm 1.5V$, $C_f = 0.02 \mu F$, Frequency = 1 KHz, Biasing Voltage = $\pm 15V$

Waveform	V_{out} (obs) (in mV)	V_{out} (Theoretical) (mV)	% error
Sinusoidal	2.0 V	1.9 V	10.5%
Triangular	2.2 2.0 V	1.9 V	10.5%
Square	27.6 V	1.9 V	1352.6%

→ Apparatus:

Digital storage Oscilloscope, function generator, Multiple power supply, bread board, connecting wires, capacitors (0.02 μF , 0.047 μF , 0.1 μF) resistors (100 Ω , 10k Ω , 100k Ω), Opamp (IC 741) and Multimeter.

At 10

Integration circuit




V_i

Sinusoidal
 $\omega = 1000 \text{ Hz}$
 $V_i = 5 \text{ V}_{p-p}$



V_o

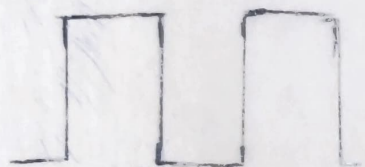

V_i


Square wave
 $\omega = 1000 \text{ Hz}$
 $V_i = 5 \text{ V}_{p-p}$



V_o



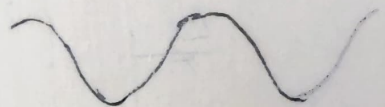Triangular
 $\omega = 1000 \text{ Hz}$
 $V_i = 5 \text{ V}_{p-p}$



$C_F = 0.02 \mu\text{F}$
 $R_F = 100 \text{ k}\Omega$
 $R_1 = 10 \text{ k}\Omega$

Differentiator




Sinusoidal



Triangular



Square

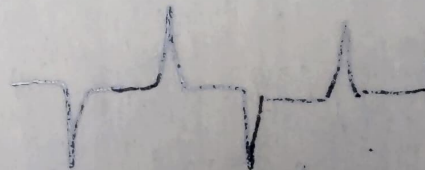

$V_i = 1.5 \text{ V}_{p-p}$
 $R_F = 10 \text{ k}\Omega$
 $R_1 = 100 \Omega$
 $C_F = 0.02 \mu\text{F}$
 $F = 1000 \text{ Hz}$

ulation:

(a) Integrator Circuits

$$A = \frac{R_f R}{\sqrt{1 + \omega^2 R_f^2 C^2}}$$

$$R_f = 100 \text{ K}\Omega, R = 10 \text{ K}\Omega$$

$$\omega = 2\pi \times 10^3$$

$$V_i = 5 \text{ V}$$

① $C_f = 0.02 \mu\text{F}$

$$A = \frac{10}{\sqrt{1 + (2\pi \times 10^3)^2 (10^{-6})^2 (0.02)^2 \times (10^3)^2}} = 0.79$$

$$\therefore V_o = V_i \times A = \cancel{0.79} \times 5 = 3.96 \text{ V}$$

② $C_f = 0.047 \mu\text{F}$

$$A = \frac{10}{\sqrt{1 + 872}} = 0.34$$

$$\therefore V_o = \cancel{0.34} \times 5 = 1.70 \text{ V}$$

③ $C_f = 0.01 \mu\text{F}$

$$A = \frac{10}{\sqrt{1 + 3947}} = 0.1597$$

$$\therefore V_o = 0.79 \text{ V}$$

④ $C_f =$

$$A = \frac{10}{\sqrt{1 + 3947}} = 0.1597$$

(b) Differentiator Circuits

$$V_i = 1 \text{ V}$$

$$|A| = \frac{R_f \omega C}{\sqrt{1 + \omega^2 R_f^2 C^2}}$$

$$R_f = 10 \text{ K}\Omega, C = 0.02 \mu\text{F}$$

$$R = 100 \text{ K}\Omega, V_i = 1000 \text{ Hz}$$

$$\therefore A = \frac{10 \times 2\pi \times 1000 \times 0.02 \times 10^{-6}}{\sqrt{1 + (2\pi \times 1000 \times 10 \times 10^{-6})^2}} = 1.25$$

$$V_o = V_i \times A = 1.88 \text{ V}$$

cal = 1.88

Result:

1. In the integrator circuit, as the value of the capacitor increases the output voltage decreases
2. The output of the square waveform shows maximum error



3. Integrator Circuit

Input	Output
Sinusoidal	Sinusoidal
Triangular	Parabolic
Square	Triangular

Differentiator

Input	Output
Sinusoidal	Sinusoidal
Triangular	Distorted Square
Square	Spikes (Dirac-delta)

Precautions and Discussion

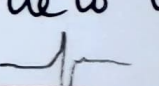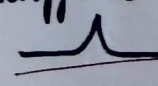1. Make sure that all connections are tight
2. Apply biasing voltage between 12-15 V
3. Keep $V_{in} \leq 2V$ during differentiation circuit
4. Ensure that the polarity of capacitor is carefully checked and the circuit made keeping its polarity in mind
5. In the integrator circuits triangular waveform generally has the least amount of error while the square waveform has the most error
6. There is generally a larger error in this experiment due to resistance in the operational amplifier along with variance in the resistance of resistor & capacitance of capacitor
7. The voltage that is given at the input should be reduced until there is no clipping observed in the output
8. The most amount of error is seen on the spots where there is distortion in the input voltage due to noise.
9. Due to this in the differentiator circuit we get a waveform of  instead of  which results in a higher than average error.
10. The same is observed in Integrator circuit where square waves have much higher % error due to noise.
9. In the integrator circuit the V_{out} decreases as the capacitance increases