


GENERAL -PURPOSE PROGRAMMABLE PERIPHERAL DEVICES.

The 8255A Programmable Peripheral
Interface.


- ◉ The 8255A is a widely used, programmable, parallel I/O device.
- ◉ It can be programmed to transfer data under various conditions, from simple I/O to interrupt I/O.
- ◉ It is flexible, versatile, and economical (when multiple I/O ports are required), but somewhat complex.
- ◉ It is an important general-purpose I/O device that can be used with almost any microprocessor.

- ◉ The 8255A has 24 I/O pins that can be grouped primarily in two 8-bit parallel ports: A and B, with the remaining eight bits as port C.
- ◉ The eight bits of port C can be used as individual bits or be grouped in two 4 bit ports: C_{UPPER} (C_U) and C_{LOWER} (C_L).
- ◉ The functions of these ports are defined by writing a control word in the control register.

8255 I/O PORTS (A) AND THEIR MODES (B)

 


(a)

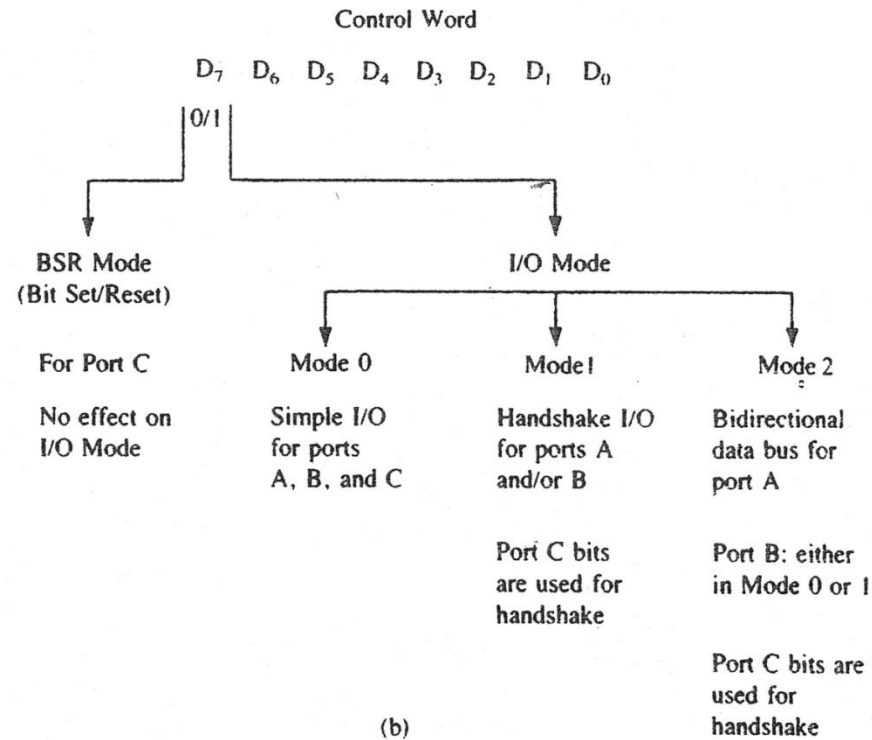


(b)

- ◉ The BSR mode is used to set or reset the bits in port C.
- ◉ The I/O mode is further divided into three modes: Mode 0, Mode 1, and Mode 2.
- ◉ In Mode 0, all ports function as simple I/O ports.
- ◉ Mode 1 is a handshake mode whereby ports A and/or B use bits from port C as handshake signals. In the handshake mode, two types of I/O data transfer can be implemented:
 - ◉ (1) status check (2) interrupt.
- ◉ In Mode 2, port A can be set up for bidirectional data transfer using handshake signals from port C, and port B can be set up either in Mode 0 or Mode 1.


BLOCK DIAGRAM OF THE 8255A.

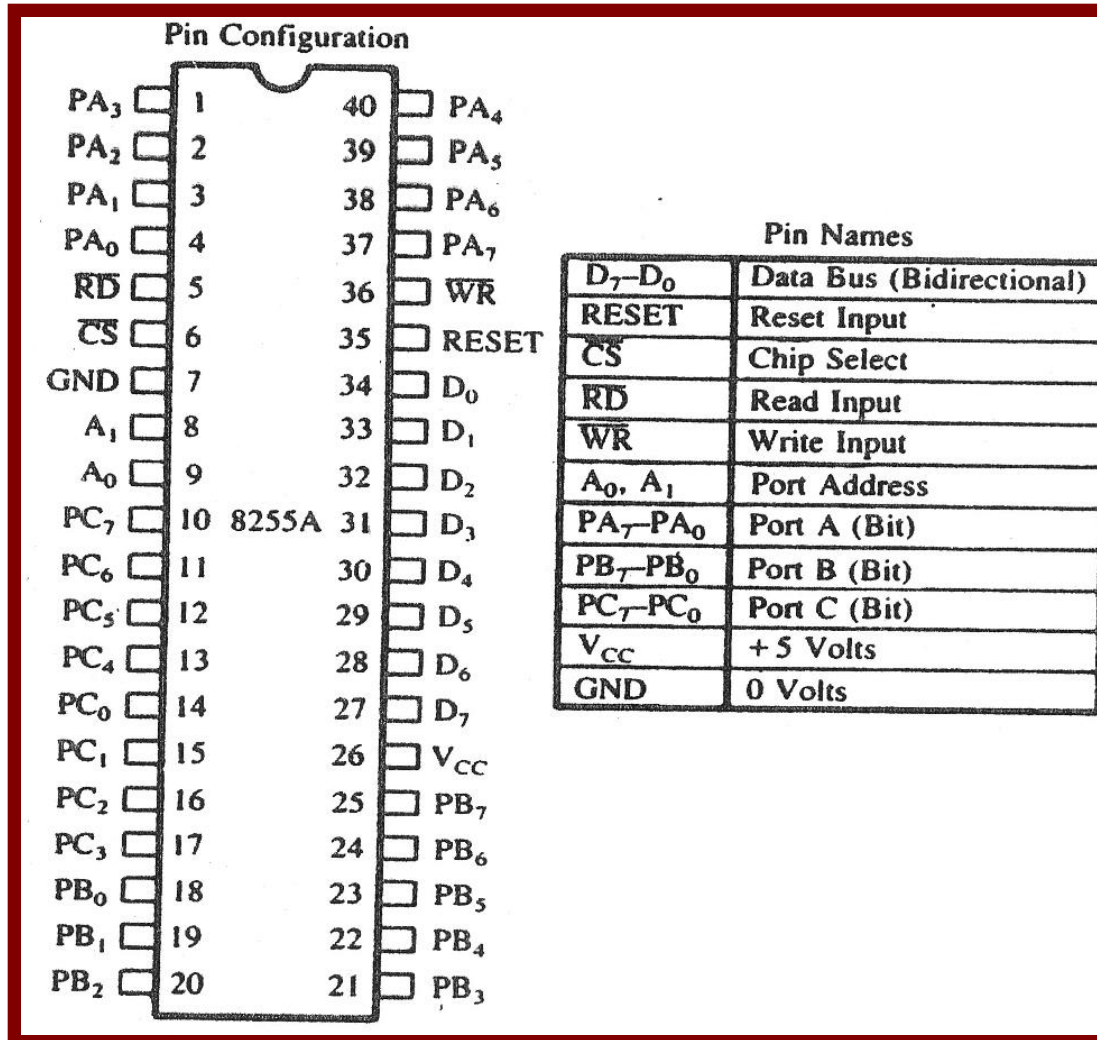

BLOCK DIAGRAM.

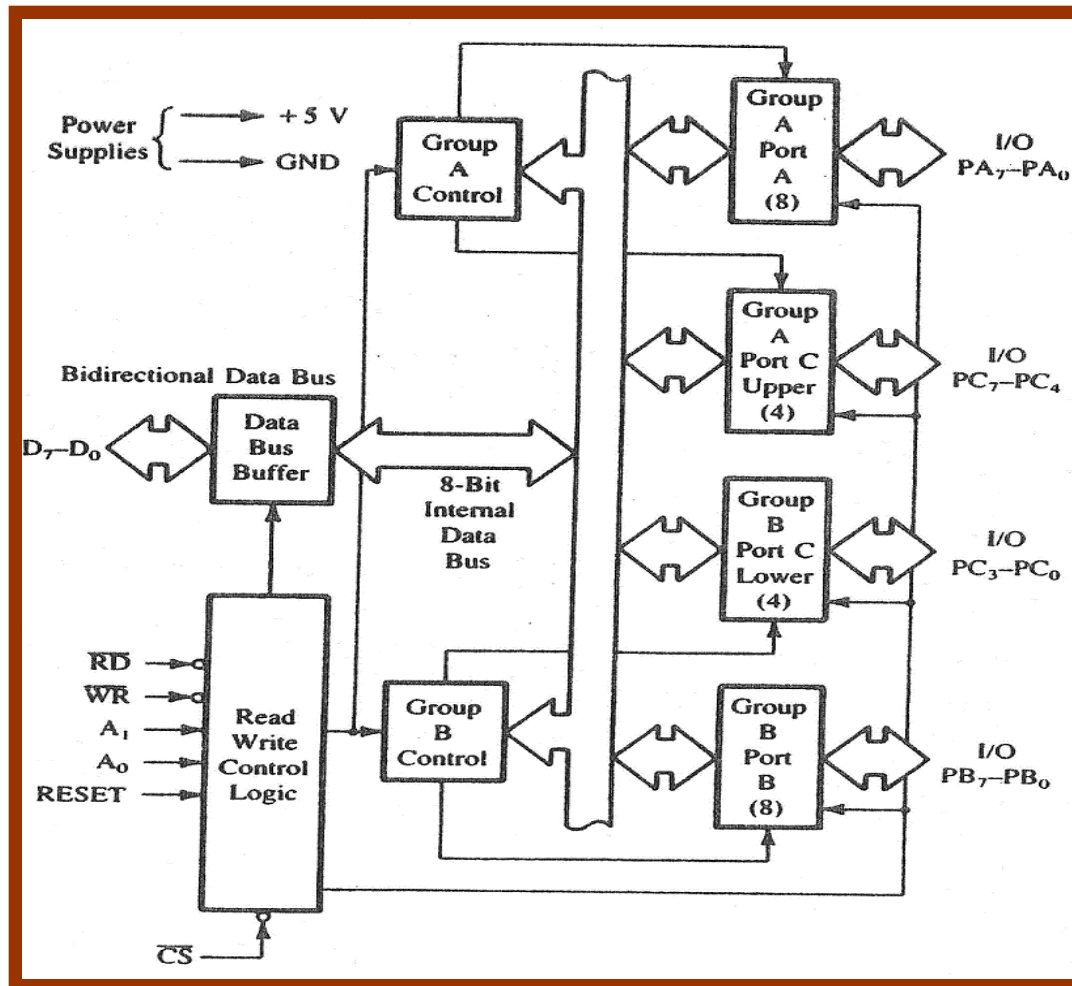

EXPANDED VERSION OF THE CONTROL LOGIC.

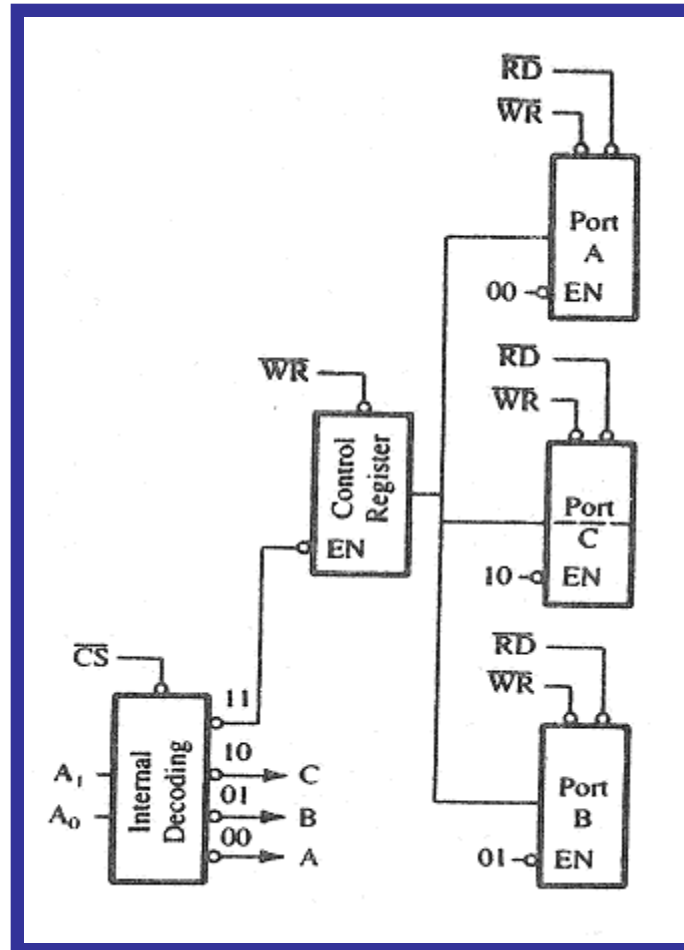

BLOCK DIAGRAM DESCRIPTION.

- ⦿ The block diagram shows two 8-bit ports (A and B),
- ⦿ Two 4-bit ports (C_U and C_L)
- ⦿ The data bus buffer, and control logic.
- ⦿ Simplified but expanded version of the internal structure, including a control register.
- ⦿ This block diagram includes all the elements of a programmable device; port C performs functions similar to that of the status register in addition to providing handshake signals.

CONTROL LOGIC.

- ◉ The control section has six lines. Their functions and connections are as follows:
- ◉ RD (Read): This control signal enables the Read operation. When the signal is low, the MPU reads data from a selected I/O port of the 8255A.
- ◉ WR (Write): This control signal enables the Write operation. When the signal goes low, the MPU writes into a selected I/O port or the control register.


- ◉ RESET (Reset): This is an active high signal; it clears the control register and sets all ports in the input mode.
- ◉ CS, A0, A1: These are device select signals. CS is connected to a decoded address, and A0 and A1 are generally connected to MPU address lines A0 and A1, respectively.

- ◉ The CS signal is the master chip select, and A0 and A1 specify one of the I/O ports or the control register as given below:

CS	A1	A0	Selected
0	0	0	port A
0	0	1	Port B
0	1	0	Port C
0	1	1	Control Register
1	x	x	8255 is not selected.

- ◉ The port addresses are determined by the CS, A0, and A1 lines.
- ◉ The CS line goes low when $A7 = 1$ and A6 through A2 are at logic 0.
- ◉ When these signals are combined with A0 and A1, the port addresses range from 80H to 83H.

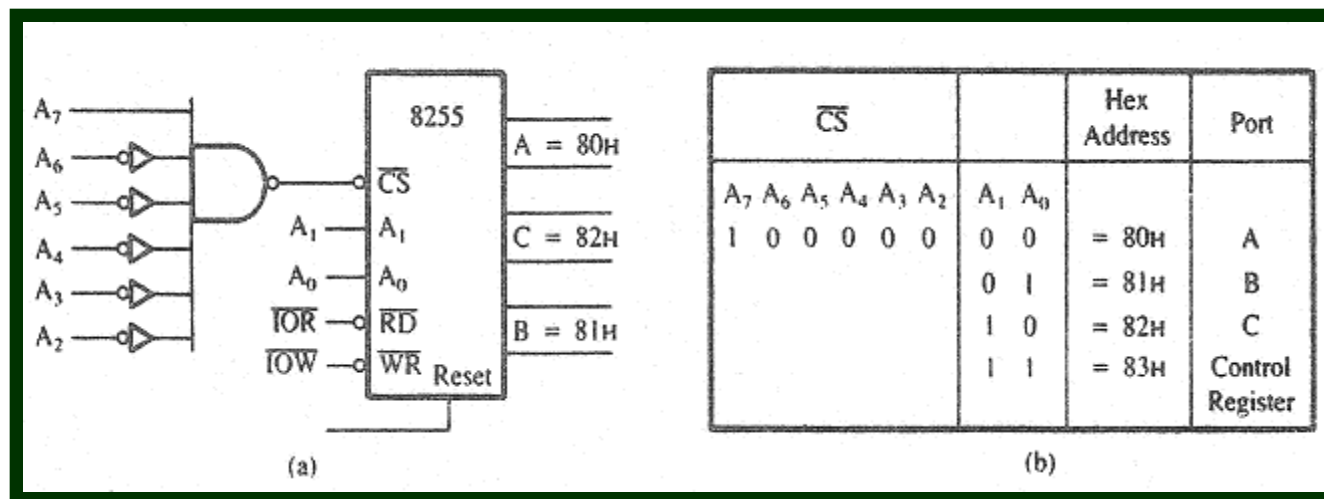
8255 CHIP SELECT LOGIC & I/O PORT ADDRESS.



CONTROL WORD

- ◉ The contents of Control register, called the control word, specify an I/O function for each port.
- ◉ This register can be accessed to write a control word when A0 and A1 are at logic 1, as mentioned previously.
- ◉ The register is not accessible for a read operation.

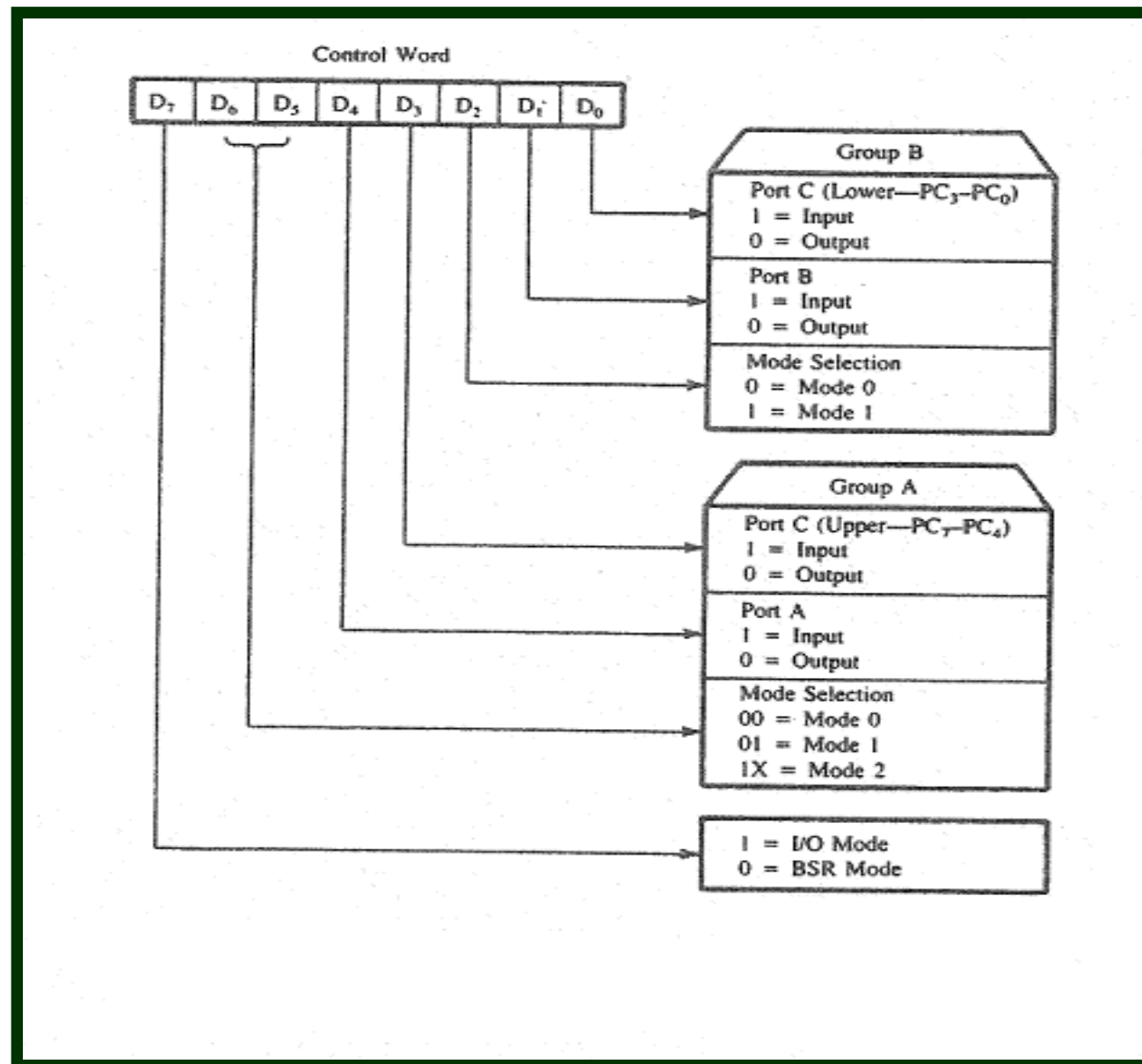- ⦿ Bit D_7 of the control register specifies either the I/O function or the Bit Set/Reset function.
- ⦿ If bit $D_7 = 1$, Bits D_6 - D_0 determine I/O functions in various modes.
- ⦿ If bit $D_7 = 0$, port C operates in the Bit Set/Reset (BSR) mode.
- ⦿ The BSR control word does not affect the functions of ports A and B.



- ◎ To communicate with peripherals through the 8255A, three steps are necessary:
 1. Determine the addresses of ports A, B, and C and of the control register according to the Chip Select logic and address lines A0 and A1.
 2. Write a control word in the control register.
 3. Write I/O instructions to communicate with peripherals through ports A, B, and C.


MODE 0: SIMPLE INPUT OR OUTPUT

- ⦿ Ports A and B are used as two simple 8-bit I/O ports
- ⦿ Port C as two ,4- bit ports
- ⦿ The input/output features in Mode 0 are as follows:
 1. Outputs are latched.
 2. Inputs are not latched.
 3. Ports do not have handshake or interrupt capability.

EXAMPLE

1. Identify the port addresses in Figure shown.
2. Identify the Mode 0 control word to configure port A and port C_U as output ports and port B and port C_L , as input ports.
3. Write a program to read the DIP switches and display the reading from port B at port A and from port C_L at port C_U .

INTERFACING 8255A I/O PORTS.

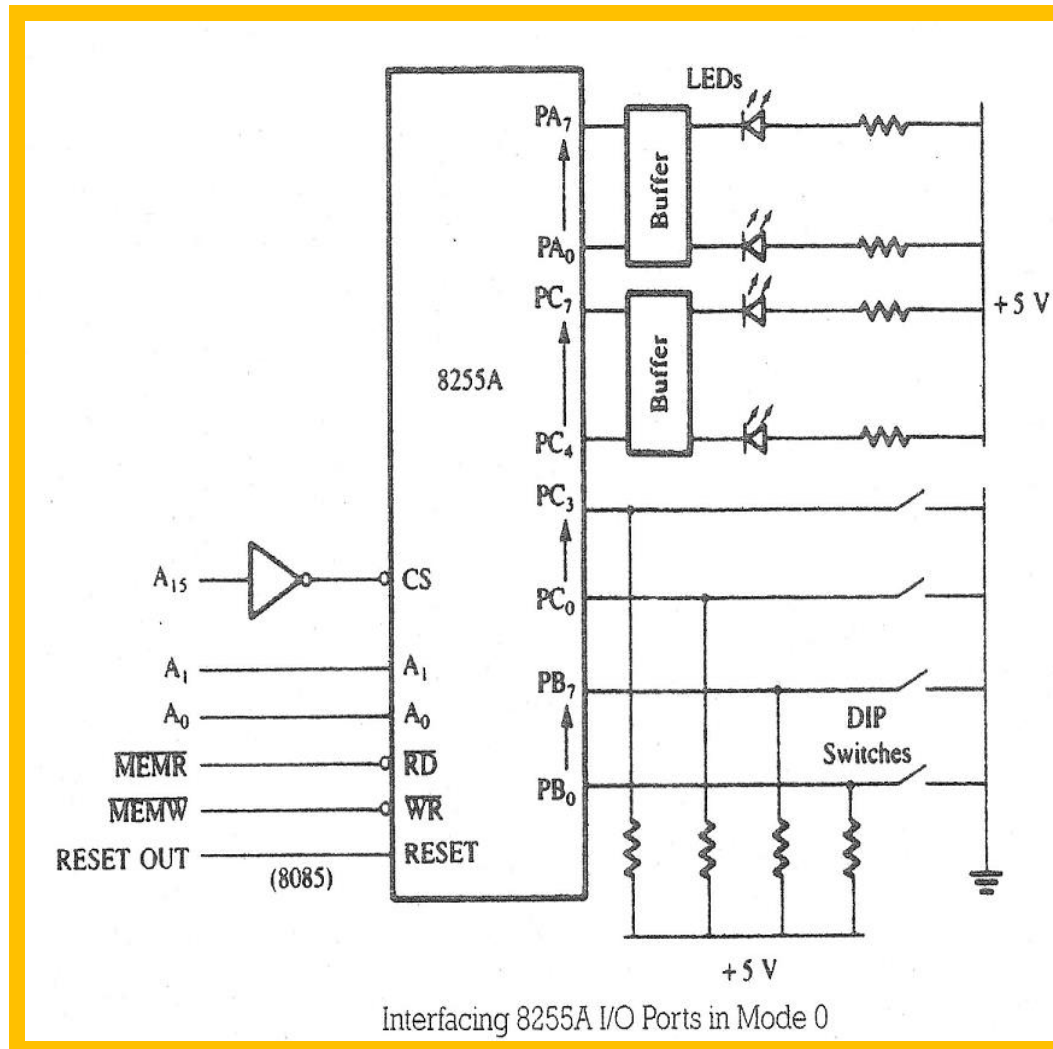

SOLUTION:

I. Port Addresses

- ⦿ This is a memory-mapped I/O; when the address line A_{15} is high, the Chip Select line is enabled. Assuming all don't care lines are at logic 0, the port addresses are as follows:


Port A = 8000H ($A_1 = 0, A_0 = 0$)

Port B = 8001H ($A_1 = 0, A_0 = 1$)

Port C = 8002H ($A_1 = 1, A_0 = 0$)

Control Register = 8003H ($A_1 = 1, A_0 = 1$)

Control Word

 


PROGRAM:

- ◉ MVI A,83H ; Load accumulator with the control word
- ◉ STA 8003H ; Write word in the control register to initialize the ports
- ◉ LDA 8001H ; Read switches at port B
- ◉ STA 8000H ; Display the reading at port A
- ◉ LDA 8002H ; Read switches at port C
- ◉ ANI 0FH ; Mask the upper four bits of port C; these ; bits are not input data
- ◉ RLC ; Rotate and place data in the upper half ; of the accumulator
- ◉ RLC
- ◉ RLC
- ◉ RLC
- ◉ STA 8002H ; Display data at port C1
- ◉ HLT

BSR (BIT SET/RESET) MODE:

- ◉ The BSR mode is concerned only with the eight bits of port C, which can be set or reset by writing an appropriate control word in the control register.
- ◉ A control word with bit $D_7 = 0$ is recognized as a BSR control word, and it does not alter any previously transmitted control word with bit $D_7 = 1$; thus the I/O operations of ports A and B are not affected by a BSR control word.
- ◉ In the BSR mode, individual bits of port C can be used for applications such as an on/off switch.

BSR CONTROL WORD:

 

EXAMPLE:

- Write a BSR control word subroutine to set bits PC_7 and PC_3 and reset them after 10 ms. Use the schematic in Figure 8255A Chip select logic and assume that a delay subroutine is available.

SOLUTION: BSR CONTROL WORDS

		D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	
To set bit PC ₇	=	0	0	0	0	1	1	1	1	= 0FH
To reset bit PC ₇	=	0	0	0	0	1	1	1	0	= 0EH
To set bit PC ₃	=	0	0	0	0	0	1	1	1	= 07H
To reset bit PC ₃	=	0	0	0	0	0	1	1	0	= 06H

PORT ADDRESS:

- ◉ Control register address = 83 H;

SUBROUTINE:

```
BSR:  MVI A,0FH      ;Load byte in accumulator to set PC7
      OUT 83H        ;Set PC7 = 1
      MVI A,07H      ;Load byte in accumulator to set PC3
      OUT 83H        ;Set PC3 = 1
      CALL DELAY      ;This is a 10-ms delay
      MVI A,06H      ;Load accumulator with the byte to reset PC3
      OUT 83H        ;Reset PC7
      MVI A,0EH      ;Load accumulator with the byte to reset PC7
      OUT 83H        ;Reset PC7
      RET
```

- ◉ From an analysis of the above routine, the following points can be noted:
 1. To set/reset bits in port C, a control word is written in the control register and not in port C.
 2. A BSR control word affects only one bit in port C.
 3. The BSR control word does not affect the I/O mode.