

PH211 - Electronics Lab

Arithmetic & Amplifier Circuits using Opamps .

Name - Rohit Ramabhadran

Roll no. 220121072

49
50

Expt. No - 3


Expt. Name - Arithmetic & Amplifier Circuits using Opamp

Date - 21/08/23


(a) an inverting amplifier (b) a non inverting amplifier (c) adder circuit and (d) subtractor circuit using 741 opamp.

Circuit Diagram:


(a) Non Inverting Circuit

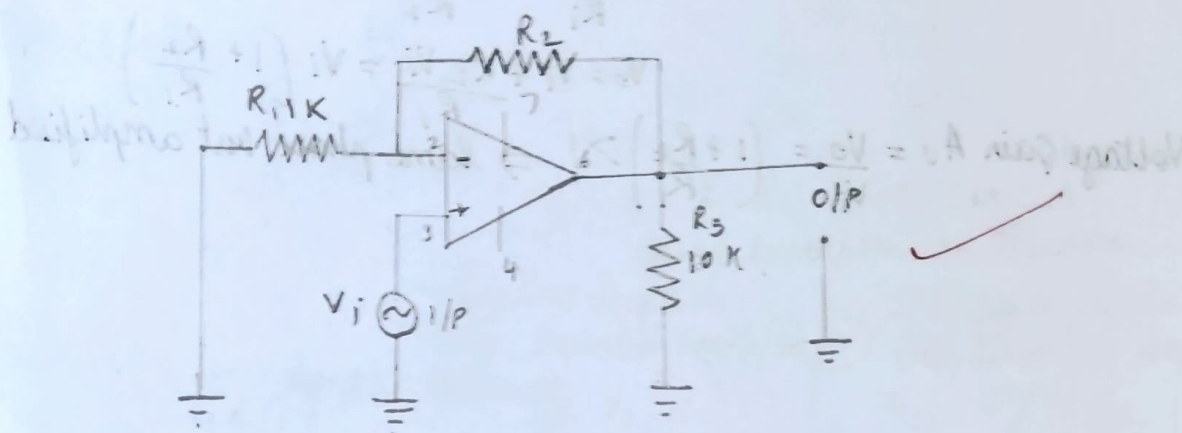


(b) Inverting Circuit.

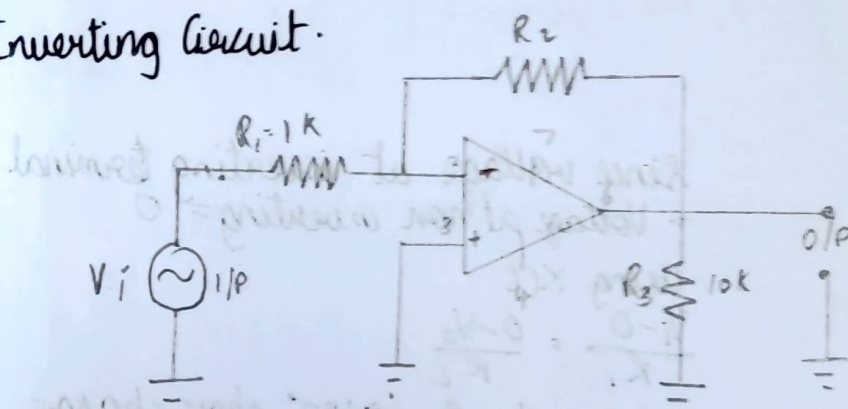

(c) Adder Circuit.

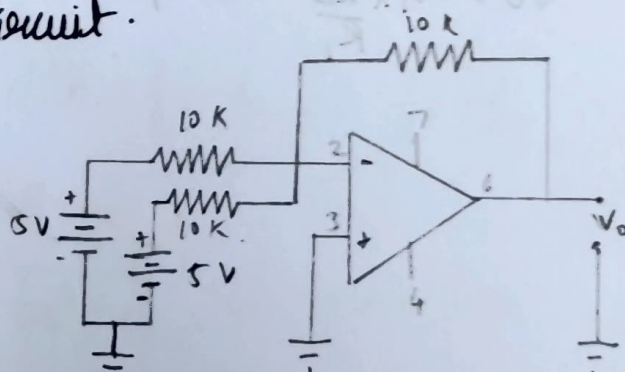


(d) Subtractor Circuit.

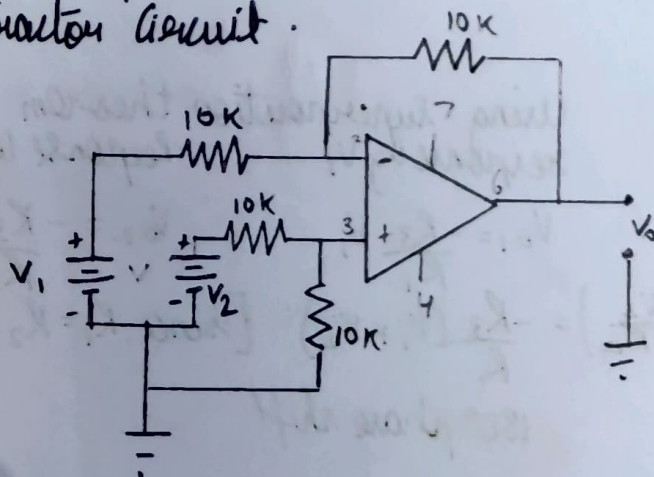

Formulas & expected output waveform:

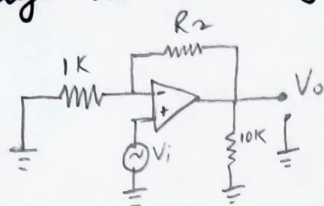(a) Non-inverting amplifier
 Since voltage at inverting and non-inverting terminal equal = V_i




Using KCL at inverting terminal

$$\frac{0 - V_i}{R_1} = \frac{V_i - V_o}{R_2}$$


$$V_o = V_i + \frac{R_2}{R_1} V_i = V_i \left(1 + \frac{R_2}{R_1} \right)$$

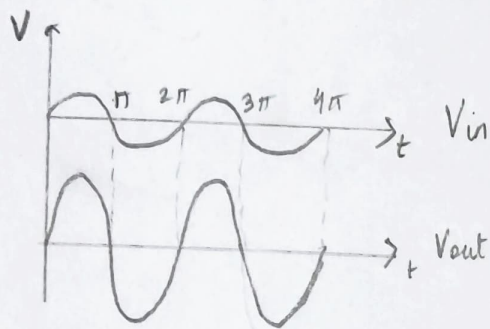Voltage Gain $A_v = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1} \right) > 1 \Rightarrow$ same phase but amplified



Expected Output

(b) Inverting Amplifier

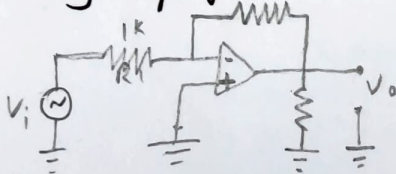


Since voltage at inverting terminal = Voltage at non inverting = 0

Using KCL

$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_2}$$


$$V_o = -V_i \times \frac{R_2}{R_1} \rightarrow 180^\circ \text{ phase change}$$
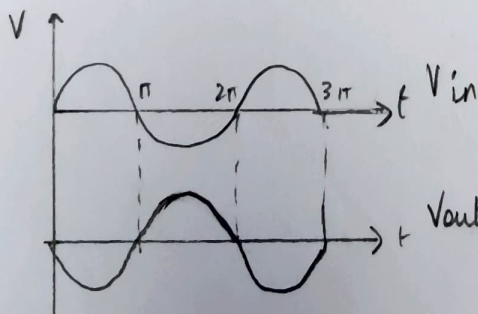
$$A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$



(phase change 180° , $R_2 > R_1$)

(c) Adder Circuit

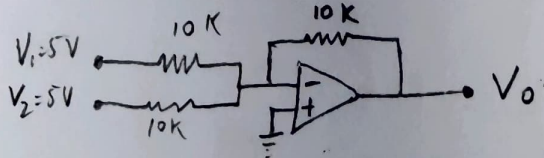



Using superposition theorem
 response by V_1 response by V_2

$$V_{o1} = -\frac{R_3}{R_1} V_1$$


$$V_{o2} = -\frac{R_3}{R_2} V_2$$

$$V_o = V_{o1} + V_{o2} = -R_3 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = -\frac{R_3}{R} (V_1 + V_2) \quad [\text{since } R_1 = R_2 = R]$$

180° phase shift

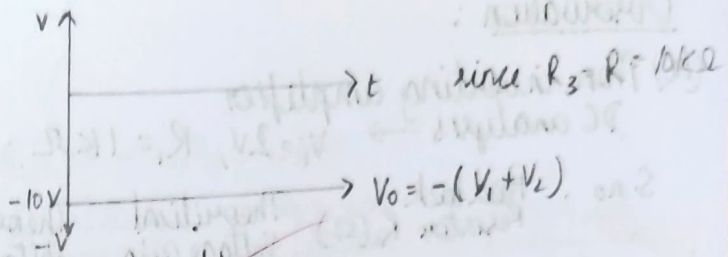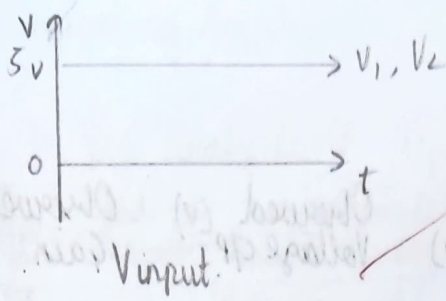

(d) Subtract circuit

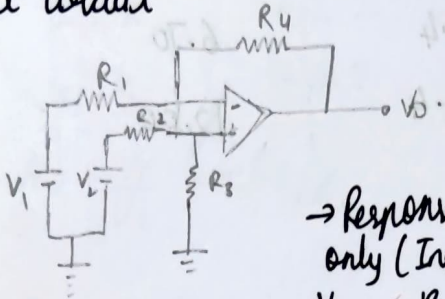

$$R_1 = R_2 = R_3 = R_4 = 10K\Omega$$

Using superposition theorem

→ Response due to V_1 only (Inverting Amplifier)

$$V_{01} = -\frac{R_4}{R_1} V_1 = -V_1$$



→ Response due to V_2 only (Non Inverting Amplifier)

$$V_{02} = V' \left(1 + \frac{R_4}{R_2} \right) = 2V'$$

$$\text{where } V' = \left(\frac{V_2}{R_2 + R_3} \right) R_3 = \frac{V_2}{2}$$

$$V_0 = V_{01} + V_{02} = (V_2 - V_1)$$


(since $R_1 = R_2 = R_3 = R_4$)

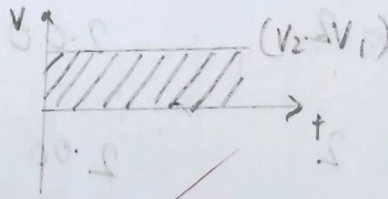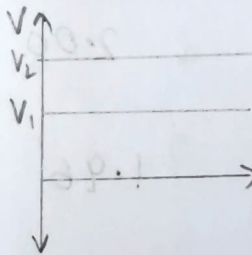

(e) bandwidth = $f_2 - f_1 \Rightarrow f_H - f_L$

$$IP = \frac{10}{10}$$

(f)

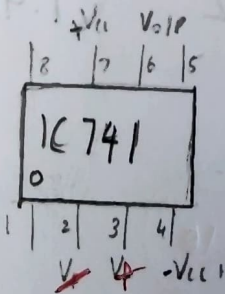

$V_- \rightarrow$ Inverting

$V_p \rightarrow$ Non Inverting

Observation :

(a) Non-inverting amplifier

DC analysis $\rightarrow V_i = 2V, R_i = 1K\Omega$

S.no.	Feedback Resistor $R_2(\Omega)$	Theoretical Voltage gain	Theoretical Voltage OP (V)	Observed Voltage OP (V)	Observed Gain
1	1K	2.0	4.0	4.17	2.085
2	2.2K	3.2	6.4	6.70	3.350
3	4.7K	5.7	11.4	12.00	6.000

$$A_v = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_i}\right)$$

A.C Analysis $\rightarrow R_2 = 1K\Omega, R_i = 1K\Omega, V_i = 1V_{p-p}$

S.no	Frequency (KHz)	Theoretical Voltage gain	Theoretical Voltage OP (V)	Observed Voltage Output (V)	Observed Gain
1	1	2	2.00	2.00	2.00
2	2	2	2.00	1.96	1.96
3	2.5	2	2.00	1.96	1.96
4	2.10	2	2.00	1.92	1.92

EXP-10

Q1) Inverting Amplifier

D-C Analysis $\rightarrow V_i = 2V, R_1 = 1K\Omega, R_2 = 10K\Omega$

S.No	Feedback Resistor $R_2(\Omega)$	Theoretical Voltage Gain (V)	Theoretical Voltage o/p (V)	Observed Voltage o/p (V)	Observed Gain
1	1K	-1	-2	-2.08	-1.04
2	2.2K	-2.2	-4.40	-4.60	-2.3
3	4.7K	-4.7	-9.40	-9.93	-4.96

$$A_v = \frac{V_o}{V_i} = -R_2/R_1$$

AC-Analysis $\rightarrow V_i = 1V, R_2 = 1K\Omega, R_1 = 1K\Omega$

S.No	Frequency (kHz)	Theoretical Voltage Gain	Theoretical Voltage o/p (V)	Observed Voltage o/p (V)	Observed Gain
1	1	-1	-1	-1	-1
2	2	-1	-1	-1	-1
3	5	-1	-1	-0.96	-0.96
4	10	-1	-1	-0.92	-0.92

(c) Adder Circuit

$$V_1 = 4.5V, R_1 = 10K\Omega, R_2 = 10K\Omega, R_f = 10K\Omega$$

S.No	$V_2 (V)$	V_o Theoretical (V)	V_o Experimental (V)
1	0	-4.5	-4.58
2	1	-5.5	-5.71
3	2	-6.5	-6.76
4	3	-7.5	-7.74
5	4	-8.5	-8.77

$$\Rightarrow V_o = -(V_1 + V_2)$$

(d) Subtraction Circuit

$$V_1 = 4.5V$$

$$R_1 = R_2 = R_3 = R_4 = 10K\Omega$$

S.No	$V_2 (V)$	V_o Theoretical (V)	V_o Experimental (V)
1	0	-4.5	-4.69
2	1	-3.5	-3.55
3	-1	-5.5	-5.51
4	2	-2.5	-2.56
5	-2	-6.5	-6.54
6	3	-1.5	-1.49
7	-3	-7.5	-7.6
8	4	-0.5	-0.51
9	-4	-8.5	-8.70

$$\Rightarrow V_o = V_2 - V_1$$

$$Obs = 10$$

Apparatus Used:

Digital storage Oscilloscope, multimeter, function generator, Multiple power supply, connecting wires, Opamp (IC 741), Resistors (1K Ω , 4.7K Ω , 2.2K Ω , 10K Ω)



$V_1 = 10$
 $V_2 = 10$
 $\phi = 0^\circ$
 $A_1 = 10$
 $f = 100$
 $R_1 = 10$



For the Inverting Circuit



$V_1 = 10$
 $V_2 = 10$
 $\phi = 0^\circ$
 $A_1 = 10$
 $f = 100$
 $R_1 = 10$



For the Inverting Circuit

Calculation:

(a) For Non-Inverting circuit.

Observation ①: Voltage gain $A_v = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1}\right)$ (DC Analysis).

Theoretical gain = $1 + \frac{R_2}{R_1}$

$$= 1 + \frac{10}{10}$$
$$= 2$$

$$\Rightarrow \frac{V_o}{V_i} = 2$$

Theoretical $V_o = 4(1) = 4V$
Output

Experimental $V_o = 4.17V$
Output

Experimental $A_v = \frac{V_o}{V_i}$
gain
 $= \frac{4.17}{2}$

$$A_v = 2.085$$

Observation ② →

Theoretical gain = $1 + \frac{R_2}{R_1}$

$$= 1 + \frac{20}{10}$$

$$= 3$$

$$\frac{V_o}{V_i} = 3.2$$

Theoretical $V_o = 3(1) = 3V$
Output

Experimental = $6.70V$
Output

Experimental $A_v = \frac{V_o}{V_i}$
gain

$$\frac{6.70}{2}$$

$$= 3.35$$

AC Analysis

Observation ① →

Theoretical gain = $1 + \frac{R_2}{R_1}$
 $= 1 + \frac{10}{10}$
 $= 2$

$$\Rightarrow V_o/V_i = 2$$

Theoretical = $V_o = 2V_i$
Output

Observed gain = 2.00

Observed Output = 2.00V

for freq = 1KHz

Observation ② →

Theoretical gain = $1 + \frac{R_2}{R_1}$
 $= 1 + \frac{20}{10}$
 $= 3$

$$\Rightarrow V_o/V_i = 3$$

Theoretical = 2.00V
Output

Observed Gain = 2.00

Observed Output = 2.00V

for freq = 2KHz

(b) Inverting Amplifier.

$$\text{Voltage Gain } A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

D.C Analysis

Observation ①:

$$\text{Theoretical gain} = -\frac{R_2}{R_1}$$

$$= -\frac{1}{1}$$

$$V_o/V_i = -1$$

$$\text{Theoretical: } V_o = -2V$$

Output

$$\text{Experimental: } V_o = -2.08$$

Output

$$\text{Experimental Gain} = -1.04$$

A.C Analysis

$$R_1 = R_2 = 1K\Omega$$

Observation ①

$$f_{\text{req}} = 1KHz$$

$$\text{Theoretical Gain} = -R_2/R_1$$
$$= -1$$

$$\text{Theoretical } V_o = -1V_{p-p}$$

Output

$$\text{Observed Gain} = -1$$

$$\text{Observed: } V_o = -1V_{p-p}$$

Output

Observation ②:

$$\text{Theoretical gain} = -\frac{R_2}{R_1}$$

$$= -\frac{2.2}{1}$$

$$V_o/V_i = -2.2$$

$$\text{Theoretical } V_o = -4.40$$

Output

$$\text{Experimental } V_o = -4.60$$

Output

$$\text{Experimental Gain} = -2.3$$

Observation ②

$$f_{\text{req}} = 10KHz$$

$$\text{Theoretical Gain} = -R_2/R_1$$
$$= -1$$

$$\text{Theoretical } V_o = -1V_{p-p}$$

Output

$$\text{Observed Gain } A_v = -0.92$$

$$\text{Observed } V_o = -0.92V_{p-p}$$

Output

Adder Circuit

$$V_o \text{ Theoretical} = -(V_1 + V_2)$$

$$V_1 = 4.5 \text{ V}$$

$$= -(4.5 + 0) = -4.58 \text{ V} \quad 0 \text{ V } 1$$

$$= -(4.5 + 1) = -5.71 \text{ V} \quad 0 \text{ V } 2$$

$$= -(4.5 + 2) = -6.76 \text{ V} \quad 0 \text{ V } 3$$

d) Subtractor Circuit

$$V_o \text{ Theoretical} = V_2 - V_1 \quad (V_1 = 4.5 \text{ V})$$

$$= 1 - 4.5 = -3.55 \quad 0 \text{ V } 1$$

$$= 2 - 4.5 = -2.56 \quad 0 \text{ V } 2$$

$$= 3 - 4.5 = -1.49 \quad 0 \text{ V } 3$$

Brief summary & Result:

- ① In Non-inverting circuit, the observed voltage gain differs from the theoretical gain by a range of $(0.08 - 0.27) \text{ V}$
(0.17 - 0.60)
- ② There is a fall in the observed voltage gain when frequency is increased in AC analysis of both inverting & Non-inverting amplifier circuits. (Reason)
- ③ In Inverting circuit, the observed gain differs from the theoretical gain by a range of $\pm (0.08 - 0.53) \text{ V}$
- ④ Bandwidth achieved in inverting circuit during AC-Analysis is (Not Required)
- ⑤ In both the Adder and the Subtractor circuit, the experimental Output Voltage achieved is very close to the theoretical voltage Output -

Result

(a) Non-Inverting

$$V_o = -\cancel{2.08} 4.17 \text{ V}$$

$$A_v = -2.085$$

for $R_2 = 1 \text{ K}\Omega$

(b) Inverting

$$V_o = -2.08$$

$$A_v = -1.04$$

for $R_2 = 1 \text{ K}\Omega$

(c) Adder

for $V_1 = 4.5 \text{ V}$, $V_2 = 0 \text{ V}$

$$V_o = -4.58 \text{ V}$$

(d) Subtractor

for $V_1 = 4.5 \text{ V}$, $V_2 = 0 \text{ V}$

$$V_o = -4.69 \text{ V}$$

Precaution:

- (1) Connect the Op-Amp pins correctly in the circuit to prevent any damage to it.
- (2) Use small value resistors in feedback network.
- (3) Be ~~care~~ careful and mindful of any short circuit as it might damage components.
- (4) Do not connect DSO or other instruments at the op amp input terminals.

Result: 9