

Experiment -
Feedback Amplifier Circuits

Name - Rohit . R

Roll No . 220121072

Date - 04/07/2023



Experiment-5

Feedback Amplifier Circuit

In : The aim of the experiment is to study the effects of various feedback configurations on amplifier output.

Objective : To construct amplifier circuits with different feedback configuration and study the effect of feedback on mid-band gain, cutoff frequencies and gain bandwidth product.

Formulae :

$$A_v \text{ (Voltage Gain)} = \frac{V_{out}(p-p)}{V_{in}(p-p)}$$

• $A_v \text{ (in dB)} = 20 \log_{10} A_v$

$$\text{Bandwidth} = (f_H - f_L) \text{ Hz}$$

f_H : higher cutoff frequency


f_L : lower cutoff frequency

$$I_E = I_C + I_B$$


$$I_C = I_{\text{majority}} + I_{\text{minority}}$$

$$\alpha_E = 26 \text{ mV (V}_T)$$

Circuit 2 :

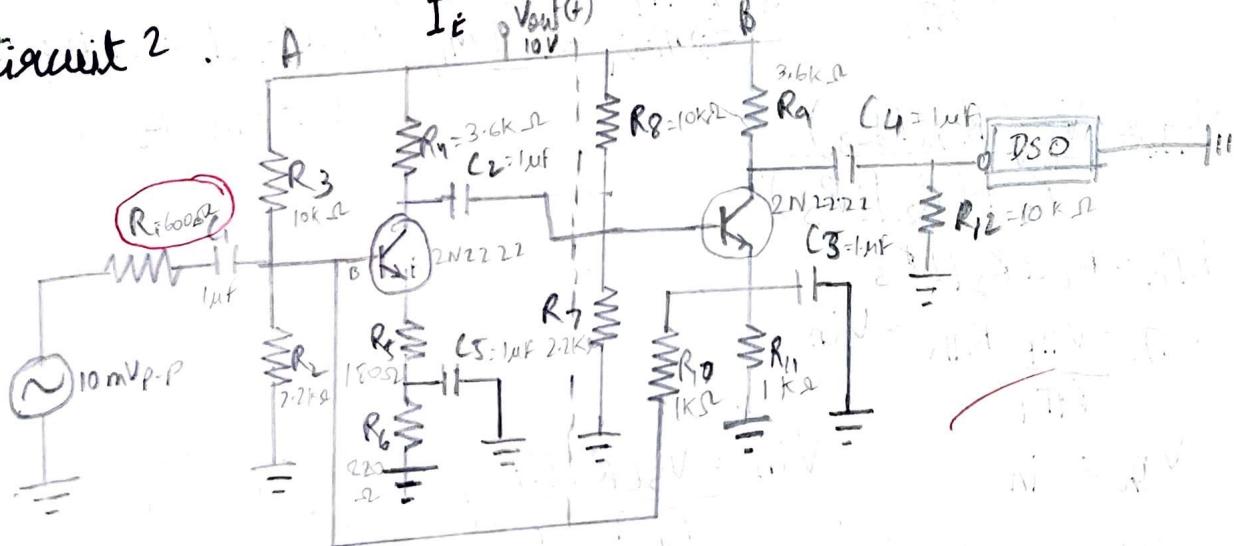

A-C Equivalent Circuit

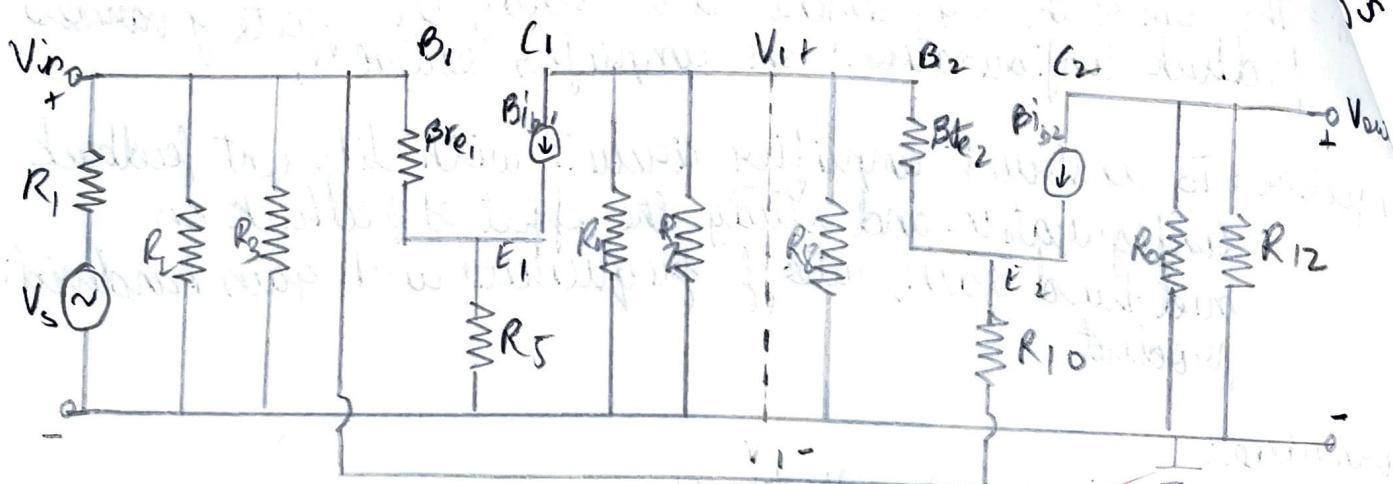

$$A_V = A_{V2} A_{V1} \left(\frac{V_{in}}{V_S} \right) = \frac{V_{out}}{V_1} \left(\frac{V_1}{V_{in}} \right) \frac{V_{in}}{V_S} = \frac{V_{out}}{V_S}$$

$$\textcircled{1} \quad V_{out} = -g_{m2} V_{TII_2} (R_g || R_{12}) \\ V_i = V_{T_I}$$

$$\frac{V_{out}}{V_1} = A_{V2} = -g_{m2} (R_C || R_C)$$

$$\textcircled{2} \quad V_1 = -g_{m1} V_{TII_1} (R_4 || R_7 || R_8 || B_{re}) \quad (B_{re} = r_{TII}) \quad g_{m2} = \frac{I_C}{V_T} = \frac{I_C}{26mV}$$

$$V_{in} = V_{TII_1} + \left(\frac{V_{TII_1}}{r_{TII_1}} + g_{m1} V_{TII_1} \right) R_5$$

$$\frac{V_1}{V_{in}} = A_{V1} = -g_{m1} (R_4 || R_7 || R_8 || B_{re}) \\ 1 + \left(\frac{1}{r_{TII_1}} + g_{m1} \right) R_5$$

Since $i_{B1} = \frac{V_{TII_1}}{r_{TII_1}} \ll g_{m1} V_{TII_1}$ $\Rightarrow A_{V1} = -g_{m1} (R_4 || R_7 || R_8 || B_{re})$

$$\textcircled{3} \quad V_{Th} = \frac{V_S (R_2 || R_3)}{R_1 + (R_2 || R_3)}$$

$$R_{Th} = R_1 || R_2 || R_3$$

$$V_{TII_1} = \frac{V_{TII_1}}{r_{TII_1}} R_{Th} = V_{in}$$

$$V_{Th} = V_{in}$$

$$V_{in} = \frac{V_S (R_2 || R_3)}{R_1 + (R_2 || R_3)}$$

$$\frac{V_{in}}{V_S} = \frac{R_2 || R_3}{R_1 + (R_2 || R_3)}$$

$$\text{IP} = \frac{10}{10}$$

Observation

$$V_{in} = 90 \text{ mV} \quad V_{CC} = 10 \text{ V}$$

Frequency (kHz)	V_o (P-P) (V)	A_v	A_v in decibels
0.5	1.55	17.22	24.72
1	1.84	20.44	26.21
2	1.9	21.11	26.44
5	2.0	22.22	26.84
10	2.3	25.55	28.13
20	2.6	29.88	29.18
30	2.9	32.22	30.16
40	3.3	36.67	31.29
50	3.3	36.67	31.29
60	3.3	36.67	31.29
70	3.3	36.67	31.29
80	3.2	38.55	31.02
90	3.1	39.44	30.73
100	3.0	33.33	30.44
200	2.8	31.11	29.86
300	2.5	27.77	28.85
400	2.3	25.55	28.13
500	2.2	24.44	27.75
600	2.0	22.22	26.84
800	1.8	20.44	26.21
1000	1.6	17.22	24.72
2000	1.4	15.56	23.86

Expt 2

→ Ground R_{12} & connect R_{12} to base of transistor (Q_1) in first circuit.

Observation: V_{in} (P-P) = 1.12V $V_{CC} = 10$ V

Frequency (kHz)	V_o (P-P) (V)	$A_v = \frac{V_o}{V_i}$	A_v (in dB)
0.5	8.20	7.32	17.29
0.75	8.0	7.15	17.07
1	8.0	7.15	17.07
2	7.8	6.97	16.85
2.5	7.6	6.8	16.65
4	7.6	6.8	16.65

Calculation:

$$A_{v\max} = \frac{V_o(\max)}{V_i} = 2 \frac{3-30}{90mV} V = 36.66$$

$$A_{v\max} (\text{dB}) = 20 \log_{10}(36.66) = 31.29$$

$$A_0 = \frac{A_{v\max}}{\sqrt{2}} = 25.92$$

$$V_{out}(\text{at } A_0) = A_0 \times V_{in} = 23.33$$

- 3dB gain f_L & f_H are at $A_{v\max} - 3\text{dB}$

$$f_L = 5 \text{ kHz} \quad f_H = 500 \text{ kHz}$$

$$\text{Bandwidth} = f_H - f_L = 495 \text{ kHz}$$

$$\text{Midband frequency} = \frac{f_H + f_L}{2} = 247.5 \text{ kHz}$$

$$\text{Midband gain} = \frac{V_o(\text{at } f=247.5)}{V_i} = 29.4$$

Result

$$\text{Bandwidth} = 495 \text{ kHz}$$

$$\text{Midband freq. } 247.5 \text{ kHz}$$

$$\text{Midband gain} = 29.4$$

$$A_{v\max} = 36.66$$

$$A_{v\max} (\text{dB}) = 31.29$$

$$A_0 = 25.92$$

$$V_{out}(\max) = 3.3 \text{ V}$$

Marked & AV

V_{in} OP:

(V)(+/-) oV (M) pure pert

2-0

1

2

3

4

5

6

7

8

9

0

1

2

3

4

5

6

7

8

9

0

1

2

3

4

5

6

7

8

9

0

Result

Av(in dB) V/s Frequency Graph

Av(in dB)

24.

25.

26.

27.

28.

29.

30.

31.

32.

33.

34.

35.

36.

Frequency (kHz)

10 kHz


100 kHz

1000 kHz

KUDIP

Y-axis
Av in dB
Unit: 2dB

Scale
x-axis =
frequency(kHz)

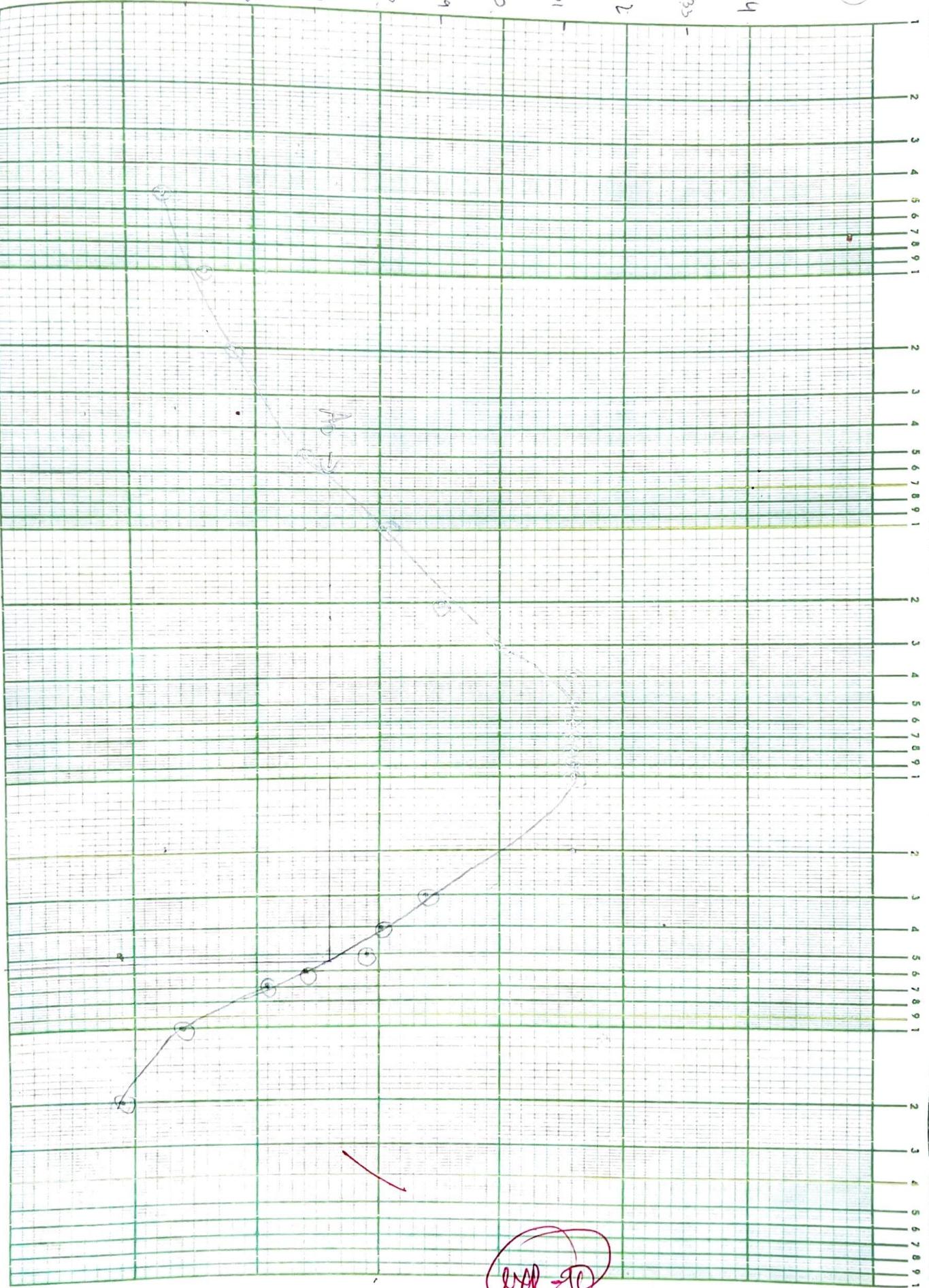

Discussions & Precautions

- Upon finishing Part A of the circuit we observed successful amplification, hence we went ahead and built the Part B of the circuit as well
- Amplification was observed and noted, upon increasing frequency, the voltage began to remain almost constant between 20 kHz to 300 kHz. From 300 kHz to 20 kHz it was increasing and it was decreasing beyond 300 kHz.
- Since we plotted the graph in dB for A_v , we have to perform " $-3dB$ " from A_{vmax} in order to get full width half max of the graph. From this we got f_H & f_L to get Bandwidth.
- In the modified circuit we gave input at high frequency and noted that the output was amplified and on increasing frequency the V_{out} decreased

Precaution

?

- Avoid shorting ~~across~~ the circuit by checking ground of power supply
- All connections should be tight
- V_{in} should be less than 150 mV to avoid clipping.

①