

PH-211

Electronics Lab.

Experiment 7: Multivibrators.

Name - Rohit Ramabhadran

Roll no. 220121072

Experiment Name: Multivibrators

Experiment No.: 7

Date - 25/09/2023

49  
50

## Experiment - 07: Multivibrators

Aim: To construct a (a) a stable and a (b) monostable multivibrator using IC 555.

Apparatus: 1) IC 555 (5) Digital CRO  
2) Bread board (6) Pulse generator for monostable  
3) Resistors & Capacitors (7) Multipower supply.  
4) Connecting Wires

### Astable:

(a) Resistors ( $1K\Omega$ ,  $3.3K\Omega$ ,  $10K\Omega$ ,  $18K\Omega$ )

(b) Capacitors ( $0.001\mu F$ ,  $0.01\mu F$ ,  $0.1\mu F$ ,  $1\mu F$ )

### Monostable:

(a) Resistors ( $900K\Omega$ )

(b) Capacitors ( $0.01\mu F$ ,  $1\mu F$ )

### Formulae's

#### 1) Astable Multivibrator

$$\Rightarrow t_{\text{high}} = 0.693(R_1 + R_2)C \quad \Rightarrow t_{\text{low}} = 0.693R_2C$$

where,

$R_1, R_2$  = Resistance

$C$  = Capacitance

$t_{\text{high}}$  = Charging phase of capacitor / Logic high phase

$t_{\text{low}}$  = Discharging phase of capacitor / Logic low phase.

$$T_{\text{Total}} = t_{\text{high}} + t_{\text{low}} = 0.693(R_1 + R_2)C + 0.693R_2C = 0.693(R_1 + 2R_2)C$$

$$f_{\text{osc}} = \frac{1}{T_{\text{Total}}} = \frac{1.44}{R_1 + 2R_2} \times \frac{1}{C} \quad f = \text{frequency of oscillator}$$

$$\text{Duty Cycle \%} = \frac{t_{\text{high}}}{T} \times 100 = \frac{R_1 + R_2}{R_1 + 2R_2} \times 100$$



$$-V_C(t) = V_F + (V_I - V_F)e^{-t/R'C}$$

$$V_I = \frac{V_{CC}}{3}$$

$V_F = V_{CC}$  (final voltage)

$V_{CC}$  (bias voltage)

$V_C$  (charging voltage)

$$-V_C'(t) = V_F + (V_I - V_F)e^{-t/R_2C}$$

$V_I = \frac{2V_{CC}}{3}$  (initial voltage)

$V_F = 0$  (final voltage)

$V_C'(t) \Rightarrow$  (Discharging voltage)

b) Monostable Multivibrator

$$T = 1.1 RC$$

$$\text{Duty Cycle} = T_{OFF} / (T_{OFF} + T_{ON})$$

$T \Rightarrow$  Time period of pulse

$T_{OFF} \Rightarrow$  time in astable state


$T_{ON} \Rightarrow$  time in stable state

Pulse width,

$$W = 1.1 RC$$

• Equivalent Circuits

a) Astable Multivibrator

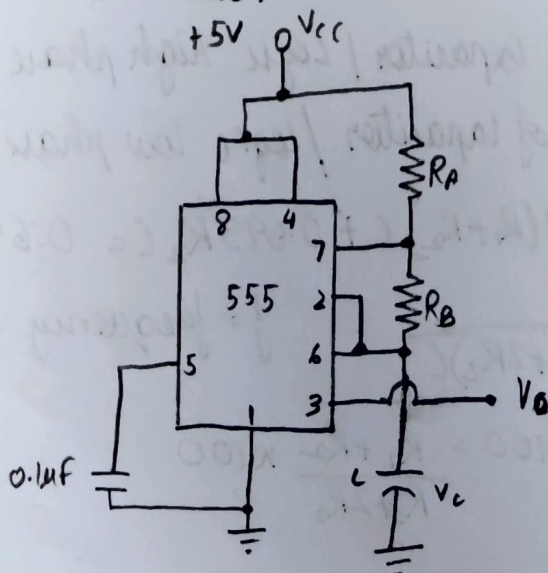

$$R_A = 1 k\Omega$$

$$R_B = 3.3 k\Omega$$

$$10 k\Omega$$


$$18 k\Omega$$

$$C = 1 \mu F$$

$$0.1 \mu F$$

$$0.01 \mu F$$



## b) Monostable Multivibrator

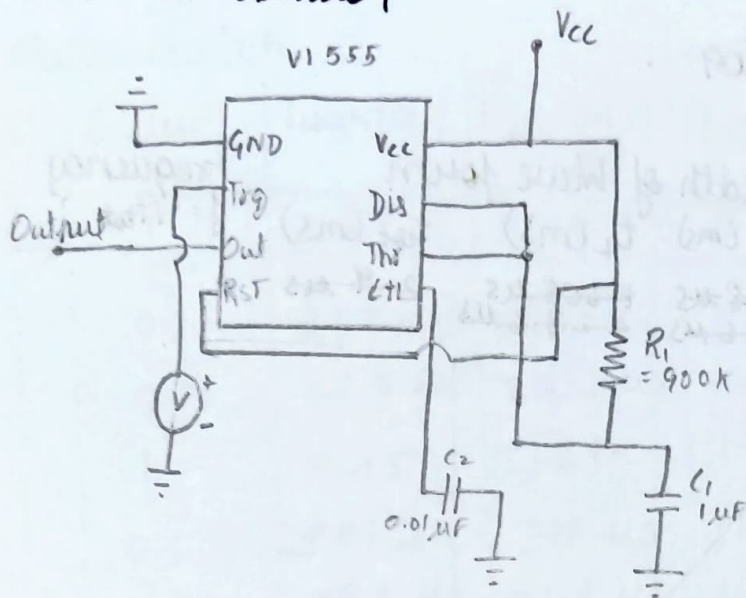

- Expected Waveform as a function of input

a) Astable Multivibrator

(b) Monostable Multivibrator

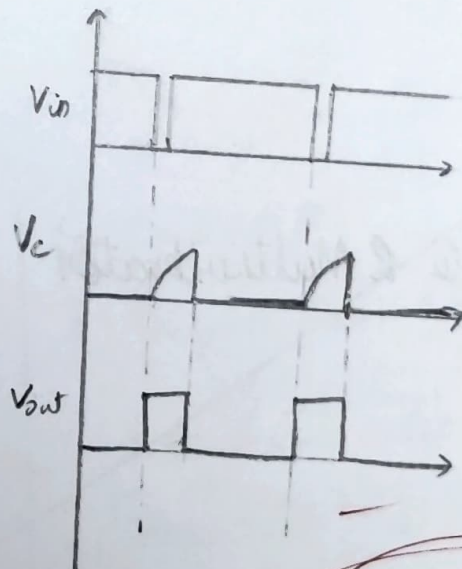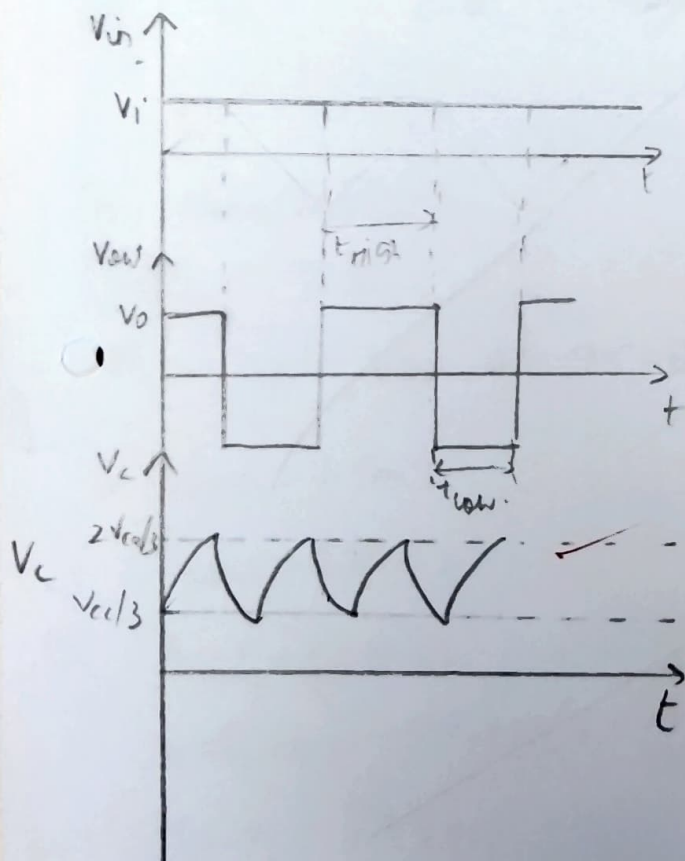

$$IP = \frac{10}{10}$$



# Observation

## (a) Astable Multivibrator

Sr No	$R_B$ (k $\Omega$ )	$C$ ( $\mu$ F)	$T_{high}$ (ms)	$T_{low}$ (ms)	$T_{tot}$ (ms)	$f_{osc}$ (exp) $f = 1/T_{tot}$	$f_{osc}$ (theo)
1	3.3	1	2.87	2.24	5.11	195.69 Hz	189.47 Hz
2	3.3	0.1	287 $\mu$ s	224 $\mu$ s	511 $\mu$ s	1.95 kHz	1.89 kHz
3	3.3	0.01	28.5 $\mu$ s	22.7 $\mu$ s	51.2 $\mu$ s	19.57 kHz	18.95 kHz
4	10	1	9.05	2.21	11.26	88.81 Hz	68.57 Hz
5	10	0.1	897 $\mu$ s	218 $\mu$ s	1115 $\mu$ s	896.9 Hz	685.7 Hz
6	10	0.01	88.2 $\mu$ s	21.9 $\mu$ s	110.1 $\mu$ s	9.08 kHz	6.85 kHz
7	18	1	14.6 $\mu$ s	2.2	16.8	59.5 Hz	38.9 Hz
8	18	0.1	1.44 ms	219 $\mu$ s	1.65	606 Hz	389.1 Hz
9	18	0.01	142 $\mu$ s	22 $\mu$ s	164 $\mu$ s	6.09 kHz	3891 Hz

## (b) Monostable

For  $R = 1k\Omega$

Duty cycle was at 75.8%

$$t_{high} = 1.5ms$$

$$t_{low} = 500\mu s$$

For  $R = 560\Omega$

$$\text{Duty cycle} = 59.17\%$$

$$t_{high} = 593\mu s$$

$$t_{low} = 409.5\mu s$$

For  $R = 560\Omega$

$$T = t_{high} + t_{low} = 593.4 + 409.5 = 1002.9\mu s$$

$$1.1 RC = 1.1 \times 560 \times 1\mu F$$

$$T_{theoretical} = 616\mu s$$

$$\text{Duty cycle} = \frac{t_{high}}{T} = \frac{593.4\mu s}{1002.9\mu s} = 59.17\%$$

$$\text{Duty cycle (obs)} = 59.17\%$$

## Result

(K) As you increase the ~~value~~ -

## Calculation

(Q) Astable Multivibrator.

$$\text{Duty cycle \%} = \frac{R_A + R_B}{(R_A + 2R_B)} \times 100\%$$

(a) For  $R = 3.3 \text{ k}\Omega$

$$\text{Duty cycle} \Rightarrow \frac{1 + 3.3}{1 + 6.6} \times 100 = 56.57\%$$

(b) For  $R_B = 10 \text{ k}\Omega$

$$\text{Duty Cycle} = \left( \frac{1 + 10}{1 + 20} \right) \times 100 = 52.30\%$$

(c) For  $R_B = 18 \text{ k}\Omega$

$$\text{Duty cycle} = \frac{1 + 18}{1 + 36} \times 100 = 51.35\%$$

(b) Monostable multivibrator:

For  $R = 560 \Omega$

$$T = t_{\text{high}} + t_{\text{low}} = 593.4 + 409.5 \\ = 1002.9 \mu\text{s}$$

$$W = 1.1RC = 1.1 \times 560 \times 1 \mu\text{F}$$



$$T_{\text{theo}} = 6.16 \mu\text{s}$$

$$\text{Duty cycle} = \frac{t_{\text{high}}}{T} = \frac{593.4 \mu\text{s}}{1002.9 \mu\text{s}} \\ = 59.17\%$$


$$\text{Duty cycle (observed)} = 59.27\%$$



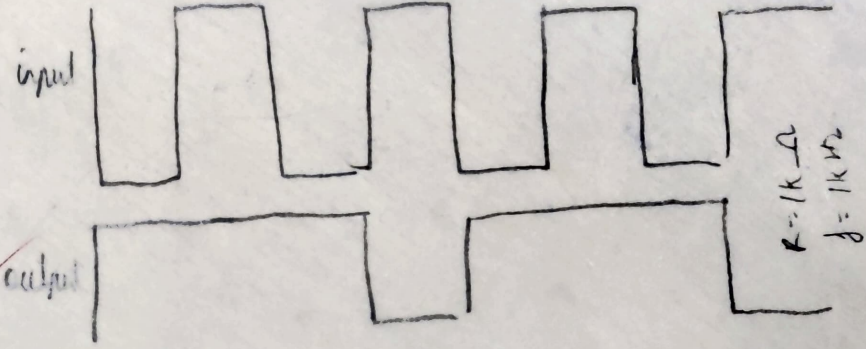
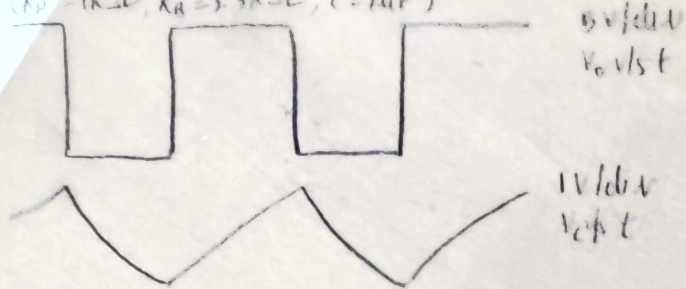
①  $R_A = 1k\Omega$ ,  $R_B = 3.3k\Omega$ ,  $C = 1\mu F$



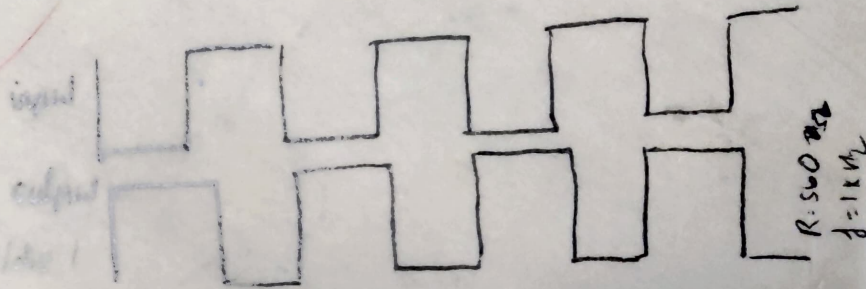②  $R_A = 1k\Omega$ ,  $R_B = 10k\Omega$ ,  $C = 1\mu F$



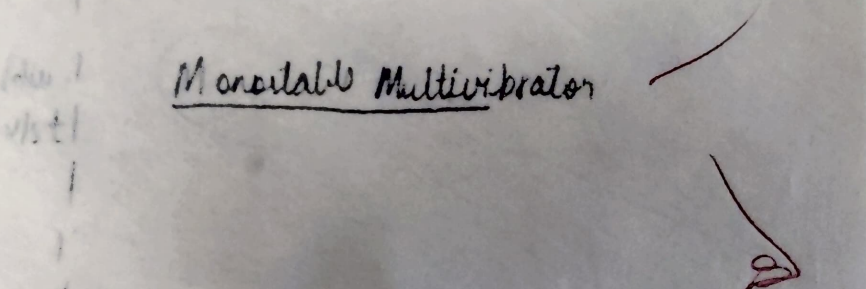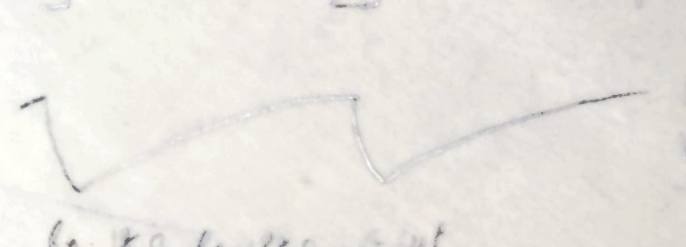③  $R_A = 1k\Omega$ ,  $R_B = 10k\Omega$ ,  $C = 1\mu F$



Monostable Multivibrator

$R_A = 1k\Omega$ ,  $R_B = 10k\Omega$ ,  $C = 1\mu F$

Monostable Multivibrator

## Result

- The  $T_{\text{high}} \approx T_{\text{low}}$  for the output signal in a stable multivibrator when  $R_B \gg R_A$  for Astable Multivibrator.
- The Duty cycle ~~is~~ seen for Monostable Multivibrator is 59.27%.

## Discussion and precaution and Result

(a) Astable multivibrators worked as expected.

(b) As we increase the biasing voltage  $V_{CC}$  for astable multivibrators the frequency increases & pulse width decreases.

(c)  $T_{\text{high}} \approx T_{\text{low}}$  for output signal in astable multivibrator when  $R_B \gg R_A$ .

(d) Operate using a  $V_{CC}$  that gives you output frequency as close to theoretical value.

(e) Connections must be tight.

(f) Don't pass high currents.

(g) Make sure the circuit is not shorted.

(h) 75% Duty Cycle was observed for  $R = 1K\Omega$  and 59.17% for  $560\Omega$  in monostable circuit.

(i) With decreasing capacitance,  $t_{\text{high}}$  &  $t_{\text{low}}$  increased.

(j) ~~Duty~~ Duty cycle for astable circuit for  $R_B = 3.3K\Omega$  was found as 56.52%.