

1. For the circuit shown, find the voltage gain, input impedance and output impedance (include the source resistance  $R_s$  within the input impedance of the transistor)




Feedback- method:

$$V_E = V_o \quad V_B = V_s - I_s R_s$$

$$V_B - V_E = V_B - I_s R_s - V_o$$

$$\boxed{\beta = 1}$$

$\Rightarrow$  feedback - circuit

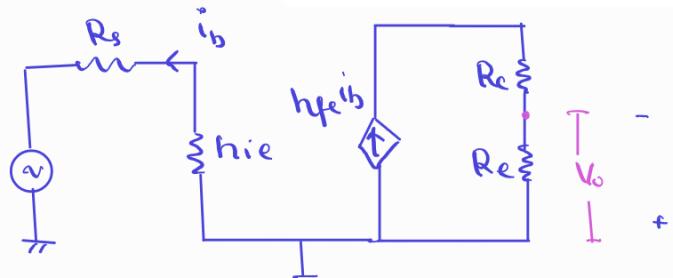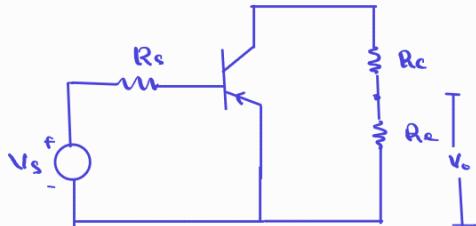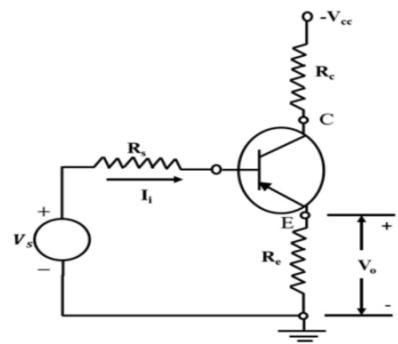

$$A_{vf} = \frac{A_v}{1 + \beta A_v}$$

$$= \frac{h_{fe} R_e}{R_s + h_{ie}} \\ + \beta \frac{h_{fe} R_e}{R_s + h_{ie}}$$

$$= \frac{h_{fe} R_e}{R_s + h_{ie} + \beta h_{fe} R_e}$$

$$V_o = -h_{fe} i_b R_e \\ = +h_{fe} \frac{V_s}{R_s + h_{ie}} R_e$$

$$A_v = \frac{V_o}{V_s} = +\frac{h_{fe} R_e}{R_s + h_{ie}}$$

$$D = 1 + \beta A_v = 1 + A_v \\ = \frac{R_s + h_{ie} + h_{fe} R_e}{R_s h_{ie}}$$

$$Z_{in} = R_s + h_{ie}$$


$$Z_{if} = (R_s + h_{ie}) D$$

$$Z'_o = R_L$$

$$R'_{of} = \frac{R_e (R_s + h_{ie})}{R_s + h_{ie} + h_{fe} R_e}$$

$$R_{of} = \frac{R_s + h_{ie}}{h_{fe}}$$

Without feedback.

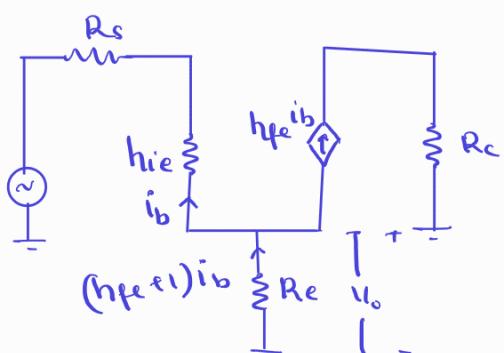

$$R_o = R_e || (R_s + h_{ie})$$

$$V_s + (h_{ie} + R_s) i_b + R_e (h_{fe} + 1) i_b = 0$$

$$i_b = \frac{-V_s}{h_{ie} + R_s + R_e (h_{fe} + 1)}$$

$$Z_{in} = h_{ie} + R_s + R_e (h_{fe} + 1)$$

$$V_o = -(h_{fe} + 1) i_b R_e$$



$$\frac{V_o}{V_s} = \frac{(h_{fe} + 1) R_e}{h_{ie} + R_s + R_e (h_{fe} + 1)}$$

2. For the circuit shown, find the ac voltage  $V_i$  as a function of  $V_s$  and  $V_f$ . Assume that the inverting-amplifier input resistance is infinite, that  $A = Av = -1,000$ ,  $\beta = V_f/V_s = \frac{1}{100}$ ,  $R_S = R_C = R_e = 1K$ ,  $h_{ie} = 1K$ ,  $h_{re} = h_{oe} = 0$ , and  $h_{fe} = 100$ . (b) Find  $A_{vf} = V_o/V_s = Av_i/V_s$ .

$$V_i = V_i(V_s, V_f)$$

$$R_i(\text{inv}) = \infty$$
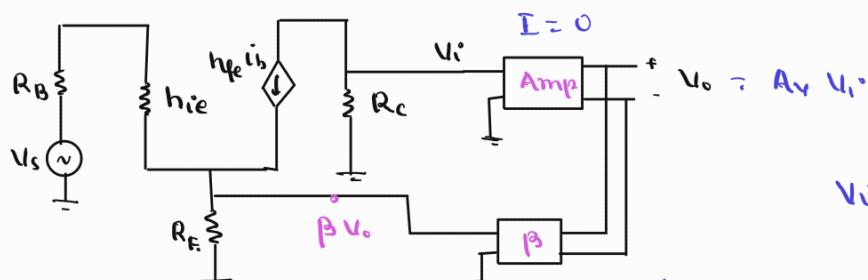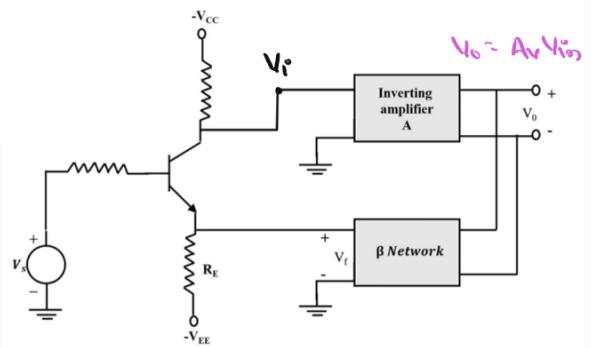
$$Av = -1000 \quad \beta = \frac{1}{100}$$



$$V_i \left( 1 - \frac{h_{fe} R_C \beta Av}{R_B + h_{ie}} \right) = -\frac{h_{fe} R_C}{R_B + h_{ie}} V_s \quad \left| \begin{array}{l} V_i = -\frac{h_{fe} R_C (V_s - \beta V_o)}{R_B + h_{ie}} \end{array} \right.$$

$$V_i = -\frac{h_{fe} R_C V_s}{1 - \frac{h_{fe} R_C \beta Av}{R_B + h_{ie}}}$$

$$\frac{V_o}{A} = -\frac{h_{fe} R_C}{R_B + h_{ie}} (V_s - \beta V_o)$$


$$V_o \left( \frac{1}{A} - \frac{h_{fe} R_C}{R_B + h_{ie}} \beta \right) = -\frac{h_{fe} R_C}{R_B + h_{ie}} V_s$$

$$Av = \frac{V_o}{V_s} = -\frac{h_{fe} R_C}{R_B + h_{ie}} \cdot \frac{1}{\frac{1}{A} - \frac{h_{fe} R_C}{R_B + h_{ie}} \beta}$$



Method-2

$$V_s - i_B R_B - V_{BE} - \beta V_o = 0$$
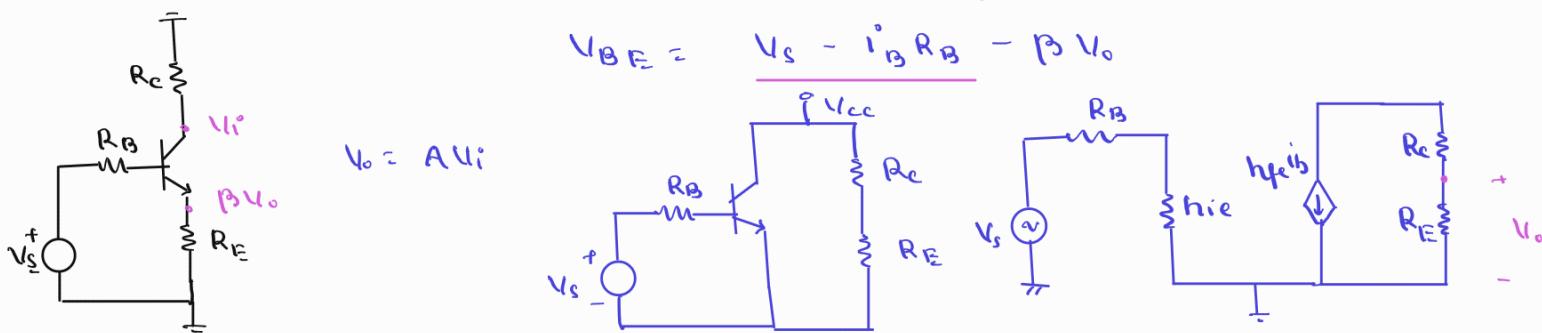
$$V_{BE} = \frac{V_s - i_B R_B - \beta V_o}{R_E}$$




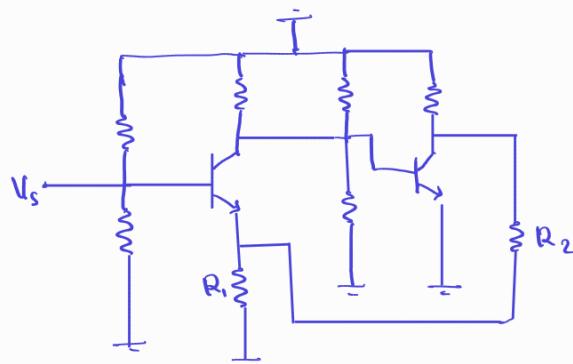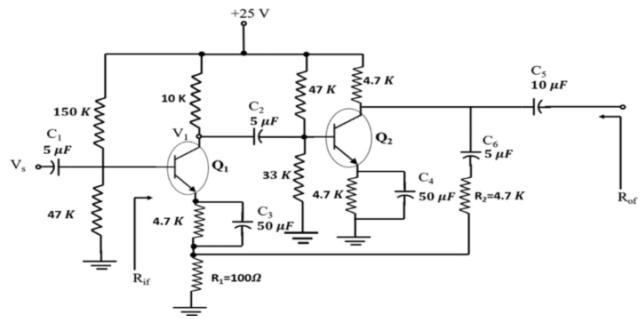3. For the circuit shown below find the voltage gain, input impedance and output impedance (to find feedback factor  $\beta$ , assume current gain of the second amplifier is very large, so that current through 4.7k resistance in the emitter of Q1 is negligible as compared to current through feedback network resistance 4.7 k which is connected 5 microfarad capacitor in series) (Assume  $R_s=0$ ,  $h_{ie} = 1.1k$ ,  $h_{re} = h_{oe} = 0$ )



$$R' = R_1' \parallel R_2''$$

$$R'' = R_2'' \parallel R_1''$$

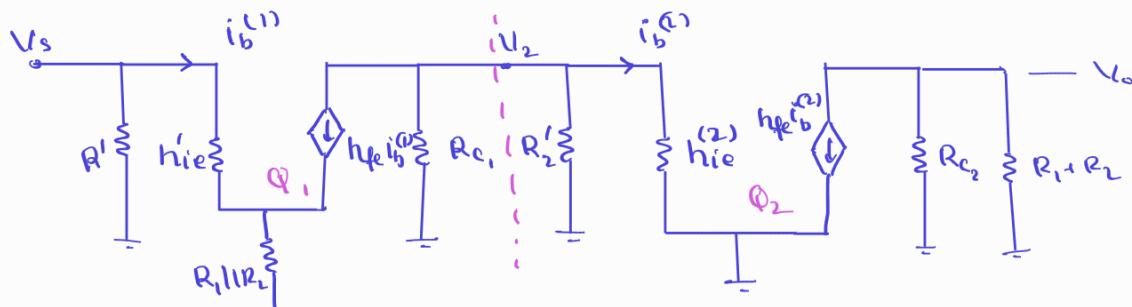

$$Av_1(Q_1) = \frac{V_2}{V_s} = -\frac{h_{fe} i_b^{(1)} R_{C1}}{V_s}$$

$$\left| \frac{V_o}{R_1 + R_2} + \frac{V_o}{R_{C2}} + h_{fe} i_b^{(2)} = 0 \right.$$

$$= -\frac{h_{fe} V_s R_{C1}}{h_{ie} + (R_1 \parallel R_2)(h_{fe} + 1)} \cdot \frac{1}{V_s} = -\frac{h_{fe} R_{C1}}{h_{ie} + (R_1 \parallel R_2)(1 + h_{fe})}$$

$$Av_2(Q_2) = -\frac{h_{fe} i_b^{(2)} R_L^{(2)}}{V_2}$$

$$R_L^{(2)} = R_{C2} \parallel (R_1 + R_2)$$

$$= -\frac{h_{fe} R_L^{(2)}}{h_{ie}^{(2)}}$$

$$Av = Av_1 Av_2 = \frac{h_{fe} R_{C1}}{h_{ie}^{(1)} + (R_1 \parallel R_2)(h_{fe} + 1)} \times \frac{h_{fe} R_L^{(2)}}{h_{ie}^{(2)}}$$

$$Av_f = \frac{Av}{1 + \beta Av}$$

$$Z_{in} = \frac{V_s}{i_b} = h_{ie} + (R_1 \parallel R_2)(h_{fe} + 1)$$

$$Z_{if} = Z_{in}(1 + \beta Av)$$

$$Z_o = (R_1 + R_2) \parallel R_{C2}$$

$$Z_{of} = \frac{Z_o}{1 + \beta Av}$$


4. For a general amplifier circuit, find out the current gain, input impedance and output impedance when input is a current source and feedback is a current feedback (i.e current shunt feedback circuit).

$$I_f = \frac{V_i^{(1)} - V_{e_2}}{R_f} \approx -\frac{V_{e_2}}{R_f}$$

$V_i^{(1)} \ll V_{e_2}$

for  $Q_2 : I_c \approx I_E$

$$V_{e_2} = (I_f - I_o) R_E$$

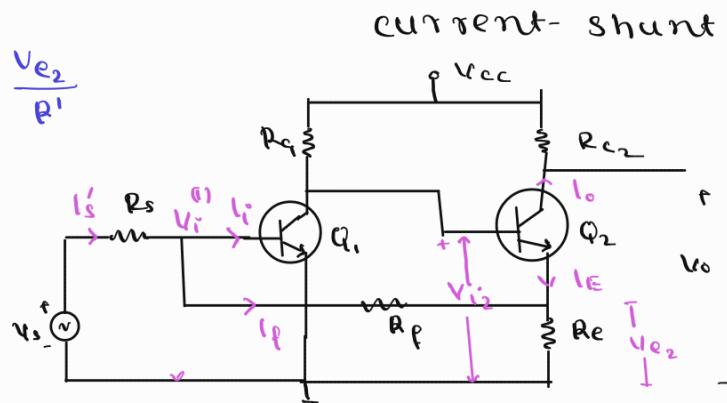


$$I_f = (I_o - I_f) \frac{R_E}{R_f}$$

$$\Rightarrow \left(1 + \frac{R_E}{R_f}\right) I_f = I_o \frac{R_E}{R_f}$$

$$\Rightarrow I_f = \frac{R_E}{R_E + R_f} I_o$$


$$\beta = \frac{R_E}{R_E + R_f}$$

circuit without feedback

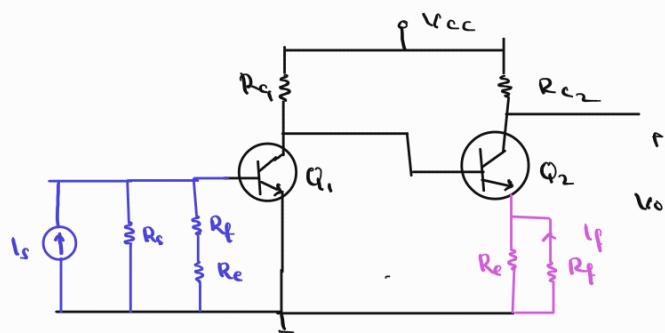

$$Z_{in} = R_s \parallel (R_f + R_E) \parallel h_{ie}$$
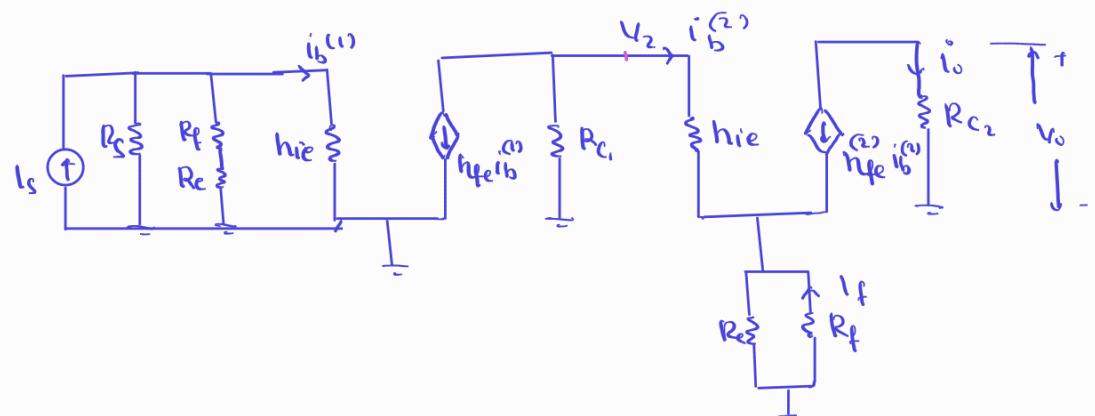
$$Z_{if} = \frac{R_s \parallel (R_f + R_E) \parallel h_{ie}}{1 + A_i \beta}$$



$$A_i = \frac{I_o}{I_s} = \frac{I_o}{I_b^{(2)}} \cdot \frac{I_b^{(2)}}{I_b^{(1)}} \cdot \frac{I_b^{(1)}}{I_s}$$

$$A_i = \frac{i_o}{i_s} = - \frac{h_{fe}^{(2)}}{\frac{i_b^{(2)} i_s}{R_{C_1}} + h_{ie}^{(2)} + (R_e + R_f) (h_{fe}^{(2)} + 1)} \cdot \frac{i_s (R_s || R_f + R_e)}{h_{ie}^{(1)} + (R_s || (R_f + R_e))}$$

$$= - h_{fe}^{(2)} \cdot \frac{- h_{fe}^{(1)} R_{e_1}}{R_{e_1} + h_{ie}^{(2)} + (R_e + R_f) (h_{fe}^{(2)} + 1)} \cdot \frac{R_s || (R_f + R_e)}{h_{ie}^{(1)} + (R_s || (R_f + R_e))}$$

$$A_{if} = \frac{A_i}{1 + \beta A_i}$$

$$A_{vf} = \frac{V_o}{V_s} = \frac{i_o R_{C_2}}{i_s R_s} = A_{if} \frac{R_{C_2}}{R_s}$$

$$R_{ef} = R_{C_2} (1 + \beta A_i)$$

5. In the two-stage feedback amplifier shown, the transistors are identical and have the following parameters:  $h_{fe} = 50$ ,  $h_{ie} = 2 K$ ,  $h_{re} = 0$ , and  $h_{oe} = 0$  calculate

$$(a) A_{If} = \frac{I_o}{I_s}, (b) R_{if} = \frac{V_i}{I_s}, (c) A'_{if} = \frac{I_o}{I'_i}, (d) A_{vf} = \frac{V_o}{V_s}$$

$$I_f = \frac{V_{ib} - V_{E_2}}{R_f}$$

$$V_{ib} \ll V_{E_2}$$

$$I_f = -\frac{V_{E_2}}{R_f}$$


$$V_{E_2} = -I_e R_{E_2}$$

$$= -(I_o - I_f) R_{E_2}$$


$$I_f = \frac{(I_o - I_f) R_{E_2}}{R_f}$$

$$\frac{R_f + R_{E_2}}{R_f} I_f = I_o \frac{R_{E_2}}{R_f}$$
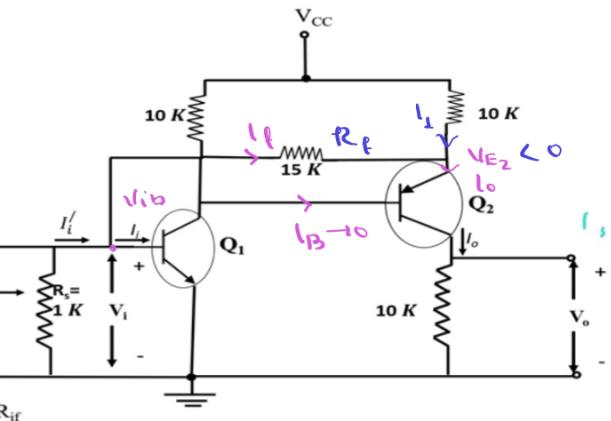
$$\Rightarrow I_f = I_o \frac{R_{E_2}}{R_f + R_{E_2}}$$


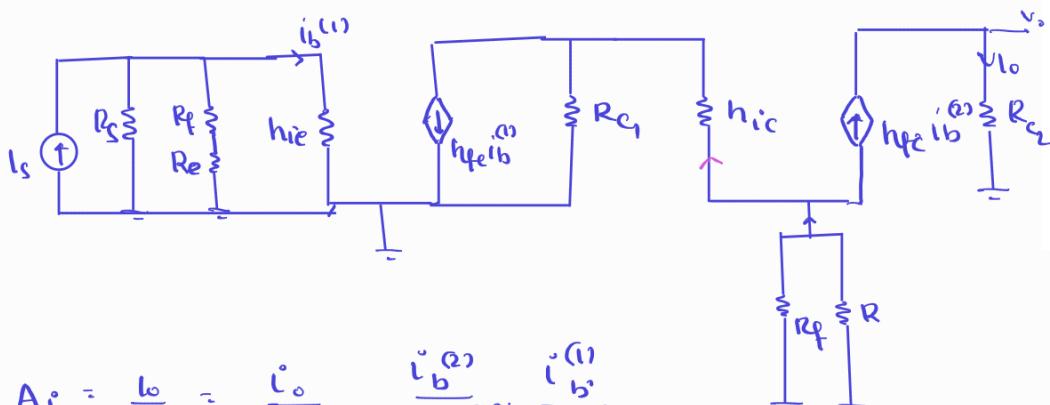
$$\beta = \frac{R_{E_2}}{R_f + R_{E_2}}$$



$$A_i = \frac{I_o}{I_s} = \frac{I_o^{(2)}}{I_b^{(2)}} = \frac{I_b^{(2)}}{I_b^{(1)}} \cdot \frac{I_b^{(1)}}{I_s}$$


$$= \frac{h_{fc}}{I_b^{(1)}} \frac{h_{fe} I_b^{(1)} R_{c1}}{R_{e1} + Z_{in}^{(2)}}$$

$$Z_{in}^{(2)} = h_{ic} + (h_{fc} + 1)(R_f \parallel R)$$

$$\frac{I_s (R_s \parallel (R_f + R_e))}{(R_s \parallel (R_f + R_e)) + h_{ie}} \cdot \frac{1}{I_o}$$

$$A_f = h_{fc} \frac{h_{fe} R_{c1}}{R_{e1} + Z_{in}^{(2)}} \frac{R_s \parallel (R_f + R_e)}{(R_s \parallel R_f + R_e) + h_{ie}}$$

$$A_{If} = \frac{A_i}{I_f \beta A_i}$$

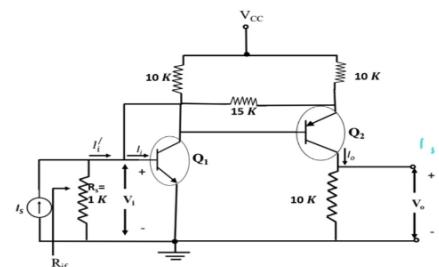

$$Z_{in} = R_s \parallel (R_f + R_e) \parallel h_{ie}$$

$$Z_{if} = \frac{Z_{in}}{1 + A_{if} \beta}$$


$$A_{if}' = h_{fe} \frac{h_{fe} R_e}{R_e + Z_{in}} e_1$$

$$A_{vf} = \frac{V_o}{V_s} = \frac{I_o R_o}{I_s R_s} = A_{if}' \frac{R_o}{R_s}$$

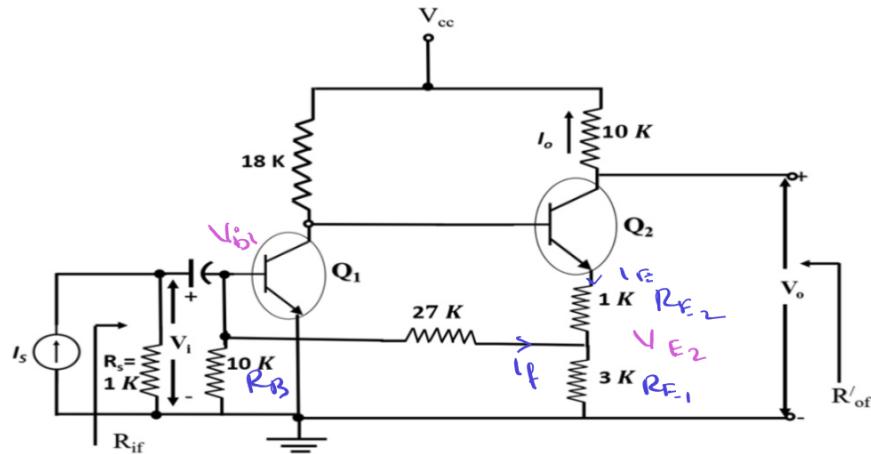6. For the circuit shown (and with the h parameter values given in Prob. 4) find

$$(a) A_{if} = \frac{I_o}{I_s}, (b) R_{if}, (c) A_{vf} \equiv \frac{V_o}{V_s} \text{ where } I_s \equiv \frac{V_s}{R_s}, (d) A'_{vf} \equiv \frac{V_o}{V_i}, (e) R'_{of}$$

Assume: To find the value of feedback factor  $\beta$ , assume that  $V_i \ll V_{e2}$  (voltage at the emitter of Q2) and  $I_{e2} \approx I_{c2}$



$$I_f = \frac{V_{B1} - V_{E2}}{R_f}$$



$$I_f = -\frac{V_{E2}}{R_f}$$

$$= -\frac{(I_f - I_o) R_{E1}}{R_f}$$

$$\frac{R_f + R_{E1}}{R_f} I_f = \frac{I_o}{R_f} \frac{R_{E1}}{R_f}$$

$$\Rightarrow I_f = I_o \frac{R_{E1}}{R_f + R_{E1}}$$

$$\beta = \frac{R_{E1}}{R_f + R_{E2}}$$

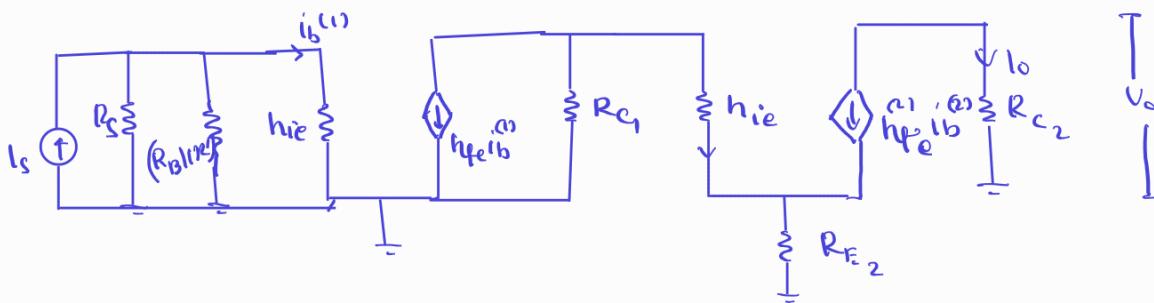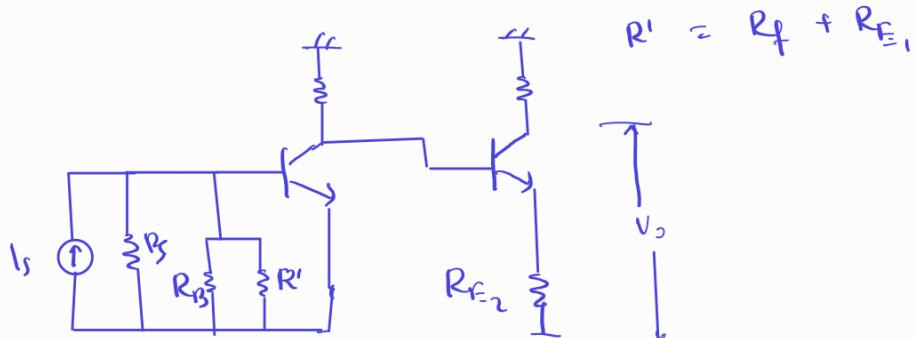

$$A_E = + h_{fe} \cdot \frac{(h_{fe} R_{C_1})}{R_{E_1} + h_{ie} + (h_{fe}+1) R_{E_2}} \quad \frac{(R_s || R_B || R_l)}{(R_s || R_B || R_l) + h_{ie}}$$

$$A_{EF} = \frac{A_E}{1 + \beta A_I}$$

$$R_{if} = \frac{(R_s || h_{ie} || R_B || R_l)}{1 + \beta A_I}$$

$$A_{uf} = A_E \frac{R_o}{R_s}$$

$$R'_{of} = R_{C_2} (1 + \beta A_I)$$