
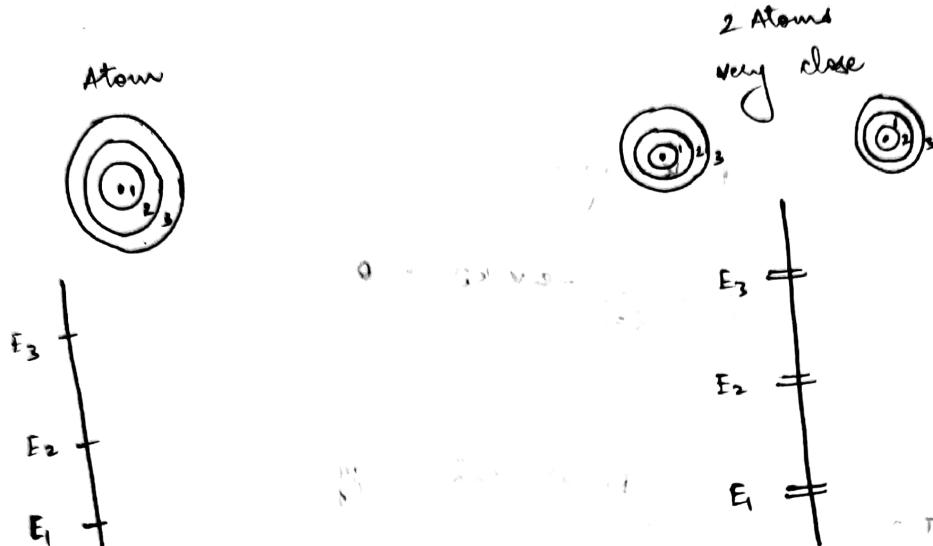



Analog Electronics

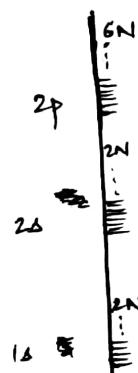


No. of atoms = N



No. of atoms = N
(considering spin)

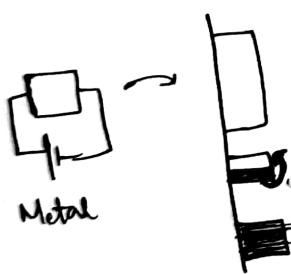


In metal,
there is no
band gap.

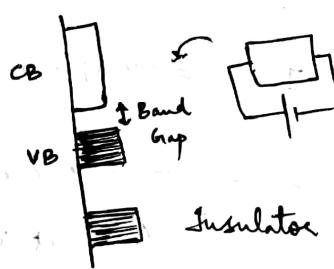


A completely filled band
is an inert band.

Band Gap is the gap
b/w topmost completely
filled band &
bottom of completely
unoccupied band.
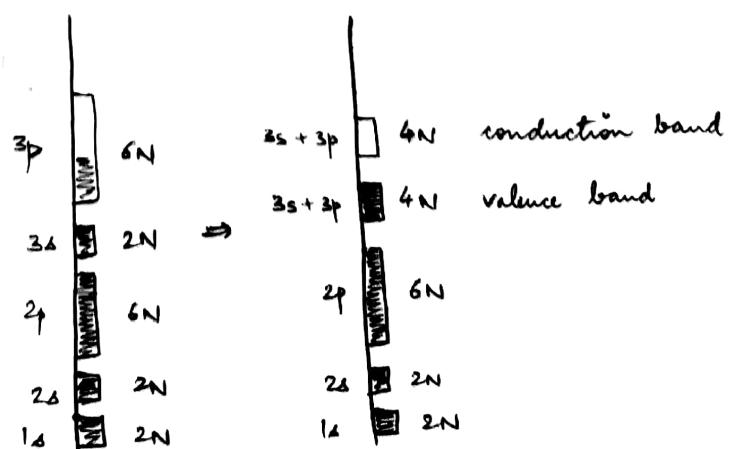
$$14 \Rightarrow 1s^2 2s^2 2p^6 3s^2, 3p^2$$




Flat band model

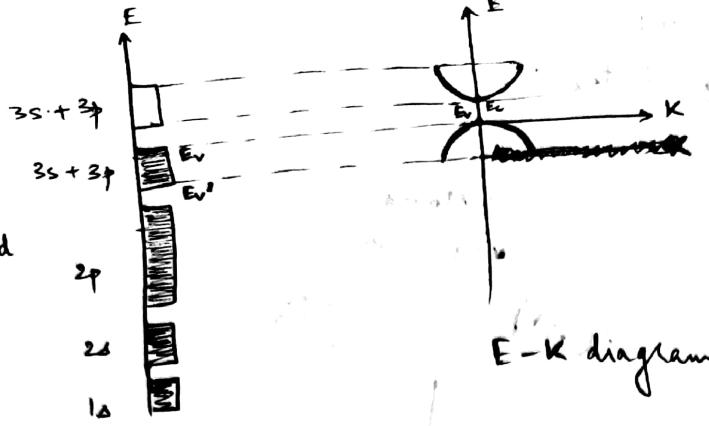

$$p = \hbar k$$

E-K diagram

$$I = \sum_{i \in I} -ev(k_i) = 0$$

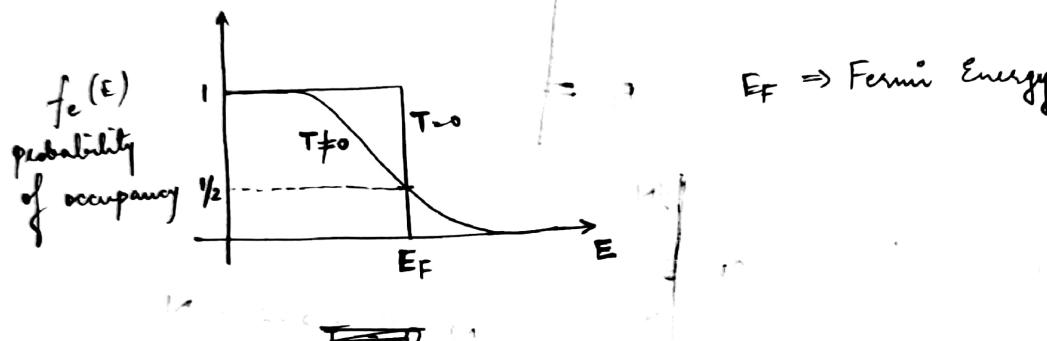


$E_F \Rightarrow$ Fermi Energy

$$n = \int f_e(E) D_c(E) dE$$

$D_c(E) dE \Rightarrow$ No. of states b/w E & $(E+dE)$

↓
no. of electrons

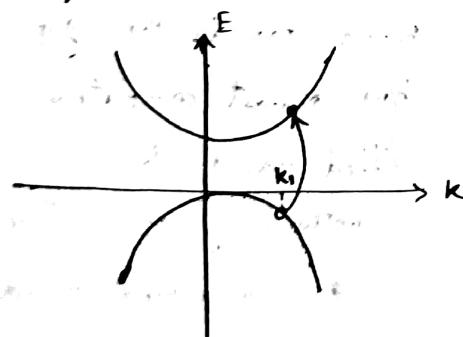


$$I = -\sum ev(k) \neq 0$$

$$I' = -\sum ev(k) \neq 0 \\ (\text{k except } k=k_1)$$


$$-\left[\sum_{k \neq k_1} ev(k) + ev(k_1) \right] = 0$$
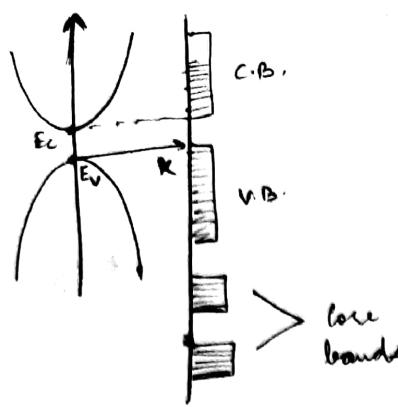
$$I' = -ev(k) = ev(k_1) \\ (\text{k except } k=k_1)$$



$$n = \int_{E_C}^{\text{top}} f_e(E) D_e(E) dE$$

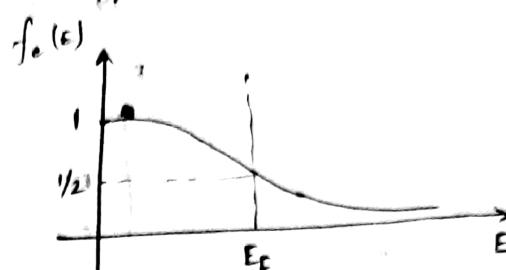
$$f_e(E) = \frac{1}{e^{(E-E_F)/k_B T} + 1}$$



$$D_e(E) = \frac{1}{2\pi^2} \left(\frac{2m}{\pi^2}\right)^{3/2} (E - E_C)^{1/2}$$

$$D_e(E) \propto (E - E_C)^{1/2}$$

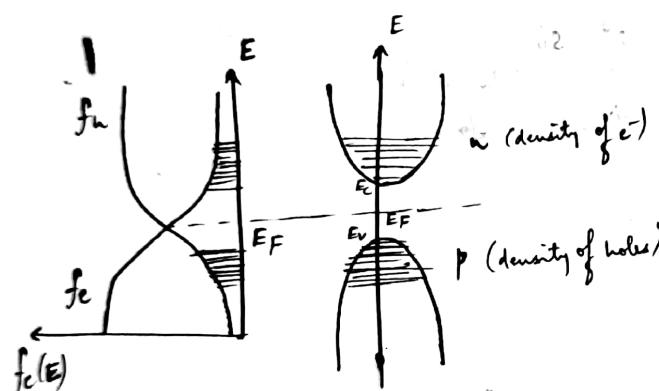
$f_n(E)$ & $f_e(E)$ are symmetric about E_F



E_F lies exactly in the middle of band gap in intrinsic semiconductor

$$f_n(E) = 1 - f_e(E)$$


↓
prob. of finding holes

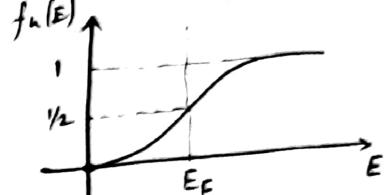


$$D_n(E) \propto (E_V - E)^{1/2}$$

$$p = \int_{\text{bottom}}^{E_V} f_n(E) D_n(E) dE$$
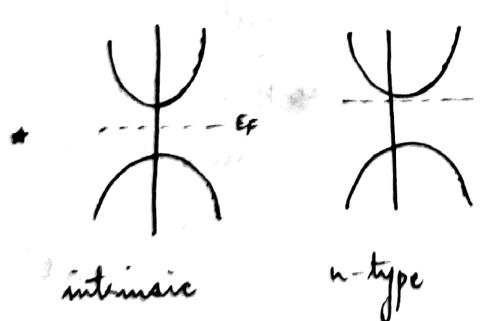
$$\begin{aligned} &= \frac{1}{s_i} = \frac{1}{s_i} = \frac{1}{s_i} = \frac{1}{s_i} = \\ &\quad \downarrow \quad \uparrow \\ &\quad \frac{1}{s_i} = \frac{1}{s_i} = p = \frac{1}{s_i} = \\ &\quad \downarrow \quad \uparrow \\ &\quad \frac{1}{s_i} = \frac{1}{s_i} = \frac{1}{s_i} = \frac{1}{s_i} = \end{aligned}$$



$$n_p = \text{const.}$$

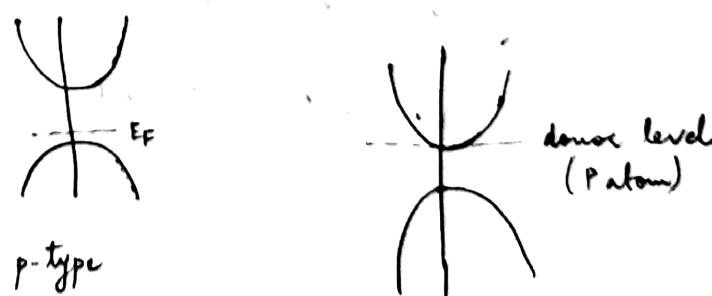


$$n = (n_i + n_D) \approx n_D$$

↓
density of intrinsic atoms
density of donor atoms


$$p \rightarrow \text{density of acceptor atoms} \quad p = p_i + p_A \approx p_A$$

$$n_i = 2 \left(\frac{k_e T}{2\pi \hbar^2} \right)^{3/2} (m_e^+ m_w^*)^{3/2} e^{-E_g/2k_B T}$$





Intrinsic
(Si)

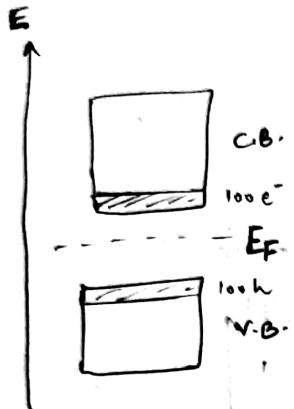

N-type

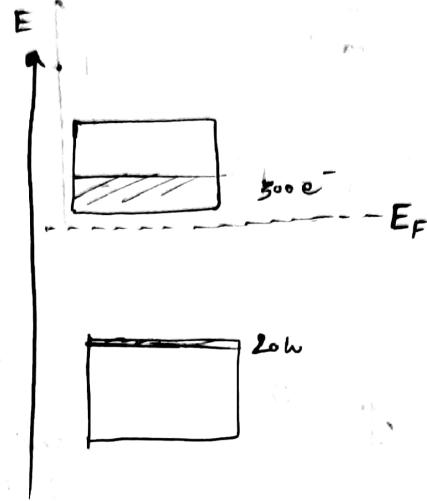


P-type

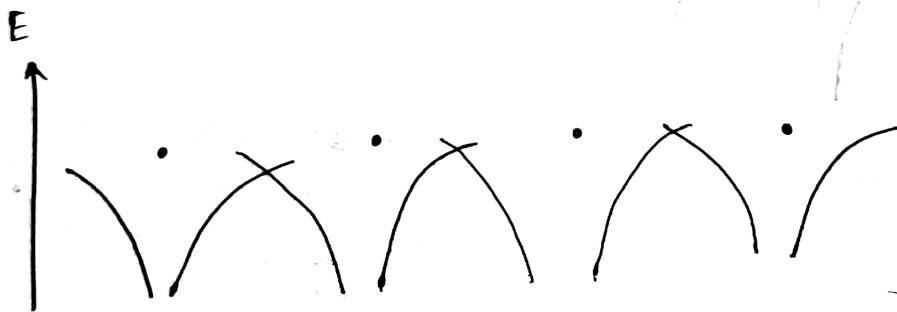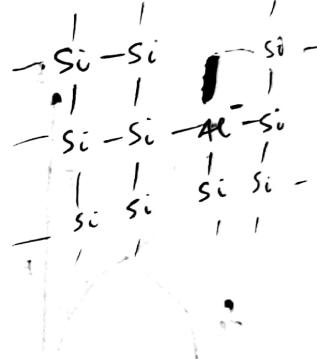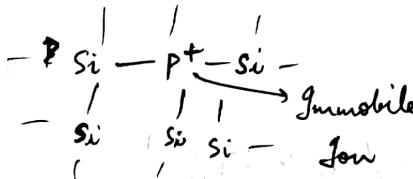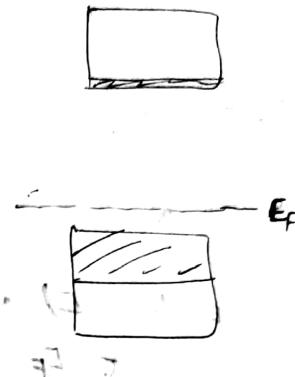

Crystal

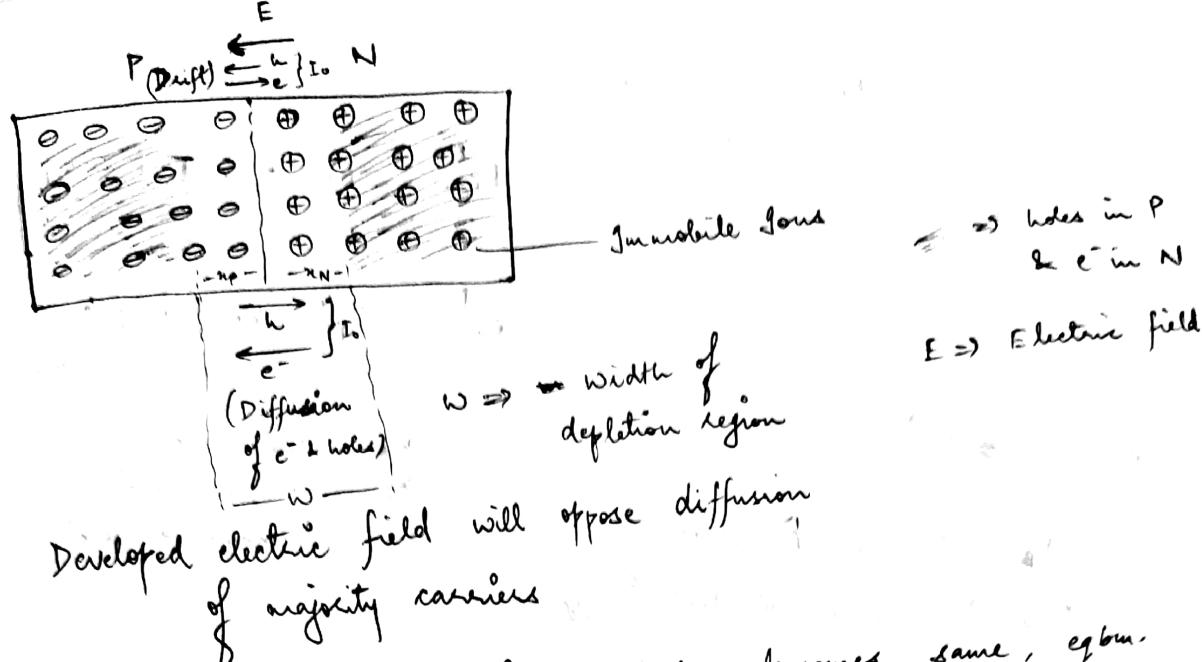Huge potential barrier at the surface
(e⁻ cannot eject out)



When diffusion & drift of e^- & holes becomes same, eqbm.
 is established. Diffusion is never stopped.



& no current flows.
 Drift of minority carriers depends on conc. of them & not on electric field.


$$\text{Drift velocity } v = \frac{\Delta s}{\Delta t}$$

$v = \text{chemical Potential}$
 Diffusion

$$E_F \approx v$$

At eqbm, v (or E_F) is uniform.

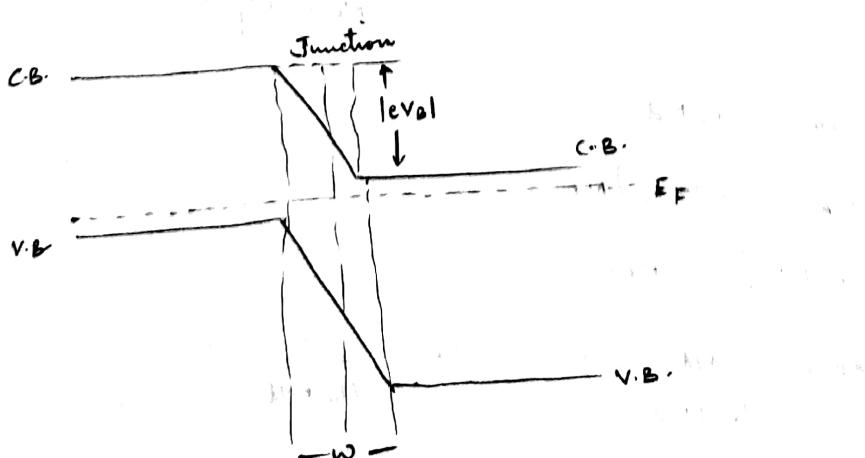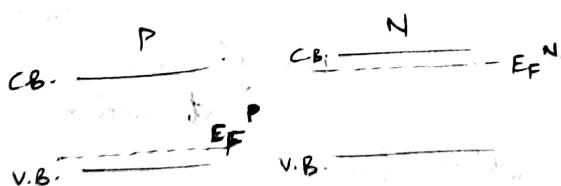

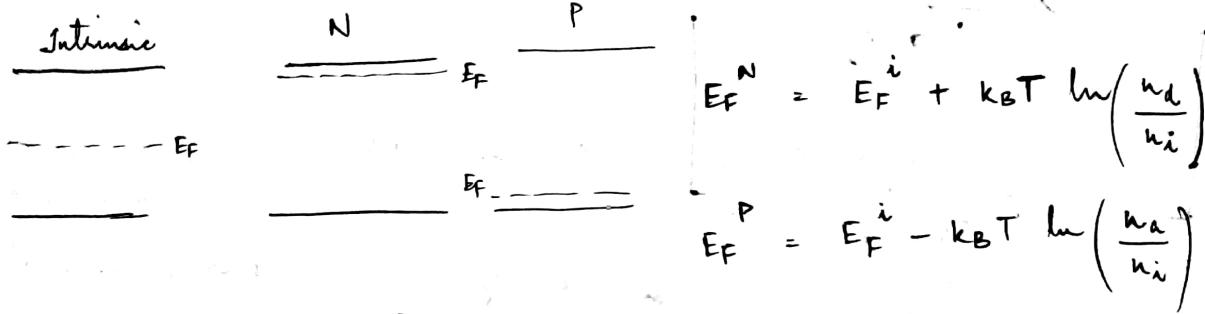

$$eV_B = E_F^N - E_F^P$$

$V_B \Rightarrow$ Barrier Potential

$eV_B \Rightarrow$ Barrier Potential Energy


$$eV_B = k_B T \ln \left(\frac{n_a \cdot n_d}{n_i^2} \right)$$

$n_d = \text{donor conc}$
 $n_a = \text{acceptor conc}$
 $n_i = \text{intrinsic e- conc}$

$x_p = \text{part of depletion region in p-type}$
 $x_n = \text{part of depletion region in n-type}$

$$I = I_0 \left(e^{\frac{qV}{nk_B T}} - 1 \right)$$

↓ ↓
Diffusion Drift

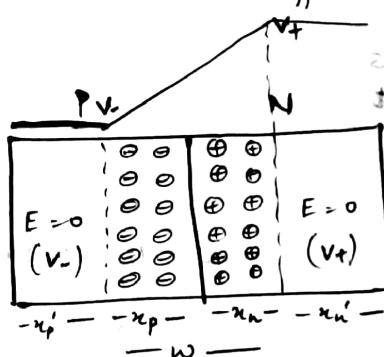

$$V_B = V_+ - V_-$$

$A \Rightarrow$ cross-sectional area

p-n junction
at electronics

$$(x_p A) N_a = \cancel{(A)} (x_n A) N_d \quad (\text{charge neutrality})$$


$$x_p N_A = x_n N_d$$

$$x_p N_A = (w - x_p) N_d$$

$$x_p (N_A + N_d) = N_d \cdot w$$

$$x_p = \frac{N_d}{N_d + N_A} \cdot w$$

$$x_n = \frac{N_A}{N_d + N_A} \cdot w$$

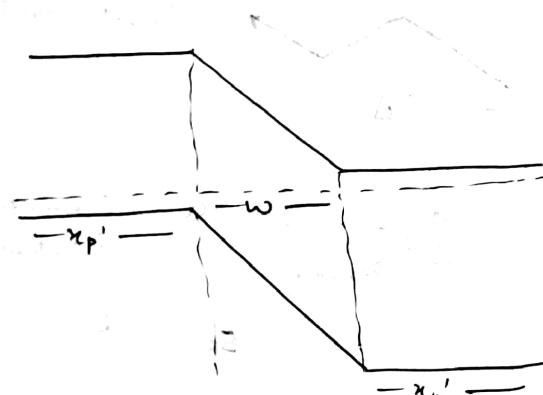

$$\vec{\nabla} \cdot \vec{E} = \frac{g}{\epsilon} \quad (\text{differential form of Gauss law})$$

$$\vec{\nabla} \cdot \vec{E}_P = \frac{-eN_a}{\epsilon} \quad -n_p < n < 0$$

$$\vec{\nabla} \cdot \vec{E}_N = \frac{+eN_d}{\epsilon} \quad 0 < n < n_N$$

$$\frac{dE_P}{dn} = -\frac{eN_a}{\epsilon}$$

$$+\int^{n_p(n)} dE_P = -\frac{eN_a}{\epsilon} \int_{-n_p}^n dn$$

$$E_p(n) = -\frac{eN_a}{\epsilon} [n + n_p] \quad -n_p < n < 0$$


$$E_N(n) = \frac{eN_d}{\epsilon} [n - n_N] \quad 0 < n < n_N$$

$$\begin{aligned} V &= \int dV = \int E(n) dn \\ &= \int_{-n_p}^0 -E_p(n) dn + \int_0^{n_N} -E_N(n) dn \\ &= \int_{-n_p}^{n_N} \frac{eN_a}{\epsilon} (n + n_p) dn + \int_0^{n_N} \frac{eN_d}{\epsilon} (n_N - n) dn \\ &= \frac{eN_a}{\epsilon} \left[\frac{n^2}{2} + n_p n \right]_{-n_p}^0 + \frac{eN_d}{\epsilon} \left[n_N n - \frac{n^2}{2} \right]_0^{n_N} \\ &= \frac{eN_a}{\epsilon} \left[\frac{-n_p^2}{2} + n_p^2 \right] + \frac{eN_d}{\epsilon} \left(n_N^2 - \frac{n_N^2}{2} \right) \end{aligned}$$


$$V_B = \frac{eN_a}{\epsilon} \frac{-n_p^2}{2} + \frac{eN_d}{\epsilon} \frac{n_N^2}{2}$$

$$V_B = \frac{1}{2\epsilon} e \left[N_a \left(\frac{N_d}{N_a + N_d} w \right)^2 + N_d \left(\frac{N_a}{N_a + N_d} w \right)^2 \right]$$
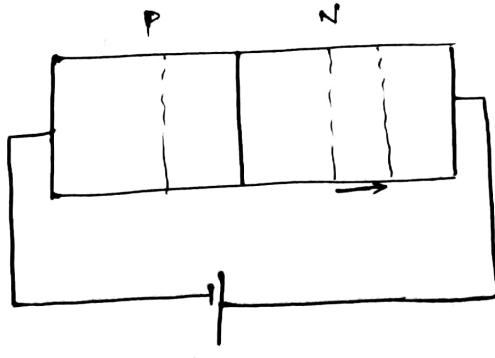
$$\frac{eN_a N_d w^2}{2\epsilon (N_a + N_d)} \Rightarrow V_B = \frac{e}{2\epsilon} w^2 \frac{N_a N_d}{N_a + N_d}$$





Reverse bias

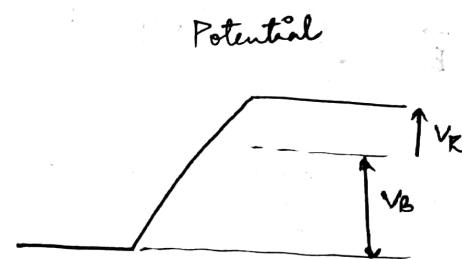

Barrier width increases &

V_F increases

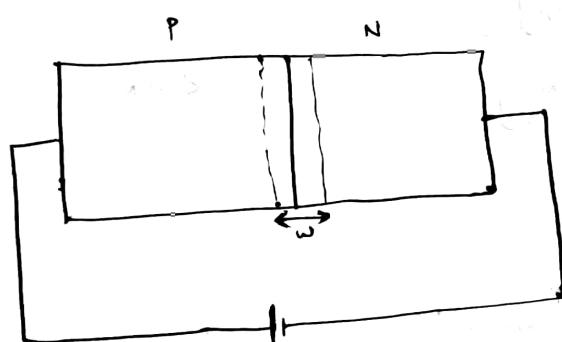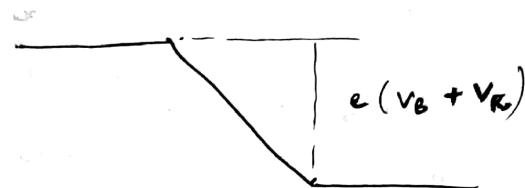


Forward bias

Potential energy

BARRIER width decreases

~~No bias~~ No bias

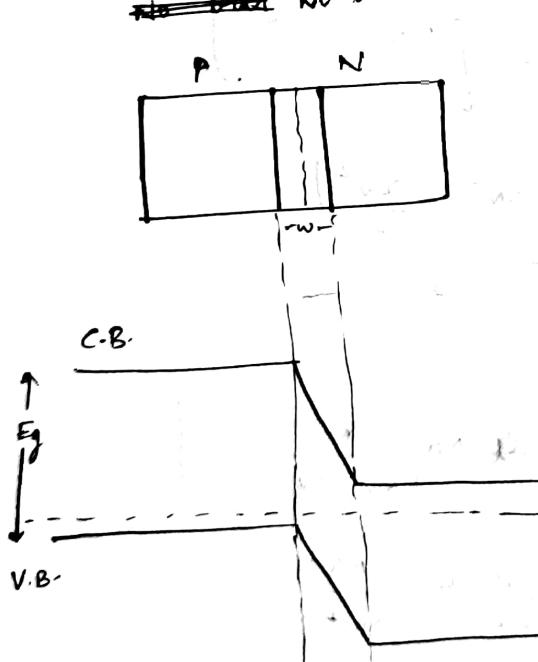


C.B.

V.B.

$$I_{\text{Total}} = 0$$


Reverse Bias

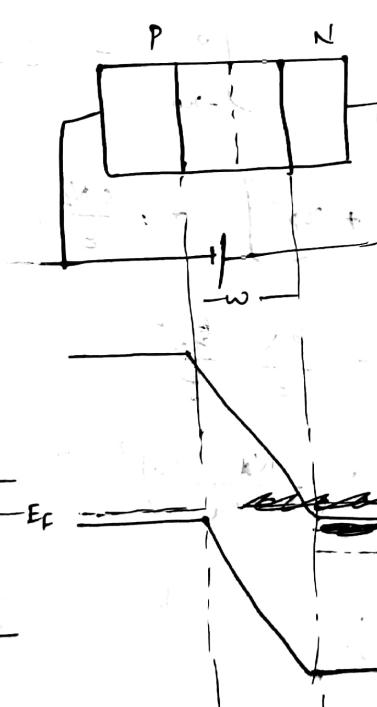


$$I_{\text{Total}}^R = I_0' - I_0$$

↓ majority ↓ minority


Forward Bias

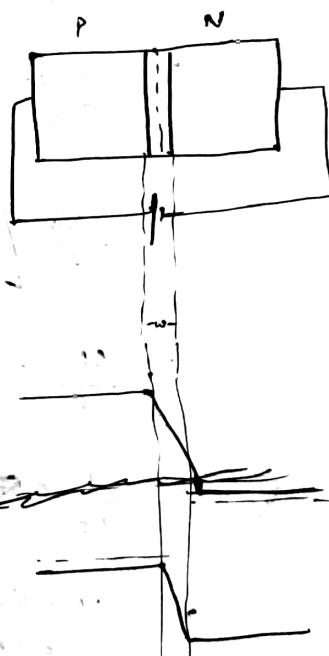

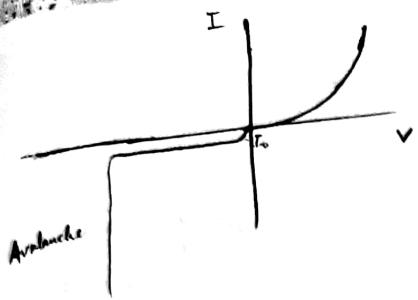
$$I_{\text{Total}}^F = I_0 \cdot e^{\frac{qV}{nk_B T}} - I_0$$



Transistor

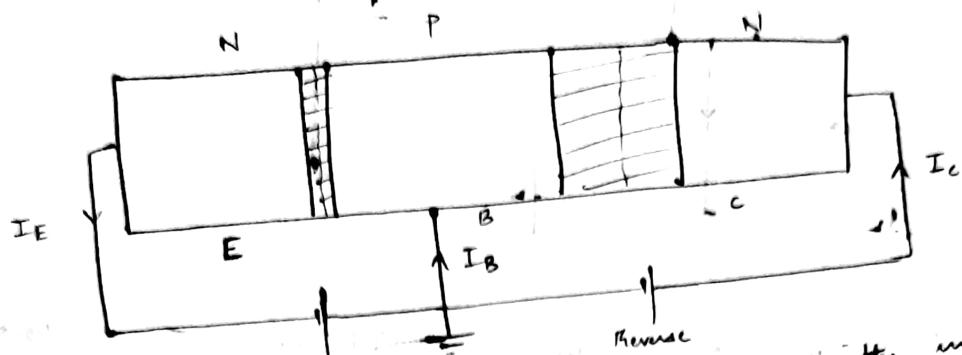

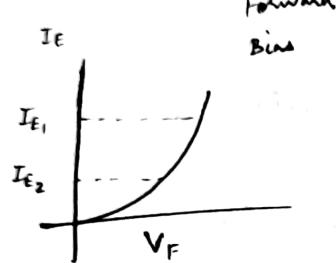
$$\begin{aligned} I_E &\Rightarrow -ve \\ I_B &\Rightarrow +ve \\ I_C &\Rightarrow +ve \end{aligned}$$





Emitter injects the minority carriers into the base.

Base controls the minority carriers.

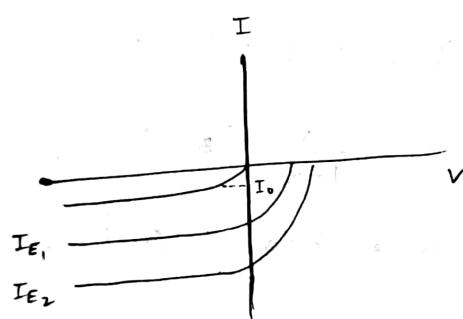Collector collects the minority carriers.



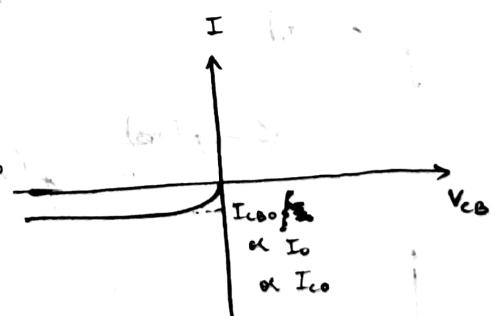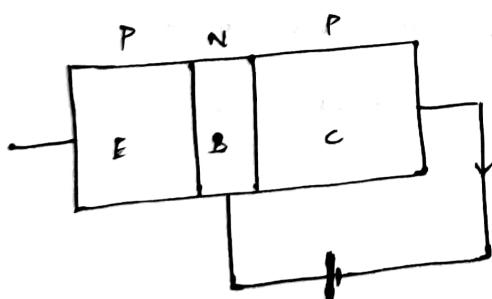Current going in $\Rightarrow +ve$
" " out $\Rightarrow -ve$



$I_{CBO} \Rightarrow I_{CB}$ when emitter is open


Doping levels are different regions

Emitter - Highly doped

Collector - Moderately doped

Base - Less doped



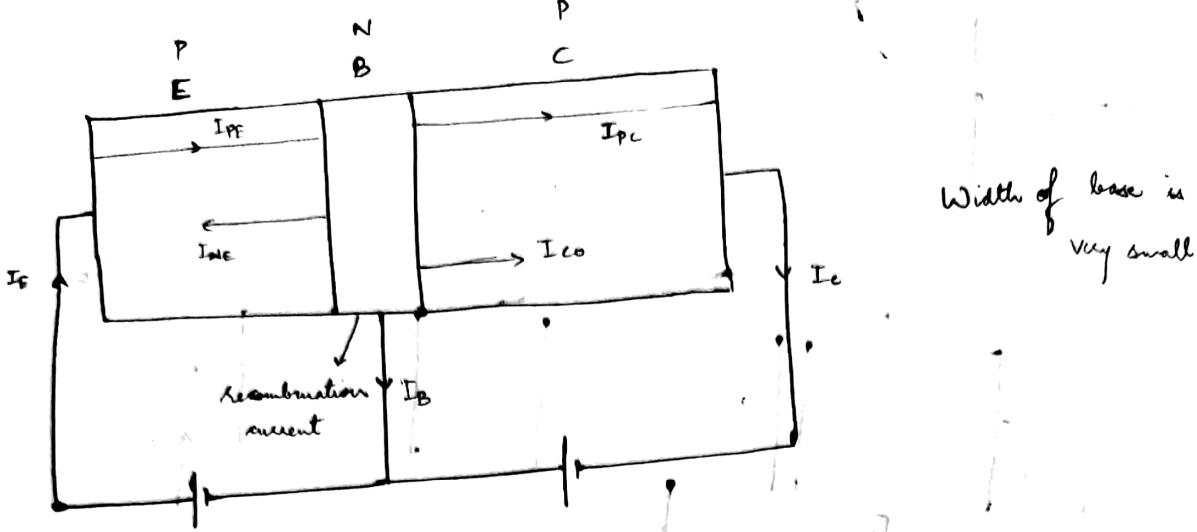

$$\text{Effective } \cancel{\text{width}} \text{ of base} = \text{Total width} - w_{\text{depletion}}$$

$$I_c = I_{pc} + I_{co}$$

I_{pc} is a fraction of I_E

$$I_c = \alpha I_E + I_{co} \quad (\text{Active region})$$


$$I_c \approx \alpha I_E$$








$$I_c \approx \alpha (I_c + I_B) + I_{co}$$

$$I_c = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{co}$$

$$I_c = \beta I_B + (\beta+1) I_{co}$$

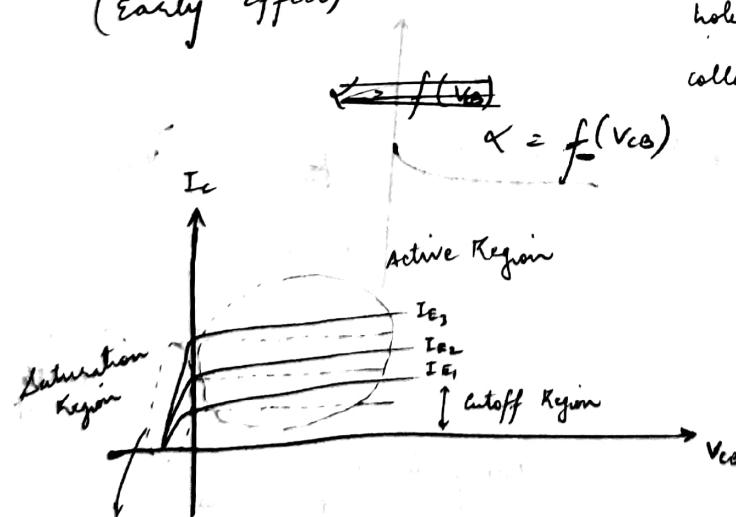Base width modulation with V_{CB} \Rightarrow Increase in V_{CB} will decrease the width & more and more holes will move to the collector increasing I_c




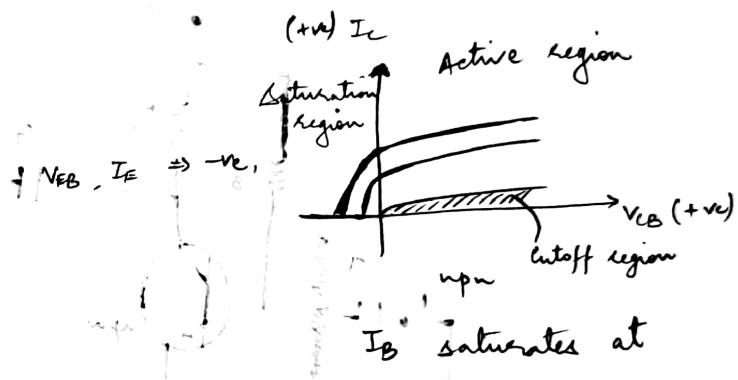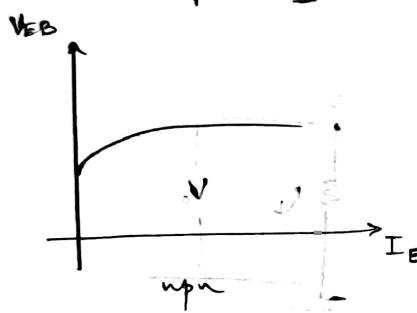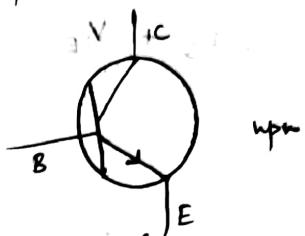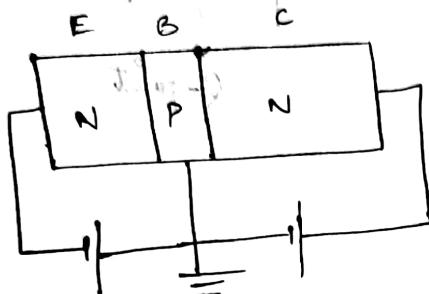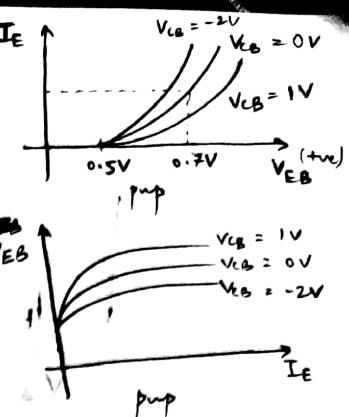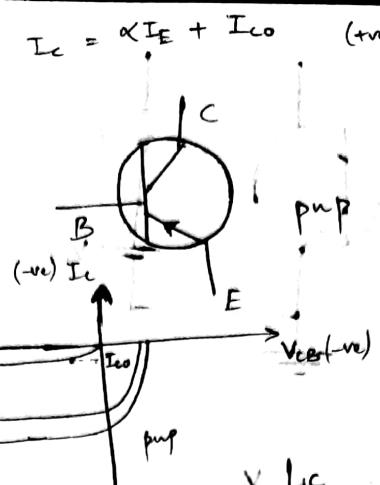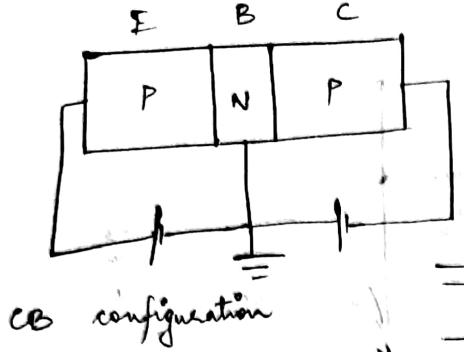

I_B saturates at saturation region

$$I_B > (I_B)_{\min}$$

Condition of saturation

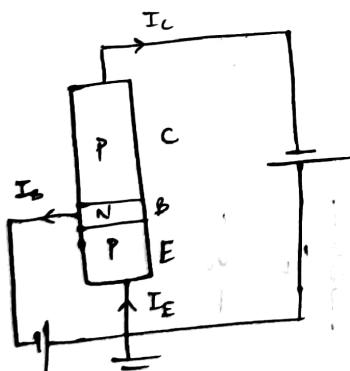

CE configuration

$$\text{Saturation region} \Rightarrow V_{CB} \approx 0.5V \Rightarrow V_{EB} \approx 0.5V$$


$$\text{Active region} \Rightarrow V_{EB} = 0.7V \quad (\text{s.i.})$$


$$V_{CE} = V_{CB} + V_{BE}$$

$$= 0.3V \quad (\text{saturation region})$$




$$I_C = \beta I_B + (\beta + 1) I_{CO}$$
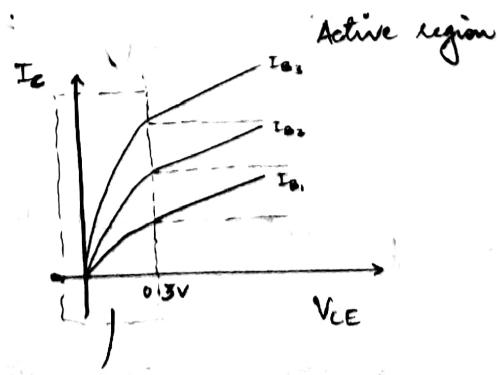
$$= \frac{\kappa}{1-\kappa} I_B + \frac{1}{1-\kappa} I_{CO}$$



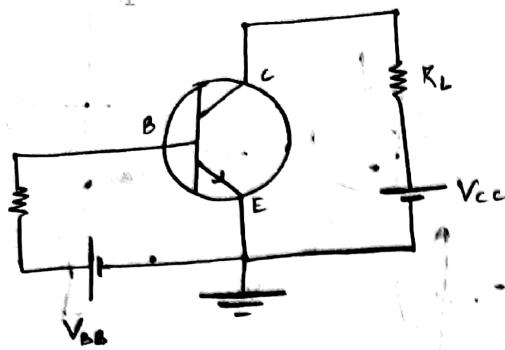

$$V_{CC} = I_C R_L + V_{CE}$$

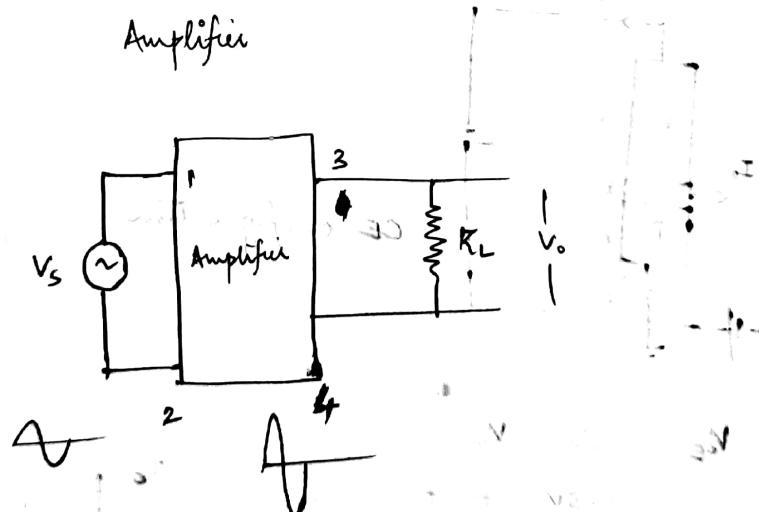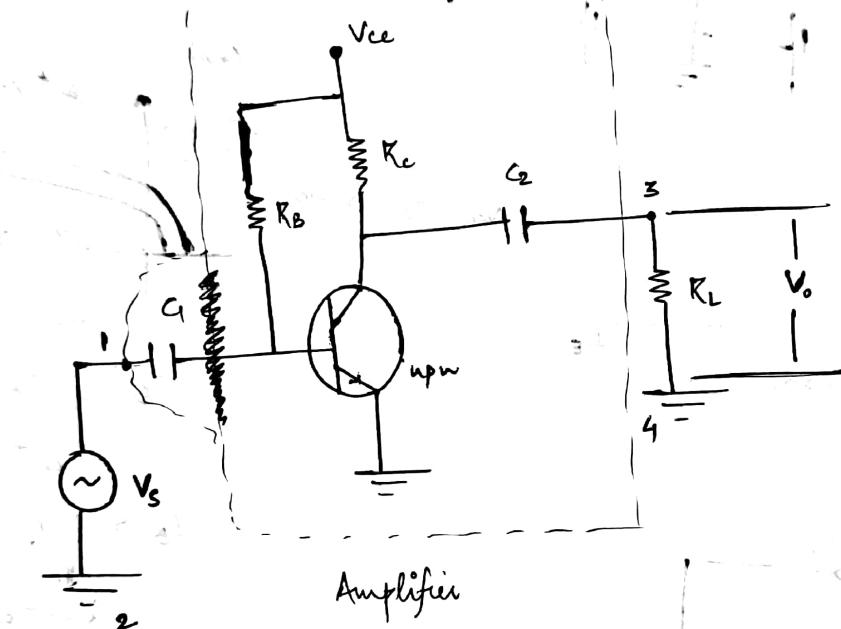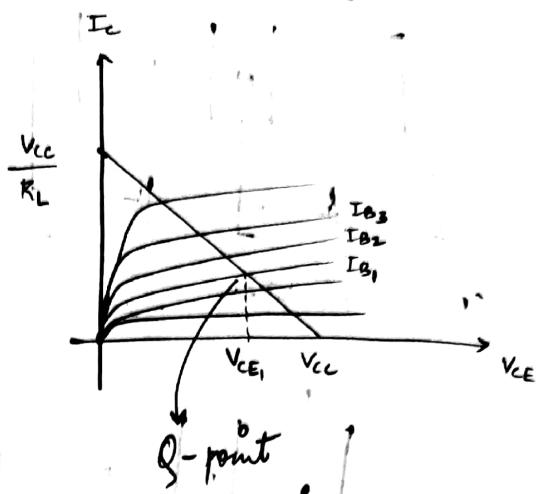

Blocking capacitor is used to block the DC part of the circuit.

$$V_{BE} = V_{BE}^{\text{DC value}} + V_{BE}^{\text{AC input signal}}$$

Instantaneous voltage at E-B junction

$$i_B = I_B + i_b$$

$$i_C = I_C + i_c$$


$$V_o = V_{CE} = V_{CC} - i_C R_C$$



Q Amplification of signal without any distortion can only be made when Q-point is in the middle of the load line.

DC Bias is required to keep it on in the active region to ensure ~~amplified~~ amplification without distortion.
Class-A amplifier is an amplifier in which Q-point is in middle of load line & is in active region.

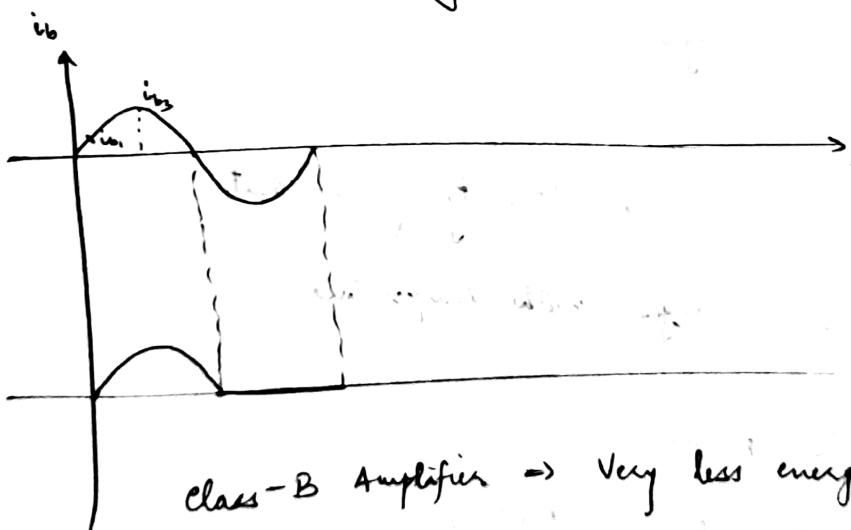DC bias - Establishment & suitable Q-point
Small signal operation





class-B Amplifier \rightarrow Very less energy consumption

Accommodate large signal

(Q-point is in saturation initially)

Can only amplify one part of signal

Distortion in crossover region

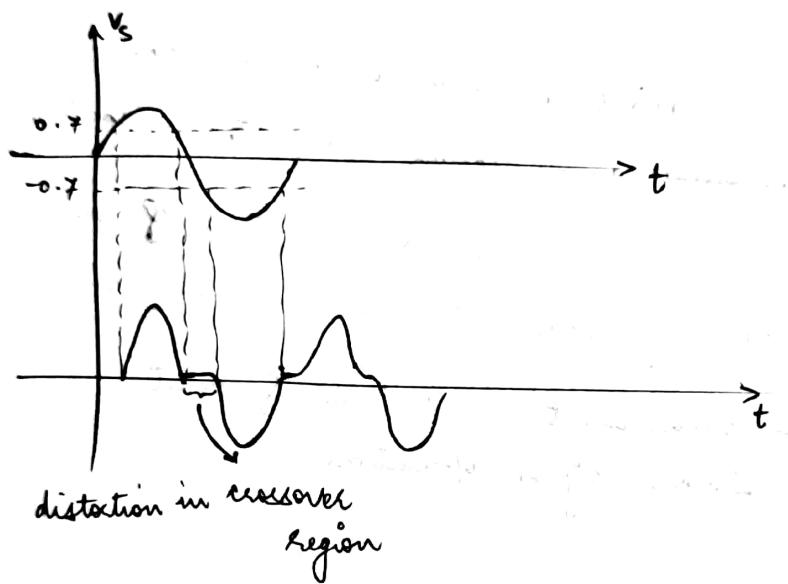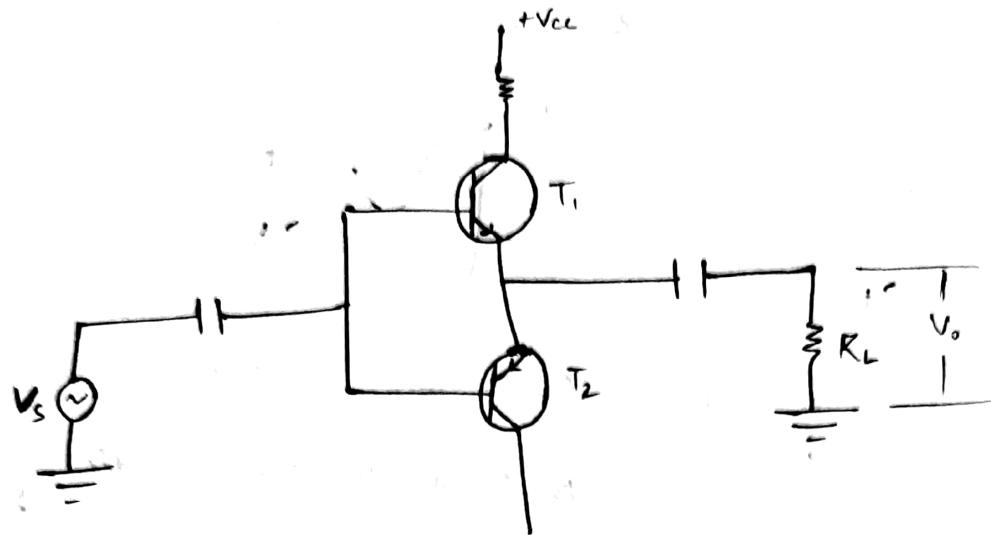

Thermal Stability of Q-Point


V_{BE} , β , I_{CO} changes with temperature


$$Q(I_c, I_B, V_{CE})$$

$$I_c = \beta I_B + (\beta + 1) I_{CO}$$

$T \uparrow \Rightarrow$ minority carriers $\uparrow \Rightarrow I_{CO} \uparrow \Rightarrow I_c \uparrow \Rightarrow Q\text{-point shifts}$
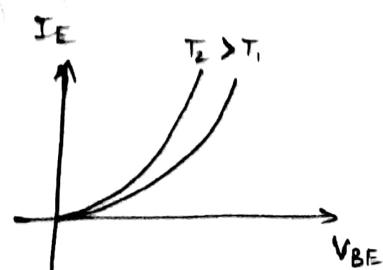
$$I_E = I_{EBO} \left(e^{\frac{eV}{kT}} - 1 \right)$$



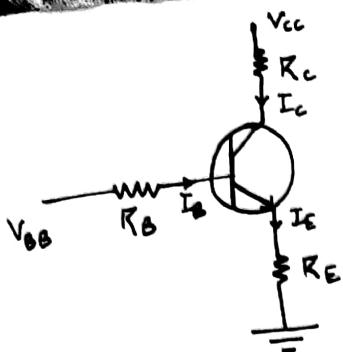

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

$$= I_B R_B + V_{BE} + (I_c + I_B) R_E$$

$$= I_B (R_B + R_E) + \cancel{V_{BE}} + I_c R_E$$

$$V_{BB} = I_c R_E + (R_B + R_E) \left[\frac{I_c}{\beta} - \frac{\beta+1}{\beta} I_{CO} \right] + V_{BE}$$

$$V_{BB} = \left(R_E + \frac{R_B + R_E}{\beta} \right) I_c - \cancel{\frac{\beta+1}{\beta} (R_B + R_E) I_{CO}} + V_{BE}$$

Thermal stability parameters

$$S = \left(\frac{\partial I_c}{\partial I_{CO}} \right)_{V_{BE}, \beta} \quad S' = \left(\frac{\partial I_c}{\partial V_{BE}} \right)_{I_{CO}, \beta} \quad S'' = \left(\frac{\partial I_c}{\partial \beta} \right)_{V_{BE}, I_{CO}}$$

$$S = \left(\frac{\partial I_c}{\partial I_{CO}} \right)_{V_{BE}, \beta} = \frac{\frac{\beta+1}{\beta} (R_B + R_E)}{\left(R_E + \frac{R_B + R_E}{\beta} \right)}$$

$$S = \frac{(\beta+1)(R_B + R_E)}{R_B + (1+\beta)R_E}$$

$$S = \frac{(\beta+1) \left(1 + \frac{R_B}{R_E} \right)}{1 + \beta + \frac{R_B}{R_E}}$$

$$S = 1 + \beta \text{ if } R_E = 0$$




$$S \approx 1 \text{ if } \frac{R_B}{R_E} \ll 1$$

$$S' = \left(\frac{\partial I_c}{\partial V_{BE}} \right)_{\beta, I_{CO}} = \frac{-\beta}{(1+\beta)R_E + R_B}$$

$$S' = \frac{-\beta}{R_B} \text{ if } R_E = 0$$

$$S' \approx \frac{-\beta}{1+\beta} \text{ if } \frac{R_B}{R_E} \ll 1$$
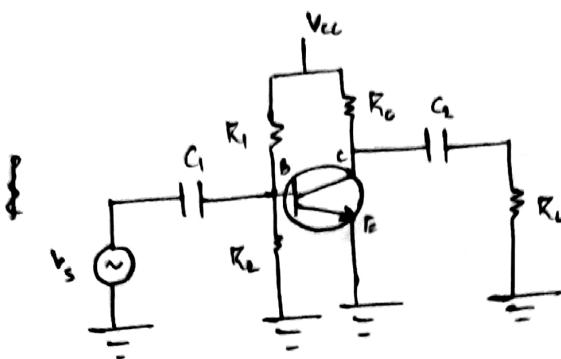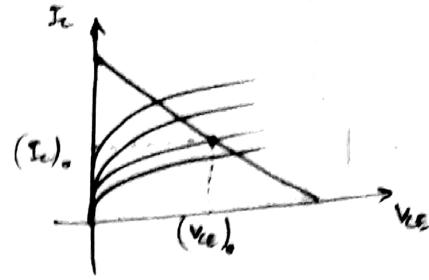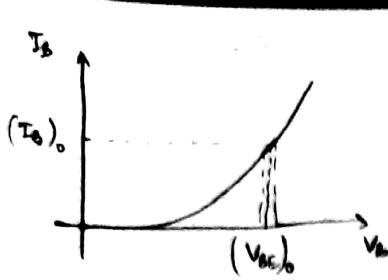
$$S'' = \left(\frac{\partial I_c}{\partial \beta} \right)_{I_{CO}, V_{BE}} = \frac{\left(R_B + R_E \right) I_c}{R_E + \frac{R_B + R_E}{\beta}} \approx \frac{S I_c}{\beta (\beta+1)}$$



$$V_{CE} \propto i_c$$

$$V_{BE} \propto i_b$$

$$V_{BE} = h_{FE} i_b$$

$$V_{BE} = (V_{BE})_o + V_{be}$$

$$i_B = (I_c)_o + i_b$$

$$V_{CE} = (V_{CE})_o + V_{ce}$$

$$i_c = (I_c)_o + i_c$$

$$\Delta V_{BE} = V_{BE} - (V_{BE})_o = V_{be}$$

$$V_{BE} = f(i_b, V_{ce})$$

$$V_{BE} = (V_{BE})_o + \left(\frac{\partial V_{BE}}{\partial i_b} \right)_{V_{ce}} \Delta i_b + \left(\frac{\partial V_{BE}}{\partial V_{ce}} \right)_{i_b} \Delta V_{ce}$$

evaluated at Q-point

evaluated at Q-point

$$V_{be} = V_{BE} - (V_{BE})_o = \left(\frac{\partial V_{BE}}{\partial i_b} \right)_{V_{ce}} \Delta i_b + \left(\frac{\partial V_{BE}}{\partial V_{ce}} \right)_{i_b} \Delta V_{ce}$$

~~$$V_{be} = h_{FE} i_b + h_{oe} V_{ce}$$~~

$$i_c = f(V_{ce}, i_b)$$

$$i_c = (I_c)_o + \left(\frac{\partial i_c}{\partial i_b} \right)_{V_{ce}} \Delta i_b + \left(\frac{\partial i_c}{\partial V_{ce}} \right)_{i_b} \Delta V_{ce}$$


evaluated at Q-point

evaluated at Q-point

$$i_c = i_c - (I_c)_o = \left(\frac{\partial i_c}{\partial i_b} \right)_{V_{ce}} i_b + \left(\frac{\partial i_c}{\partial V_{ce}} \right)_{i_b} V_{ce}$$


$$i_c = h_{fe} i_b + h_{oe} V_{ce}$$
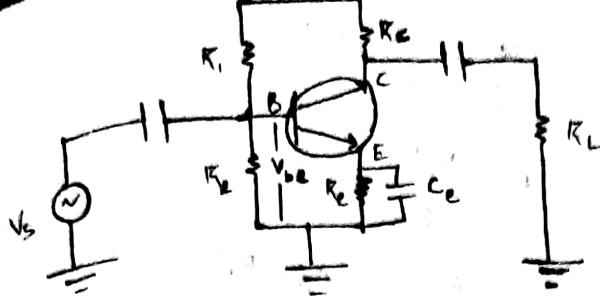
$$\frac{1}{h_{oe}} = \frac{V_{ce}}{i_c}$$



$$V_{be} = h_{fe} i_b + h_{oe} V_{ce}$$


$$i_c = h_{fe} i_b + h_{oe} V_{ce}$$

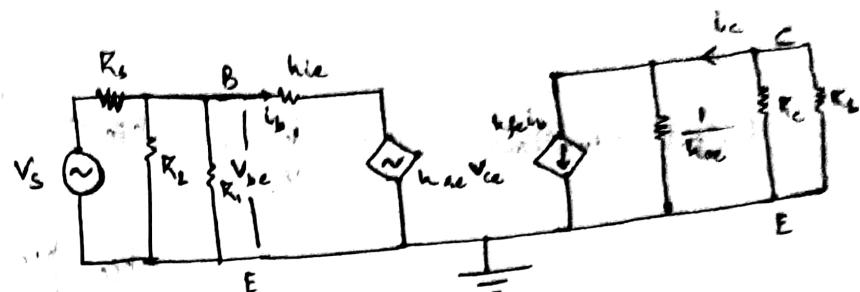

Small Signal Analysis

$R_s \rightarrow$ Internal resistance
of AC source

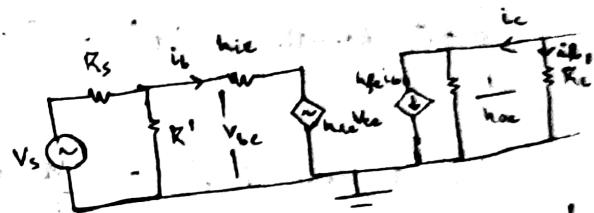1) Remove DC voltage B. source
with short



2) Remove my capacitor with
short

Current gain \Rightarrow

$$A_I = \frac{i_c}{i_b} = \frac{-i_c}{i_b}$$

$$= h_{fe} + h_{oe} \frac{V_{ce}}{i_b}$$

$$= h_{fe} + h_{oe} \frac{i_c R_L'}{i_b}$$

$$A_I = h_{fe} + h_{oe} \frac{(-i_c) R_L'}{i_b}$$

$$A_I = h_{fe} - A_I' R_L' h_{oe}$$

$$A_I = \frac{-h_{fe}}{1 + R_L' h_{oe}}$$

Input impedance (Z_i) seen from BE terminal

$$Z_i = \frac{V_{be}}{i_b} = h_{ie} + h_{oe} \frac{V_{ce}}{i_b}$$

$$= h_{ie} + h_{oe} \frac{i_c R_L'}{i_b}$$

$$Z_i = h_{ie} + h_{oe} A_I R_L'$$


$$\text{Voltage Gain } (A_v) = \frac{i_e R_L'}{V_{be}} = \frac{i_e + i_b}{i_e} \frac{i_b}{V_{be}} R_L' \\ = A_I \frac{R_L'}{Z_i} \\ \boxed{A_v = A_I \frac{R_L'}{Z_i}}$$

$$\text{Output Admittance } (\gamma) = \frac{i_c}{V_{ce}} = \frac{i_c}{V_{ce}} h_{fe} \frac{i_b}{V_{ce}} + h_{oc} \\ = h_{fe} \frac{h_{ie}}{h_{ie}} + h_{oc} \quad (\because h_{oc} + h_{ie} V_{ce} = 0) \\ \frac{i_o}{V_{ce}} = -\frac{h_{oc}}{h_{ie}}$$

Impedance


$$\text{Input } \underline{\underline{z_{in}}} = R_s + R' \parallel Z_i \quad \text{seen from } V_S$$
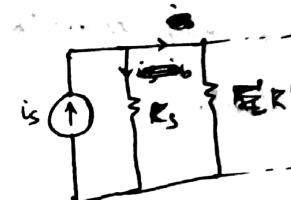
$$\text{Current Gain } (A_{IS}) = \frac{i_e}{i_b} \frac{i_b}{i_s} \\ = A_I \frac{R''}{R'' + Z_i}$$




$$R'' = R' \parallel R_s$$
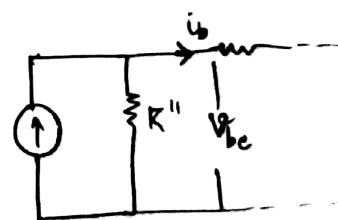
$$\cancel{(is)} (i_s - i_b) R'' = i_b Z_i$$


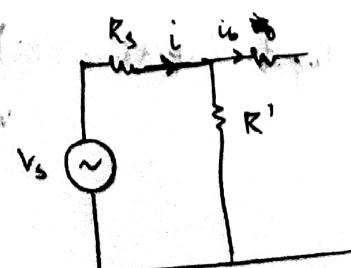
$$\frac{i_b}{i_s} = \frac{R''}{R'' + Z_i}$$



$$(i_s - i_b) R' = i_b Z_i$$

$$V_S - iR_s - (i_s - i_b) R' = 0$$

$$V_S = i(R_s + R') - i_b R'$$

$$i = \frac{V_S + i_b R'}{R_s + R'}$$