
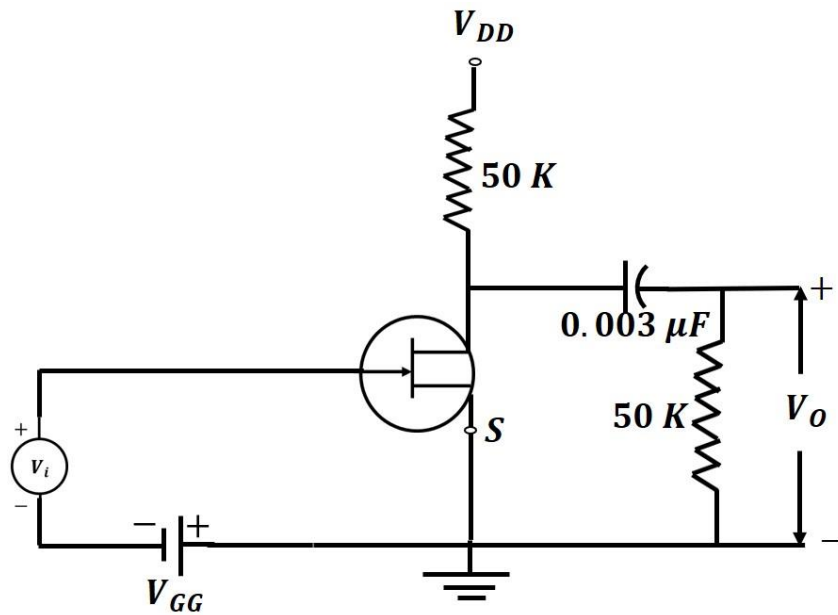


### Tutorial -3

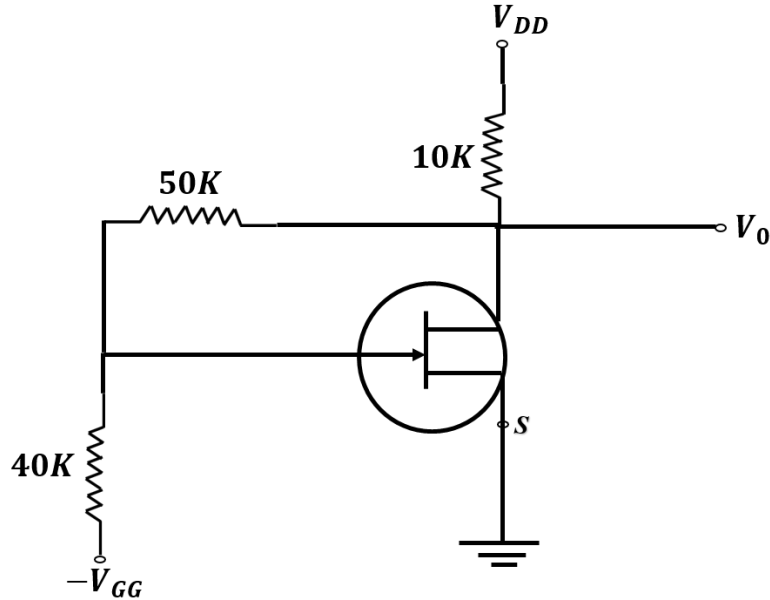1. Calculate the voltage gain  $A_v = V_o/V_i$ , at 1 kHz for the circuit shown below. The FET parameters are  $g_m = 2 \text{ mA/V}$  and  $r_d = 10 \text{ K}$ . Neglect capacitances.



2. If an input signal  $V_i$  is impressed between gate and ground, find the amplification  $A_v = V_o/V_i$ . Apply Miller's theorem to the 50 K resistor. The FET parameters are  $\mu = 30$  and  $r_d = 5K$ . Neglect capacitances.




3. (a) Prove that the magnitude of the signal current is the same in both FETs provided that

$$r = \frac{1}{g_m} + \frac{2R_L}{\mu}$$


Neglect the reactance of the capacitors.

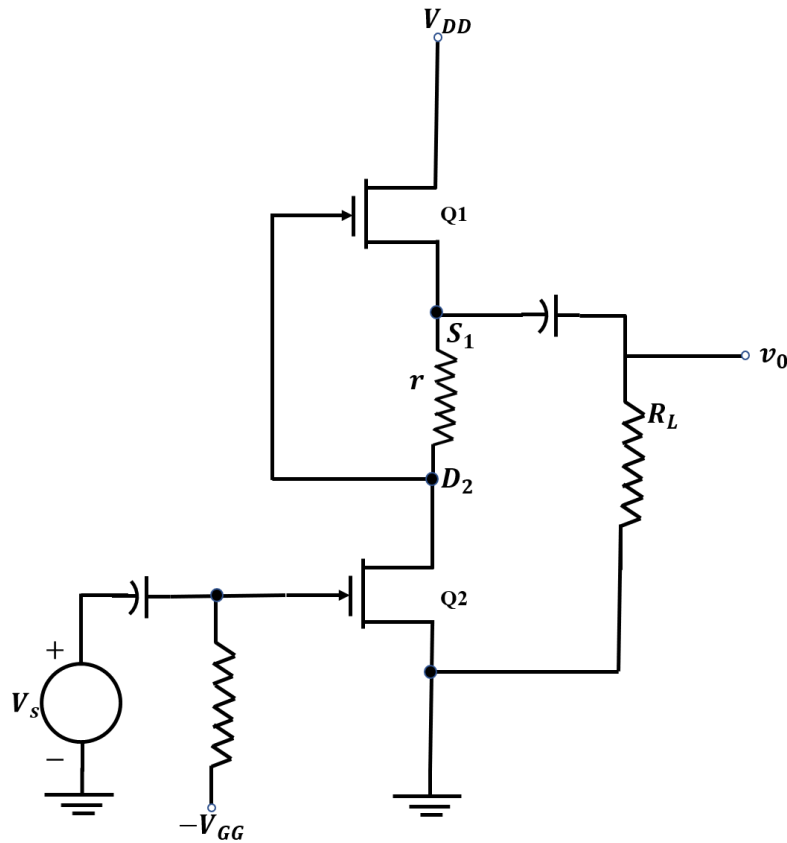(b) If  $r$  is chosen as part *a*, prove that the voltage gain is given by

$$A = \frac{-\mu^2}{\mu + 1} \frac{R_L}{R_L + r_d/2}$$



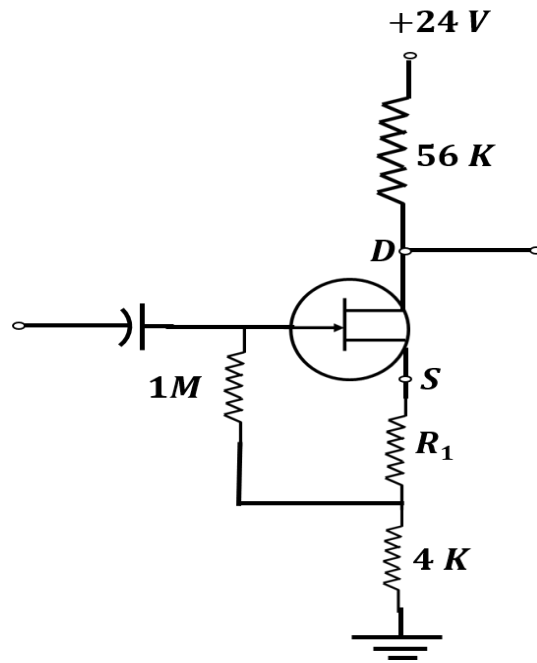4. The amplifier stage shown uses an n-channel FET having  $I_{DSS} = 1 \text{ mA}$ ,  $V_p = -1 \text{ V}$ . If the quiescent drain to ground voltage is 10 V, find  $R_1$ .



5. The FET shown has the following parameters,  $I_{DSS} = 5.6\text{ mA}$ ,  $V_p = -4\text{ V}$ .

- (a) If  $v_i = 0$ , find  $v_o$ ;
- (b) If  $v_i = 10\text{ V}$ , find  $v_o$ ;
- (c) If  $v_o = 0\text{ V}$ , find  $v_i$ ;

Note:  $v_o$  and  $v_i$  are constant voltages (and not small signal voltages).

