

Final Semester

Course: PH209

Full marks: 50

1. a) Find the *CC* *h* parameters in terms of the *CE* *h* parameters. [Marks 3]
- b) For the circuit shown below (Figure 1), find *small signal voltage gain* (A_{vs}) and *input impedance* (in terms of A_{vs}) as seen from the source terminals. Analyze the problem **without using Feedback concept and using Millar's theorem** applied to the resistance R_1 . Use h-parameter model and assume $h_{oe} = h_{re} = 0$. [Marks 5+2]

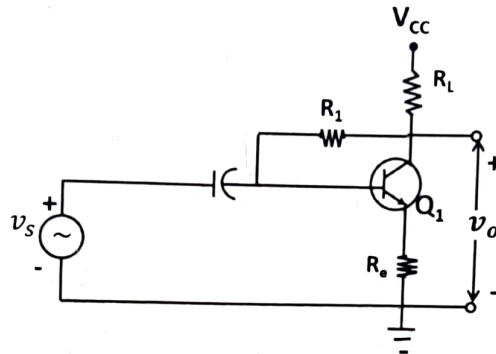


Figure 1

2. a) How negative feedback influence *voltage gain*, *input impedance* and *output impedance* of a voltage series amplifier? [Marks 1]

- b) For the circuit shown below (figure 2), find the *voltage gain*, and *input impedance* seen from the source voltage terminals **using the feedback concept** (without using the direct formula of voltage gain and input impedance).

[Use h-parameter model and assume, $R_s = 0$, $h_{fe} = 50$, $h_{ie} = 1.1k$, $h_{re} = h_{oe} = 0$, and current through $4.7k$ resistance in the emitter of Q_1 is negligible as compared to current through R_2 , and both the transistors are identical]

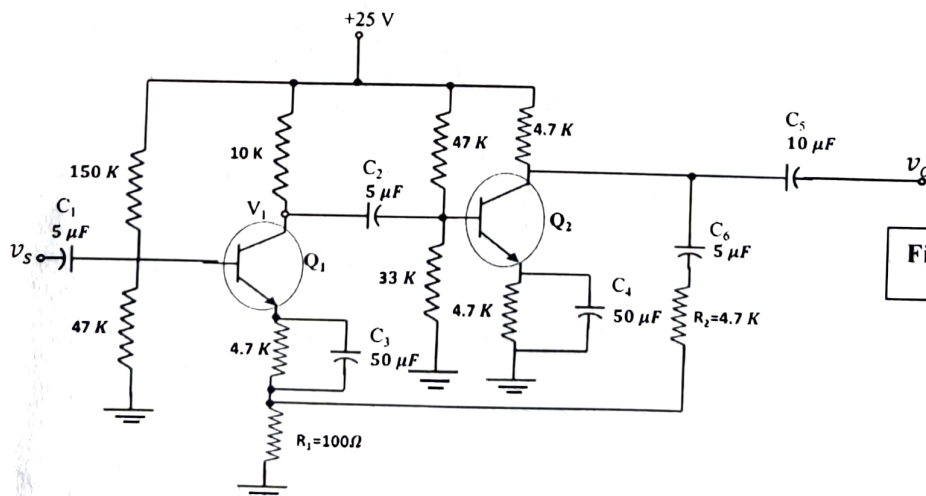


Figure 2

3. a) Briefly explain how a differential amplifier with very large CMRR can be used for amplification with minimal effect from noise signal. [Marks 3]

easy

$$A_{v1} = \frac{v_{o1}}{v_i}$$

b) What is the *virtual ground* of an ideal OPAMP?

[Marks 2]

c) Design Log and Anti-log amplifier using OPAMP (ideal), and find expression of their outputs. Using these Log and Anti-log amplifiers, draw a multiplier circuit, and show the outputs at every stage.

[Marks 2+2+1+2]

d) Show that the circuit of the accompanying figure 3 can simulate a grounded inductor if $R_1 > R_2$. In other words, show that the reactive part of the input impedance of the circuit is positive if $R_1 > R_2$. The OPAMP is an ideal one.

[Marks 6]

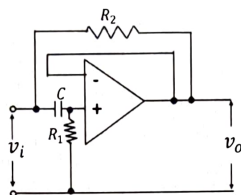


Figure 3

4. An OPAMP-based oscillator circuit (Figure 4). The signal v_s is given once and then the key switched from B point to A point

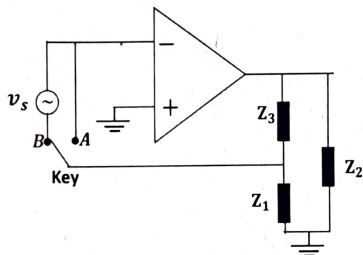


Figure 4

Considering a **non-ideal** OPAMP having *non-zero* output impedance (R_o) and *infinite input impedance*, and finite gain without load, Show that

either (i) Z_1 and Z_2 are capacitor and Z_3 is an inductor,

[Marks 6]

or (ii) Z_1, Z_2 are inductor and Z_3 is a capacitor

[Note: In a practical oscillator circuit no external signal voltage (v_s) is given, the signal is taken from the noise while switching on the device]

5. If $|I_{DSS}| = 4 \text{ mA}$, $V_p = 4 \text{ V}$, calculate the quiescent values of I_D , V_{GS} and V_{DS} for the circuit given below

[Marks 5]

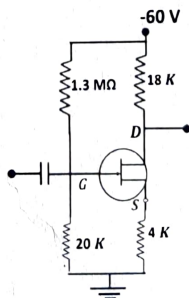


Figure 5