

1. For silicon at T=300K, Intrinsic carrier concentration ( $n_i$ ) =  $1.45 \times 10^{10} \text{ cm}^{-3}$ . This silicon is doped at room temperature (300K) with Arsenic atoms (pentavalent), and the donor concentration is ( $N_D$ ) =  $6 \times 10^{16} \text{ cm}^{-3}$ .

Find the equilibrium concentration of electrons, holes and shift of the chemical potential (Fermi level) with respect to intrinsic chemical potential.

$$n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$$

$$T = 300 \text{ K}$$

$$N_D = 6 \times 10^{16} \text{ cm}^{-3} \approx n$$

$$\text{mass-action, } np = n_i^2$$

$$\Rightarrow p = \frac{(1.45 \times 10^{10})^2}{6 \times 10^{16}} = 3.05 \times 10^{-3} \text{ cm}^{-3}$$

$$E_F = E_i + KT \ln\left(\frac{N_D}{n_i}\right) \quad K = 8.617 \times 10^{-5} \text{ eV/K}$$

Intrinsic energy level

$$\Delta E = (8.617 \times 10^{-5} \times 300) \ln\left(\frac{6 \times 10^{16}}{1.45 \times 10^{10}}\right)$$

$$= 2.5851 \times 10^{-5} \times \ln(4.1379 \times 10^6)$$

$$= 0.3938 \text{ eV}$$


2. For the circuit shown, assume  $\beta = h_{FE} = 100$

a) Find if the silicon transistor is in cutoff, saturation or in the active region.

b) Find  $V_O$

c) Find the minimum value for the emitter resistance  $R_e$  for which the transistor operates in the active region.

Assume in cutoff, current = 0

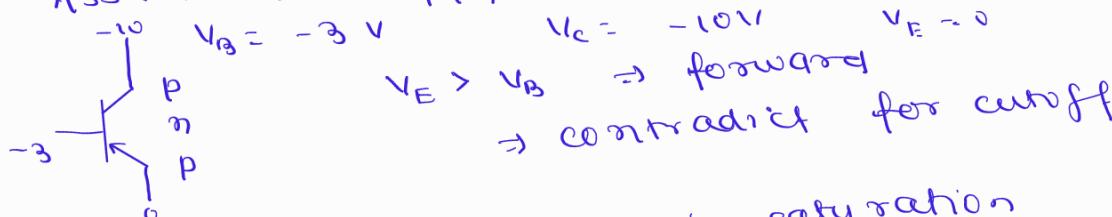

Let's, Q in saturation

$$V_{BE} = 0.8 \text{ V} \quad V_{BC} = 0.5 \text{ V}$$

$$I_E = -\frac{V_E}{R_e} \text{ mA} = -2(V_B + 0.8)$$

$$I_E = \frac{V_B + 0.5 + 10}{3}$$

$$I_E = I_B + I_C$$

$$\Rightarrow -2(V_B + 0.8) = \frac{V_B + 3}{7} + \frac{V_B + 10.5}{3}$$

$$\Rightarrow -1.6 - \frac{3}{7} - \frac{10.5}{3} = +\frac{V_B}{7} + \frac{V_B}{3} + 2V_B$$

$$\Rightarrow V_B = -2.232 \text{ V}$$


$$I_B = 0.109 \text{ mA}$$

$$I_C = 2.756 \text{ mA}$$

$$\frac{I_C}{I_B} \approx 25.28 < \beta \Rightarrow Q \text{ in saturation region}$$

$$\text{b)} V_O = -10 + 3 \times 2.756 \\ = -1.732 \text{ V}$$

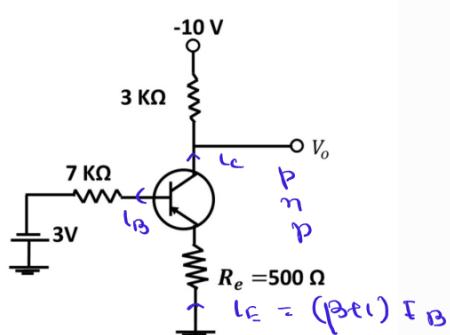c)  $R_E = ?$  Q - to be operate in active region  
 B-E forward & B-C - reverse



Input side,

$$-3 + 7 I_B + 0.7 + (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{2.3}{7 + (\beta + 1) R_E}$$

Output side,

$$-3 + 7 I_B - V_{BC} - 3(\beta I_B) + 10 = 0$$

$V_{BC} > 0$  (for reverse bias)

$$\Rightarrow 7 I_B - 3\beta I_B + 7 > 0$$

$$\Rightarrow (7 - 3\beta) I_B + 7 > 0$$

$$\Rightarrow 7 > 2.9 \beta \frac{2.3}{7 + 101 R_E}$$


$$\Rightarrow 7 + 101 R_E \geq 96.27 \Rightarrow$$

$$\Rightarrow R_E \geq 0.8838 \text{ k}\Omega$$

$$(R_E)_{\min} = 883.8 \Omega$$


3. A transistor circuit is given below (silicon transistor). The transistor has a minimum value of  $\beta=30$

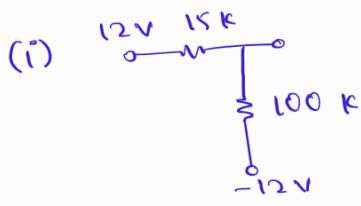- i) Find  $V_o$  for  $V_i = 12V$   
 ii) Find  $V_o$  for  $V_i = 1V$




$$R_{th} = \frac{1500}{115} \text{ k}\Omega = 13.04 \text{ k}\Omega$$
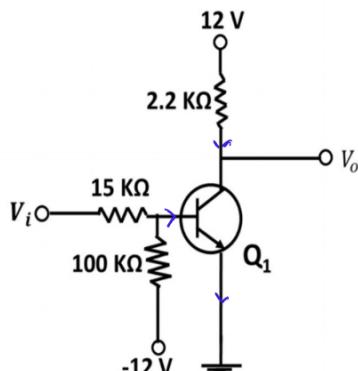
$$V_{th} = \frac{2.4}{115} \times 100 - 12 = 8.87 \text{ V}$$



Assume in cutoff

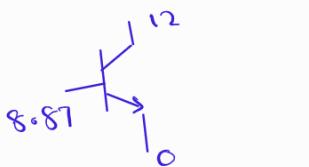$V_B > V_E \Rightarrow$  forward  
 contradiction cutoff



Assume in saturation


$$I_B = \frac{8.87 - 0.8}{13.07} = 0.617 \text{ mA}$$

$$8.87 - 13.04 \times 0.617 - 0.5 + 2.2 I_C = 12$$


$$\Rightarrow I_C = 5.307 \text{ mA}$$

$$\frac{I_C}{I_B} = 8.601 < \beta = 30 \Rightarrow \text{sat}^2 - \text{reg}^2$$
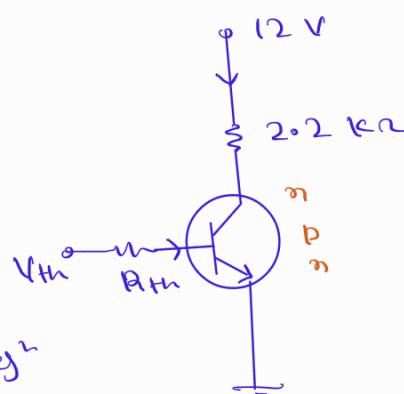
$$V_o = 12 - 2.2 \times 5.307 = 0.3246 \text{ V}$$




$$(ii) V_i = 1V$$

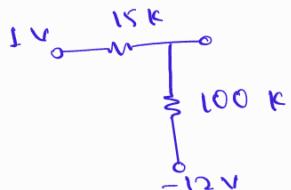

$$R_{th} = \frac{150}{115} k\Omega = 1.3004 k\Omega$$

$$V_{th} = -12 + \frac{13}{115} \times 100 = -0.6956 V$$


Assume cutoff.

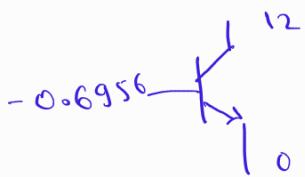

$$V_B < V_E$$

$\Rightarrow$  reverse bias


satisfy cutoff

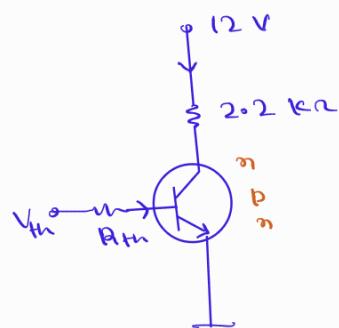


$$V_o = 12 V$$

Q4. Assume  $\beta_{min}=30$ . Find  $V_B$ ,  $V_E$ ,  $I_{C1}$ ,  $I_{C2}$  for the following circuit.


Assume  $Q_1$  &  $Q_2$

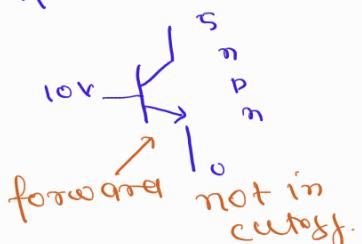

in cutoff

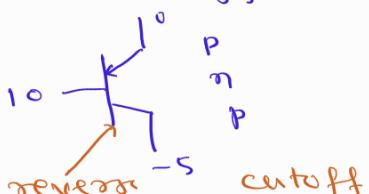

Remove  $-Q_2$

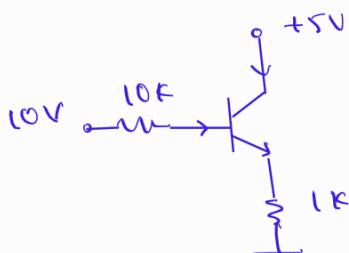


Assume saturation

$$I_B = \frac{10 - 0.5 - 5}{10} = 0.45 \text{ mA}$$

$$\frac{10 - 4.5 - 0.8}{1} = I_E \approx 4.7 \text{ mA}$$


$$I_C = 4.25 \text{ mA} = I_{C1}$$
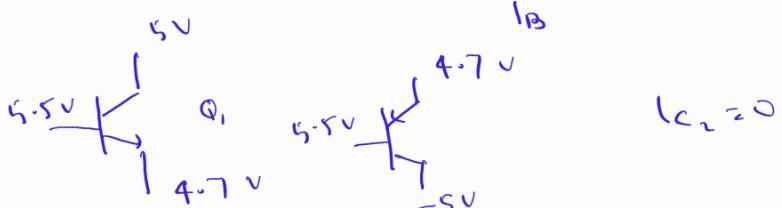
$$\frac{I_C}{I_B} = 9.44 < \beta = 30 \quad \text{saturation region}$$




Q5. For the circuit shown, transistors  $Q_1$  and  $Q_2$  operate in the active region with  $V_{BE1} = V_{BE2} = 0.7 V$ ,  $\beta_1 = 100$ , and  $\beta_2 = 50$ . The reverse saturation current may be neglected.

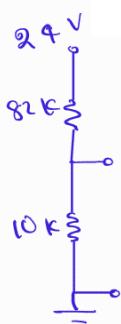
- (a) Find the currents  $I_{B2}$ ,  $I_1$ ,  $I_2$ ,  $I_{C2}$ ,  $I_{B1}$ ,  $I_{C1}$ , and  $I_{E1}$
- (b) Find the voltage  $V_{O1}$  and  $V_{O2}$



$$R_{th} = 82 // 10 = 8.0913 k\Omega$$
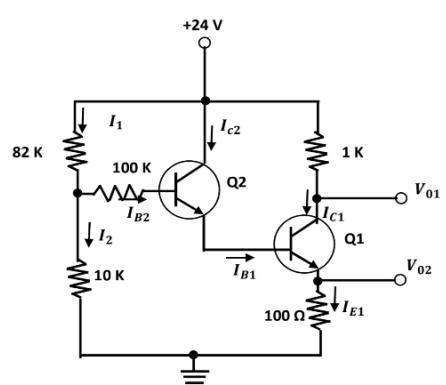
$$V_{th} = \frac{24}{92} \times 10 = 2.608 V$$



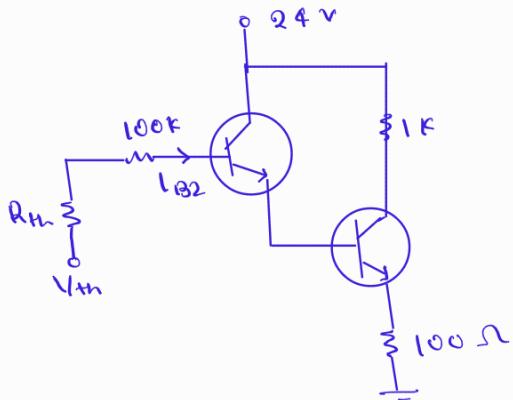

$$I_{B1} = (\beta_2 + 1) I_{B2} \quad I_{C2} = \beta_2 I_{B2}$$

$$I_{E1} = (\beta_2 + 1)(\beta_1 + 1) I_{B2}$$

$$I_{C1} = \beta_1 (\beta_2 + 1) I_{B2}$$

$$2.608 - 108.913 I_{B2} - 0.7 \times 2 - \frac{100 I_{E1}}{1000} = 0$$

$$\Rightarrow I_{B2} = \frac{2.608 - 1.4}{108.913 + 515.1}$$

$$\approx 1.935 \text{ mA}$$

$$\frac{V - 24}{82} + (1.935 \text{ mA}) + \frac{V}{10} = 0$$

$$\frac{V}{82} + \frac{V}{10} = 2.90 \cdot 7.47 \times 10^{-3}$$

$$\Rightarrow V = 2.491 \text{ V}$$

$$I_2 = 0.2591 \text{ mA}$$

$$I_1 = 0.2610 \text{ mA}$$